




RIEPICO IMPEDENZE



$$V = Z_R \cdot I$$


$$Z_R = R$$

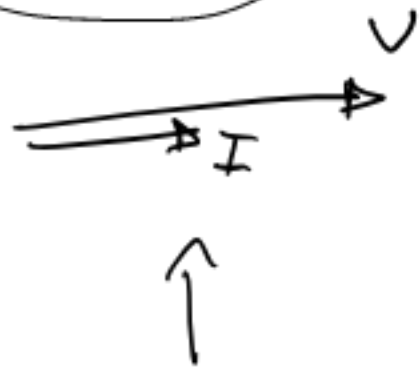

$$V = Z_L \cdot I$$

$$Z_L = jX_L$$


$$X_L = \omega L$$

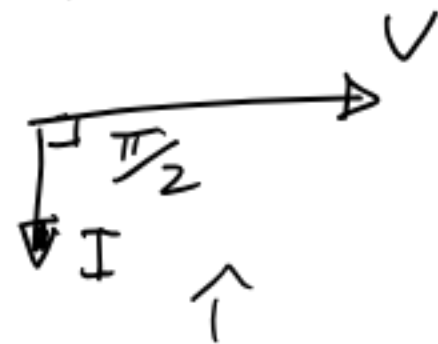

$$V = Z_C \cdot I$$


$$Z_C = -jX_C$$

$$X_C = \frac{1}{\omega C}$$

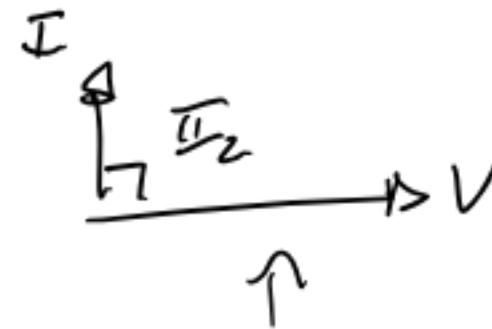

R serie / paralleli.


$$Z = R + jX$$

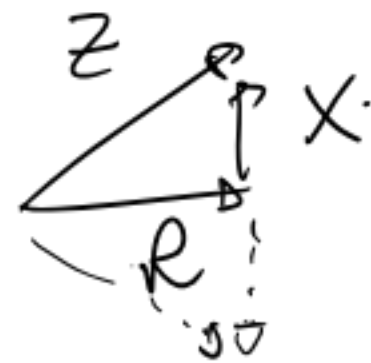

# FILTRO RC

# REGIME SINUSOIDALE

(2)

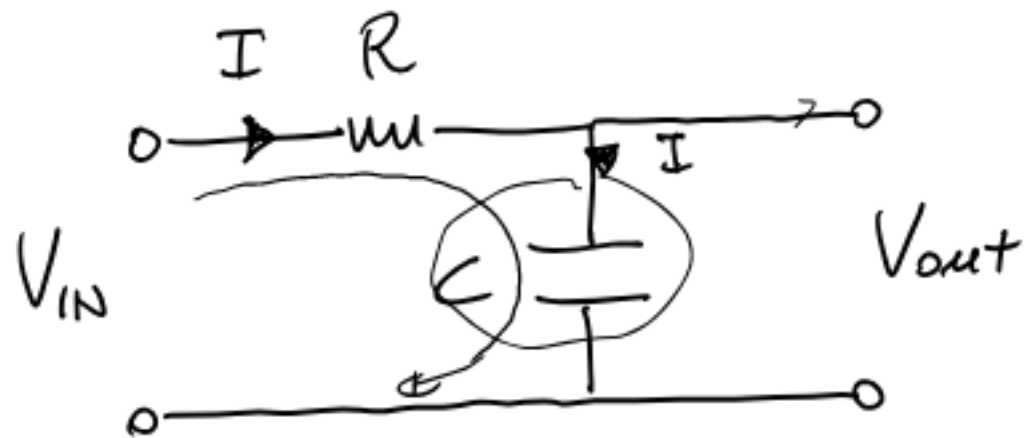

Funzione di trasferimento

$$T = \left| \frac{V_{out}}{V_{in}} \right|$$

$$\bar{T} = \frac{V_{out}}{V_{in}}$$

$$V_{out} = Z_c \cdot I$$

$$I = \frac{V_{in}}{Z}$$

$$Z = R - jX_c$$

$$X_c = \frac{1}{\omega C}$$

$$\bar{T} = \frac{Z_c \cdot I}{V_{in}} = \frac{Z_c V_{in}}{Z V_{in}} = \frac{-jX_c \cdot (R + jX_c)}{R - jX_c \cdot (R + jX_c)} = \frac{X_c^2 - jRX_c}{R^2 + X_c^2}$$

$$|\bar{T}| = T = \frac{1}{R^2 + X_c^2} \sqrt{X_c^4 + R^2 X_c^2} = \frac{X_c}{\sqrt{R^2 + X_c^2}} = \frac{X_c}{\omega C \sqrt{R^2 + \frac{1}{\omega^2 C^2}}} = \frac{1}{\sqrt{1 + (\omega RC)^2}}$$


$$T = \frac{1}{\sqrt{1 + (\omega RC)^2}} = \begin{cases} \omega \rightarrow 0 & \rightarrow 1 \\ \omega \rightarrow \infty & \rightarrow 0 \end{cases}$$

$\left( \frac{V_{out}}{V_{in}} \right)$   
 $\omega = 2\pi f$

$V_{out} \approx V_{in}$   
 $V_{out} \approx 0$

**FILTRO PASSA BASSO**


(3)

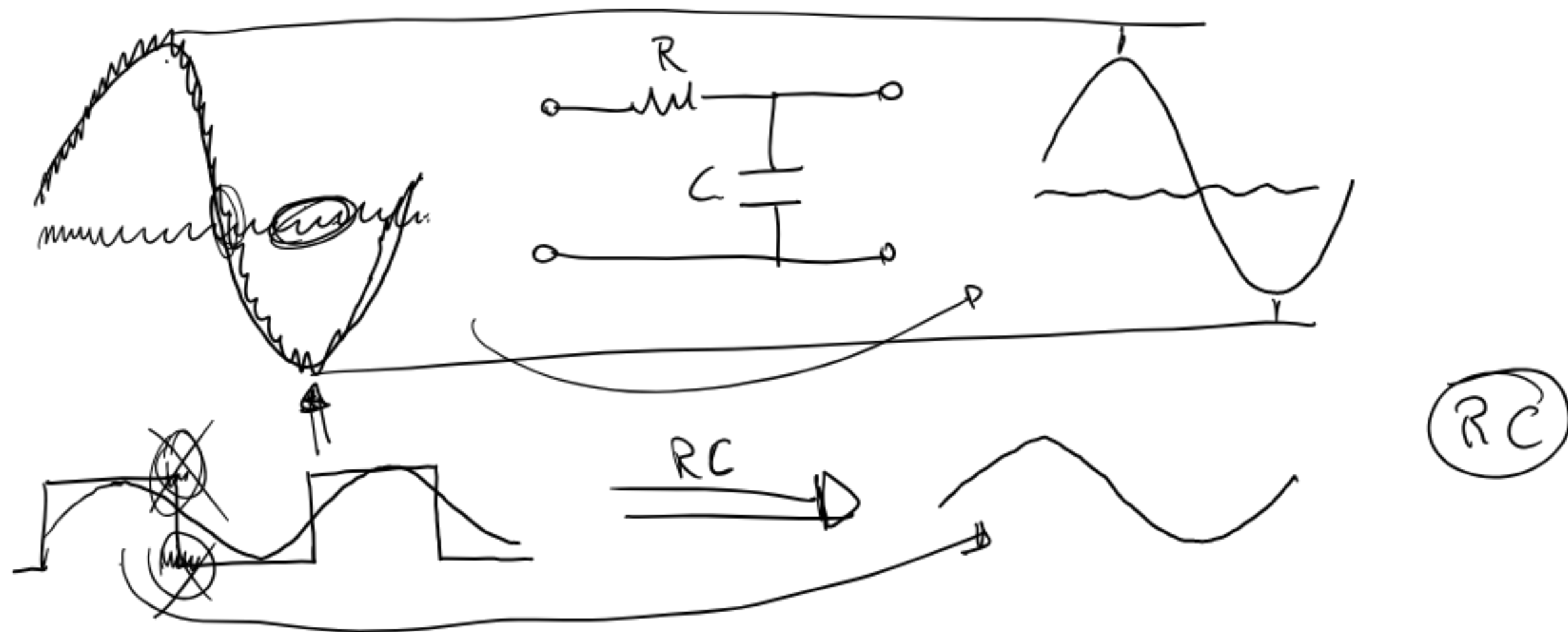

Es. appl. filtro RC

"trasformare" segnale PWM  
in segnale analogico continuo.

PWM → Analogico.

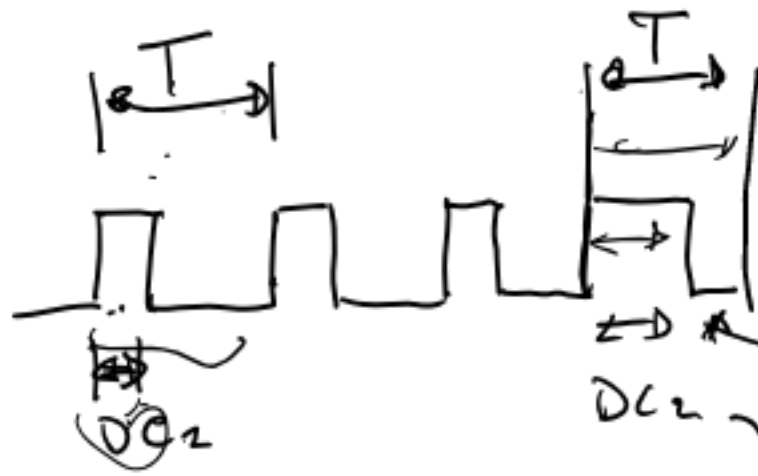




Temp. in

PWM

$DC \propto Temp.$

20 sensori

20 PWM

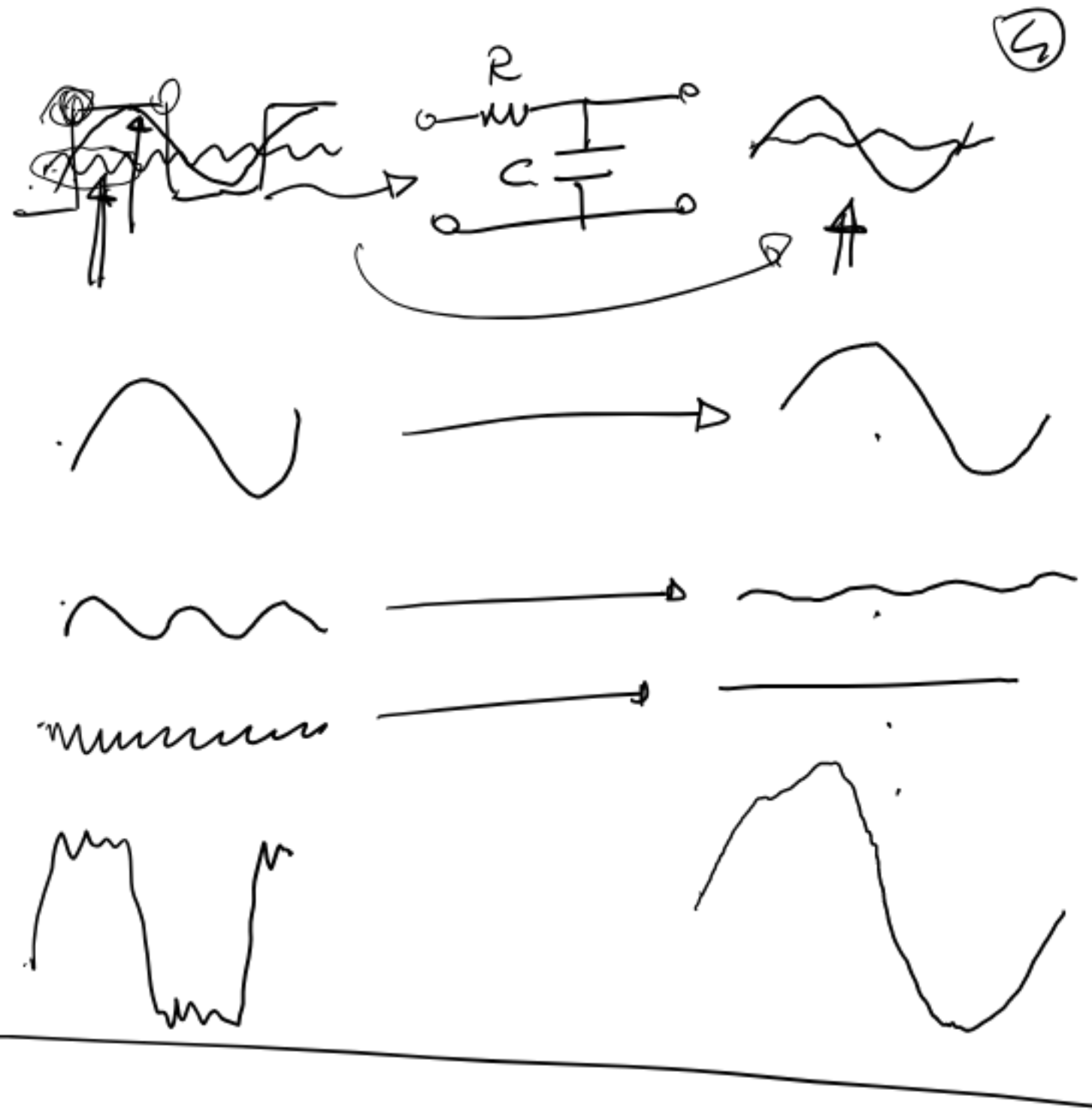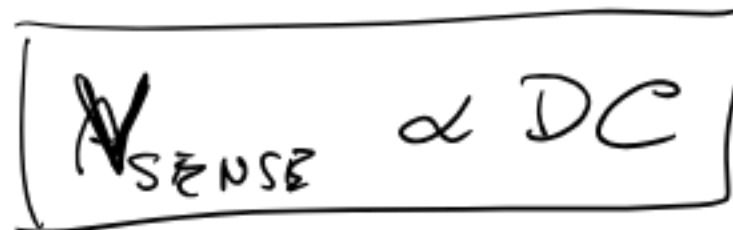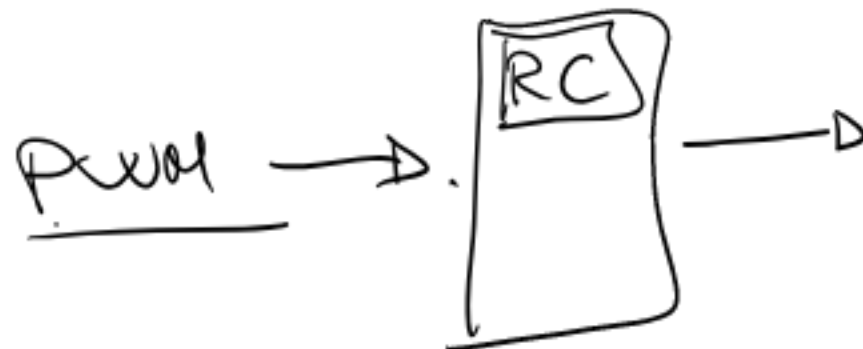


Filtra smontare tutte  
Annonche !!!






$$f(t) = a_0 + \sum \text{armonici}$$

$$a_0 = \frac{1}{T} \int_0^T f(t) dt$$

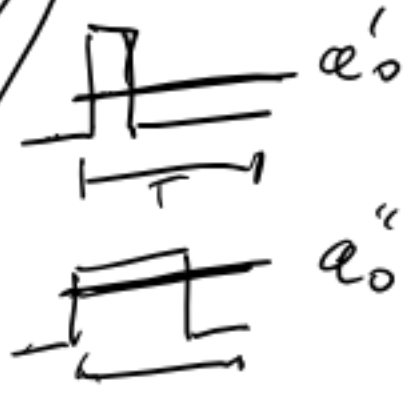




RC

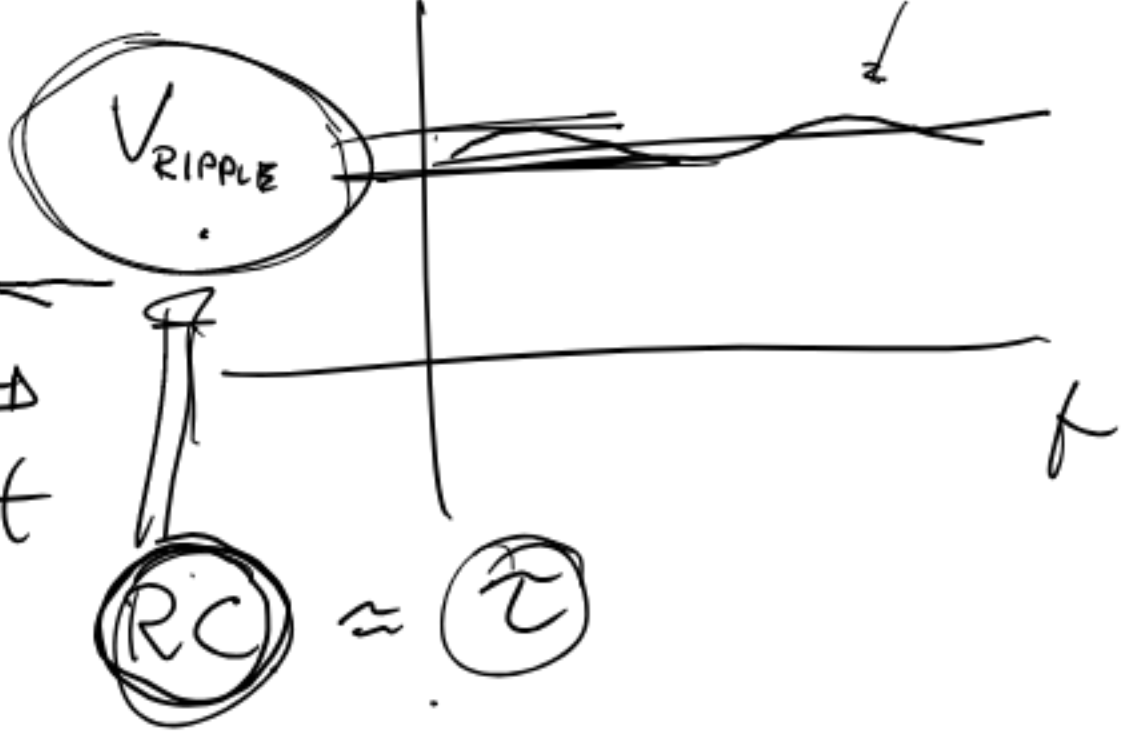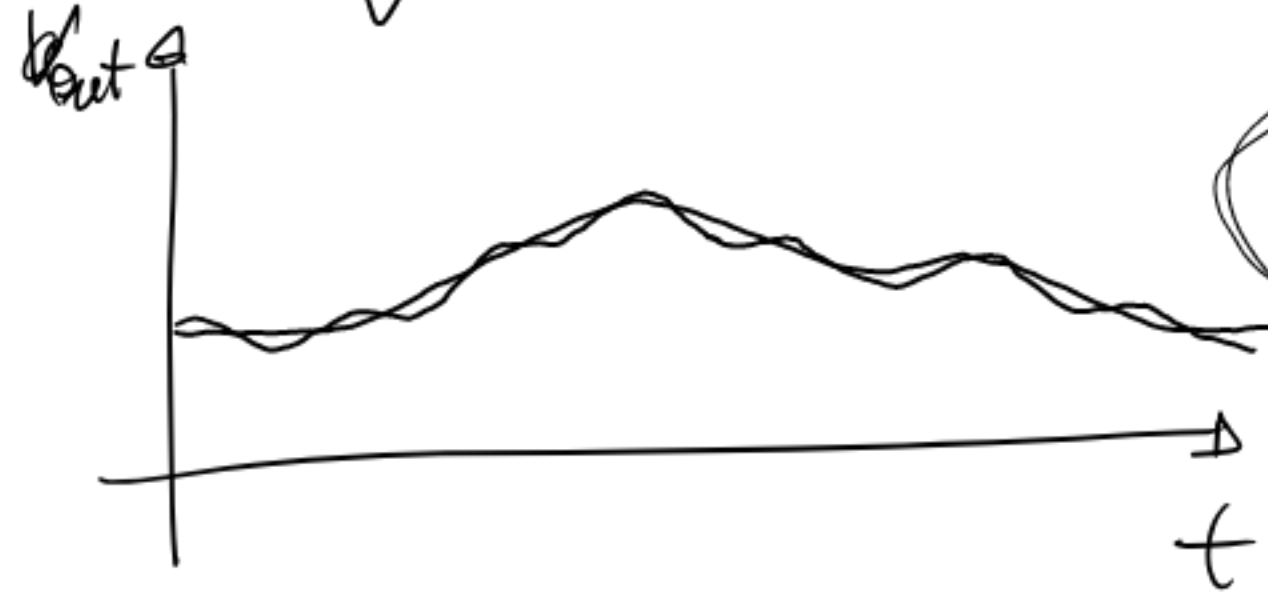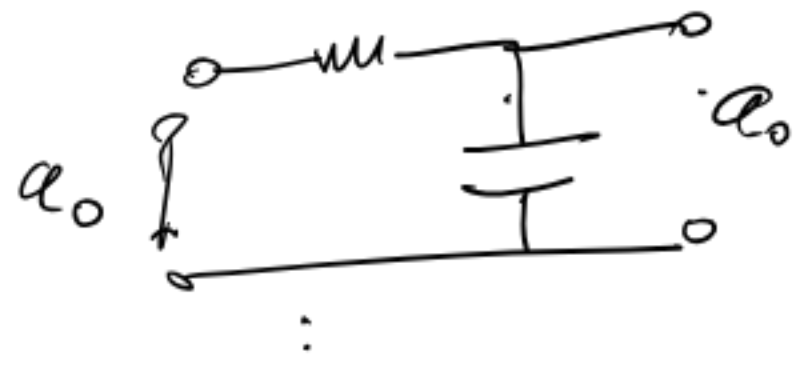

Temp






Pulse Width Modulation

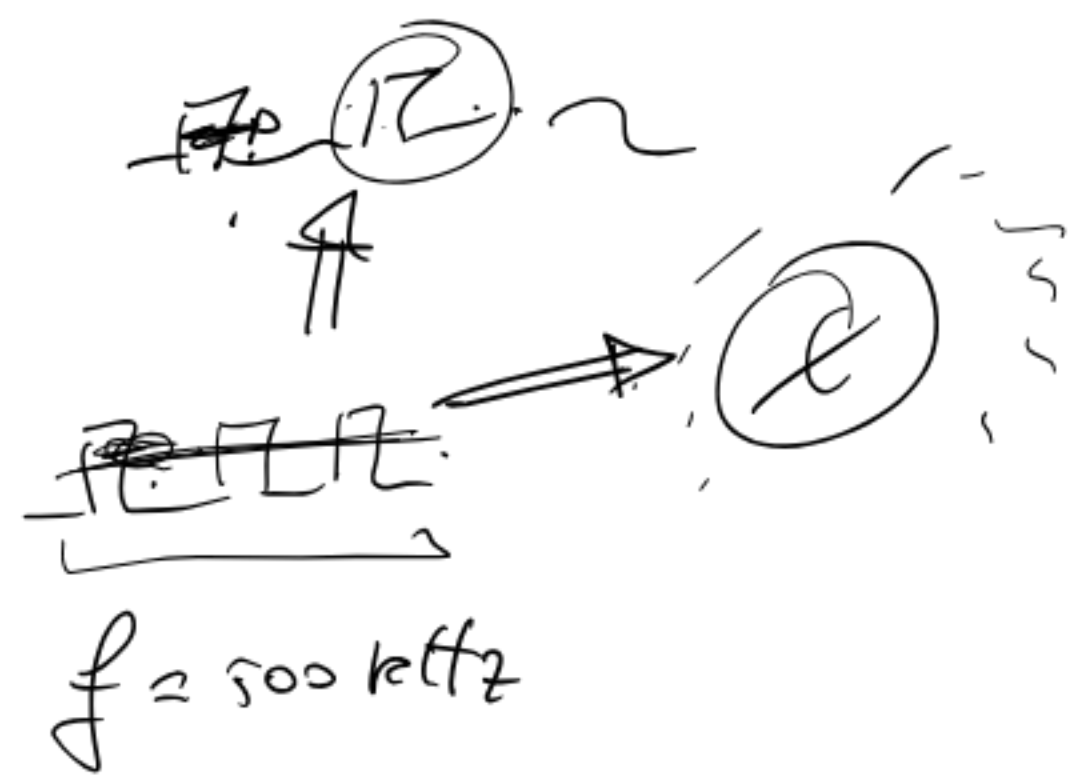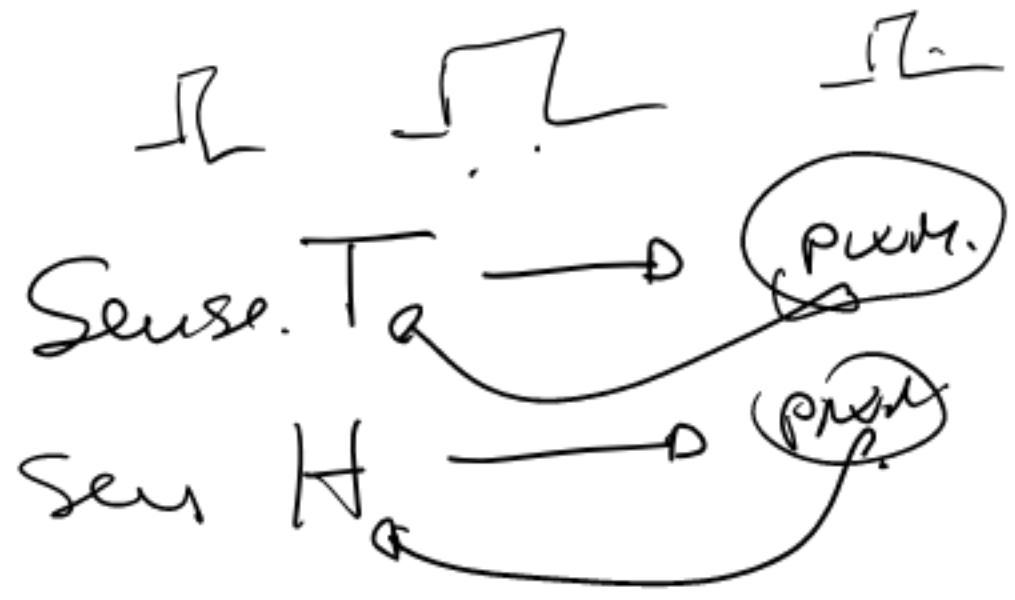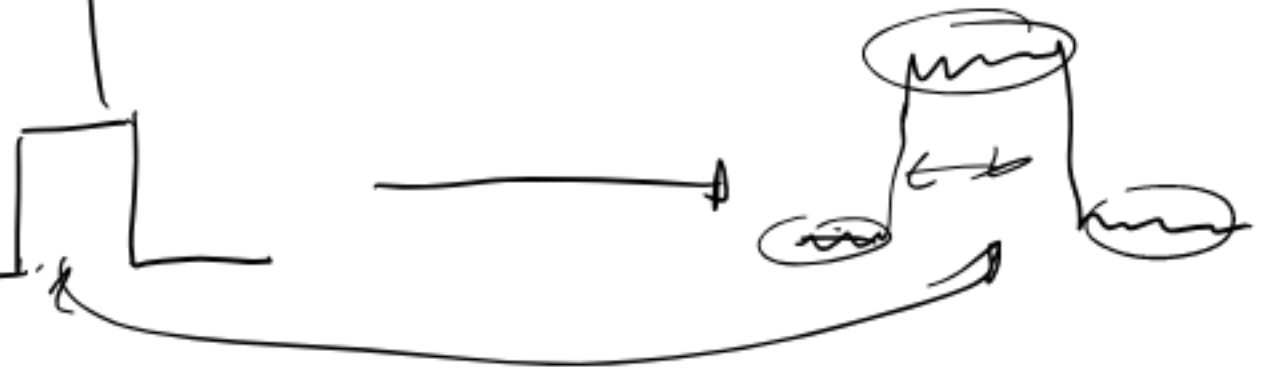




FILTRO PASSA BASSO

" PASSA ALTO

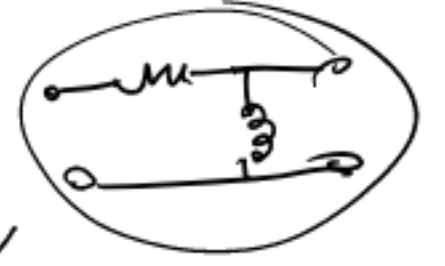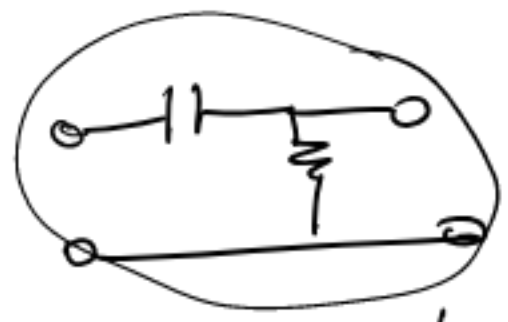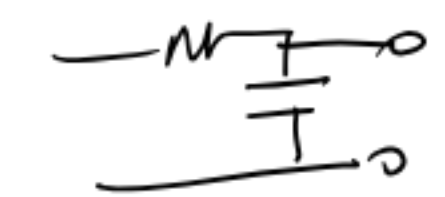

RC
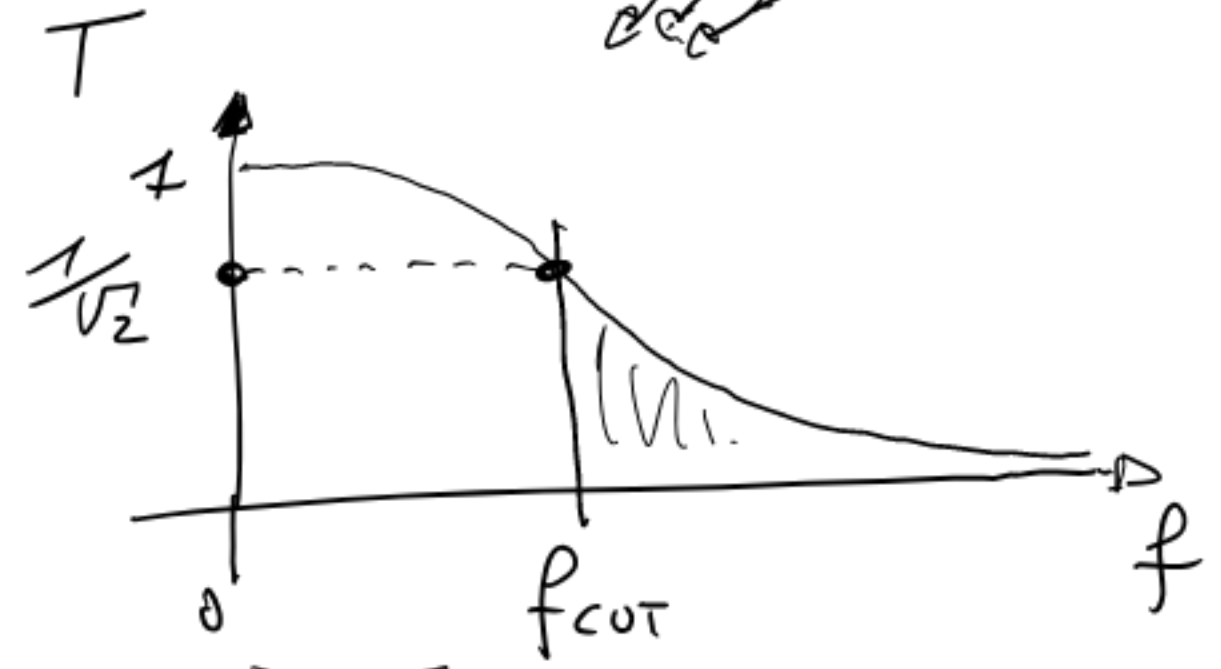
$$T = \frac{1}{\sqrt{1 + (2\pi fRC)^2}}$$



Def

$f_{cUT}$

$$T = \frac{1}{\sqrt{2}} \approx 0,70... = \boxed{70\%}$$

$$2\pi fRC = 1$$

$$f_{cUT} = \frac{1}{2\pi RC}$$

CR

PASSA ALTO


$T =$

$$\frac{1}{\sqrt{1 + (\omega RC)^2}}$$

$\omega \rightarrow 0 \rightarrow 1$   
 $\omega \rightarrow \infty \rightarrow 0$


PASSA ALTO

RC passa baixo  
CR passa alto

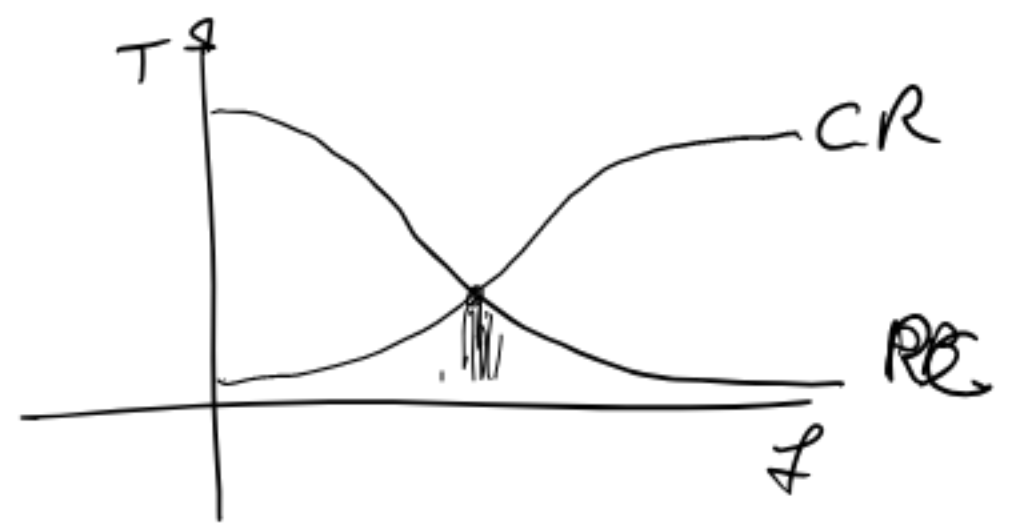

PASSA BANDA ?

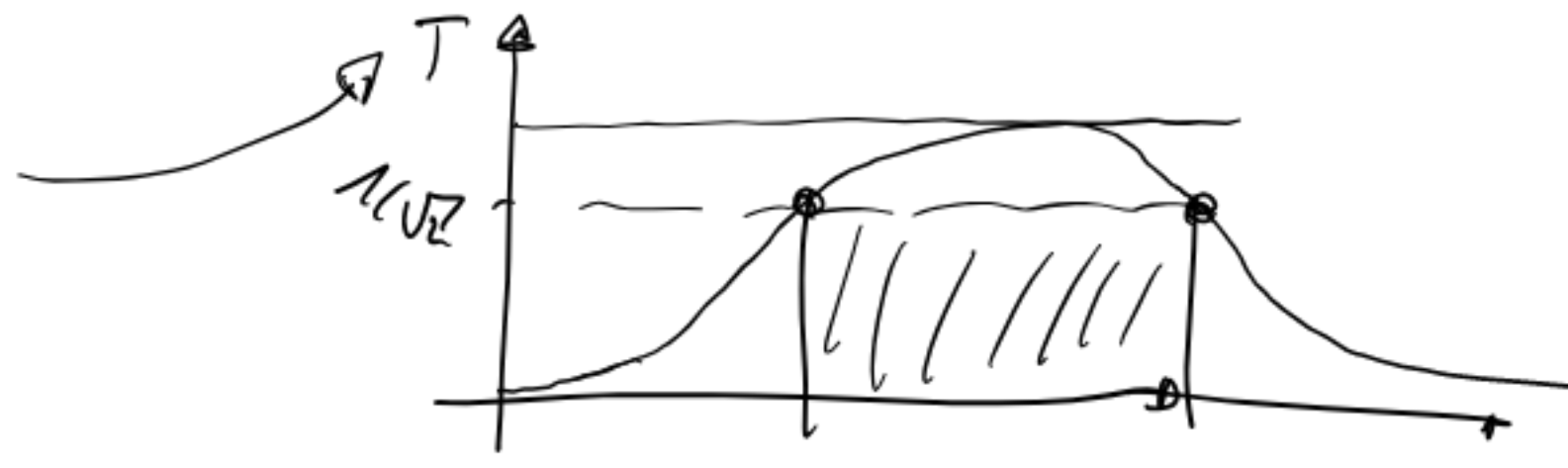$\times$   $f_{FW} \div f_{MAX}$   $\times$




$f_{SIG} = 1 \text{ kHz}$

$f_{EL} = 50 \text{ Hz}$

$f_{CEU} = 1 \text{ MHz}$



50 Hz

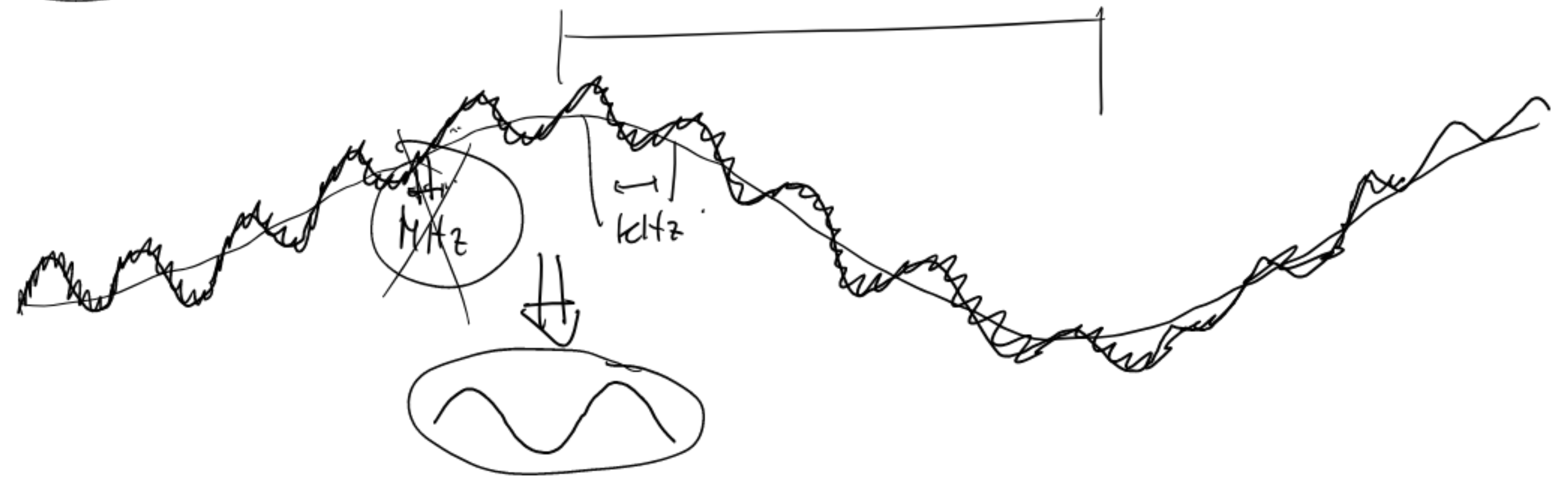



PASSA BANDA

RC + CR

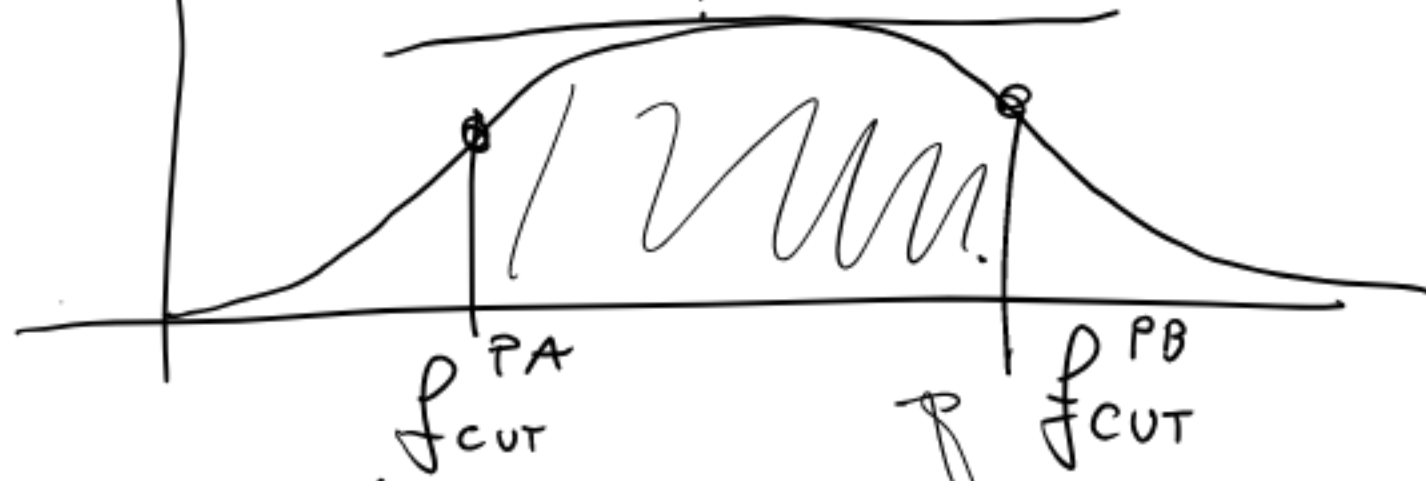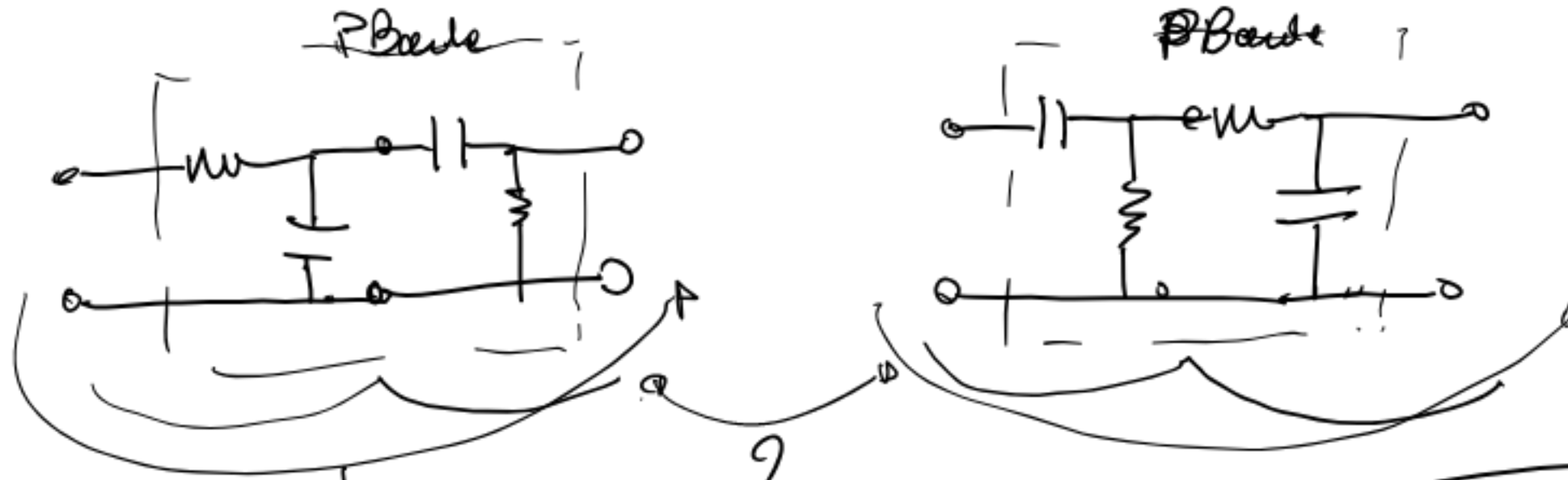

$$f_{CUT}^{PB} > f_{CUT}^{PA}$$



T (dB)

$T(dB) = 10 \cdot \log_{10}(T)$

T dB      0

                  ↓

$T(dB) = -1.5$