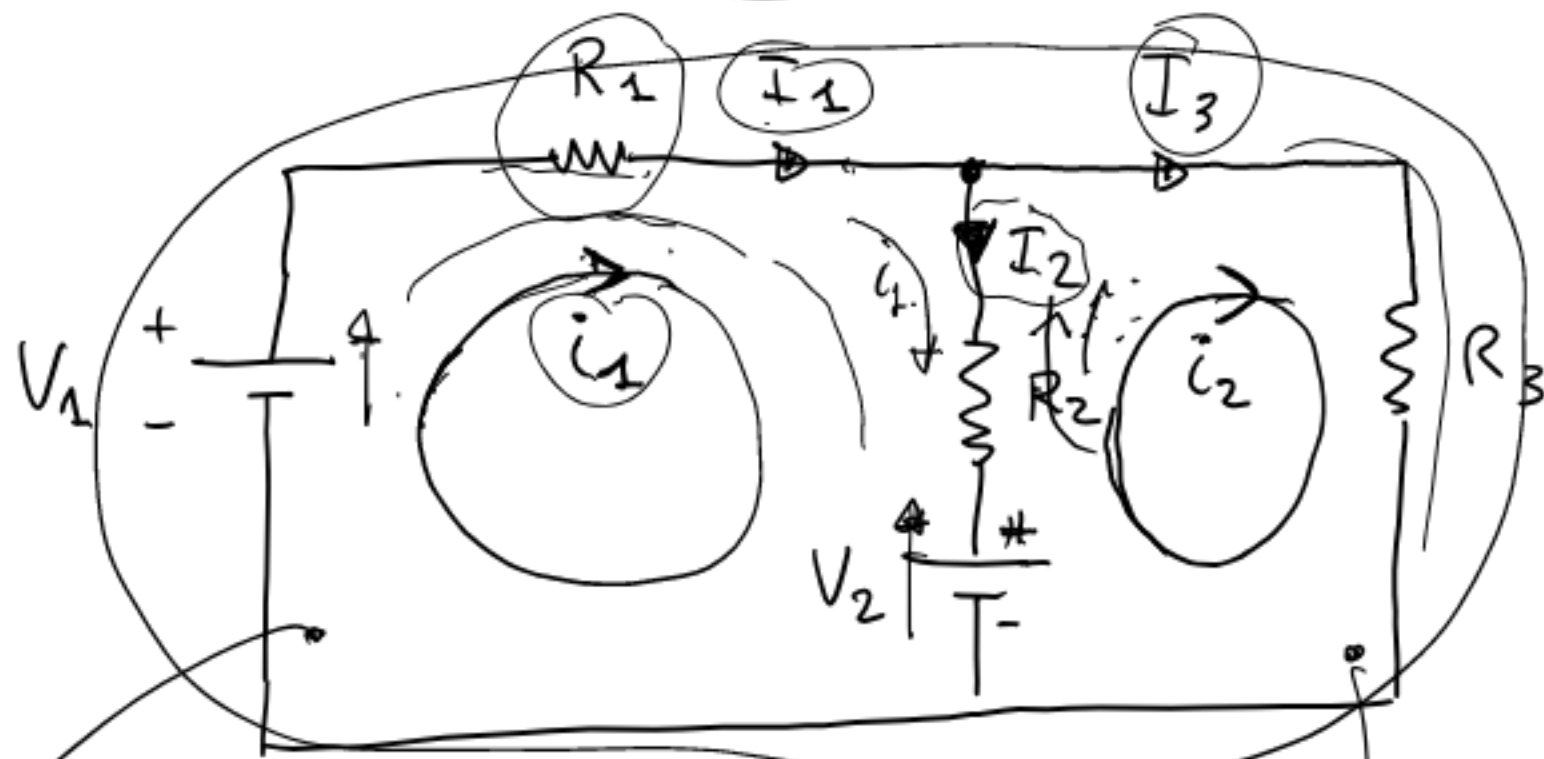


# STUDIO DI UNA RETE ELETTRICA

①



o)  $V_1, V_2, R_1, \dots \Rightarrow I_1, I_2, I_3?$

o)  $V_1, R_1, \dots, \boxed{I_2} \Rightarrow \textcircled{V_2}?$   
 $\begin{matrix} I_1 \\ I_3 \end{matrix}$

$$\sum f_{\text{ext}} = \sum R i$$

$$\begin{cases} V_1 - V_2 = R_1 \cdot i_1 + R_2 \cdot i_1 \\ V_2 = R_2 \cdot i_2 + R_3 \cdot i_2 \end{cases}$$

Corrente maglia

$i_1, i_2 \Rightarrow$

$$\underline{I_2 = i_1 - i_2}$$

$I_1 = i_1$   
 $I_3 = i_2$

~~$I_1$~~   $I_1 = I_2 + I_3$

$I_2 = I_1 - I_3$   
 $\begin{matrix} \uparrow & \uparrow \\ I_1 & I_3 \end{matrix}$

# CONDENSATORE

$C = \frac{Q}{V}$

$[F] = \text{Farad.}$

$q(t) = C \cdot V(t)$




$\int P(t) dt = \frac{dW}{dt}$

Circuito con C combinato :

- T. TRANSITORIO
- Regime

$i(t) = \frac{dq(t)}{dt} = C \cdot \frac{dV(t)}{dt}$

$i(t) = C \cdot \frac{dV(t)}{dt}$

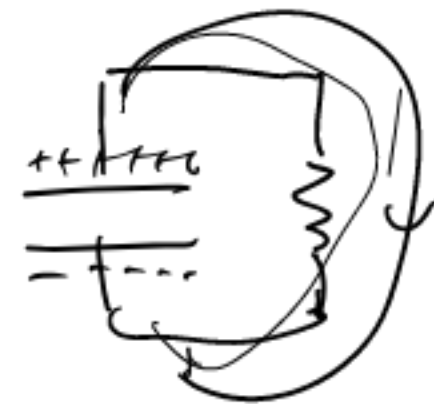


$W = \int_0^{+\infty} P(t) dt = \int_0^{+\infty} V(t) \cdot i(t) dt = C \int_0^{+\infty} V(t) \frac{dV(t)}{dt} dt =$

$= C \int V dV = \frac{1}{2} C \cdot V^2$

# TRANSITORIO CONDENSATORIZ RC

③

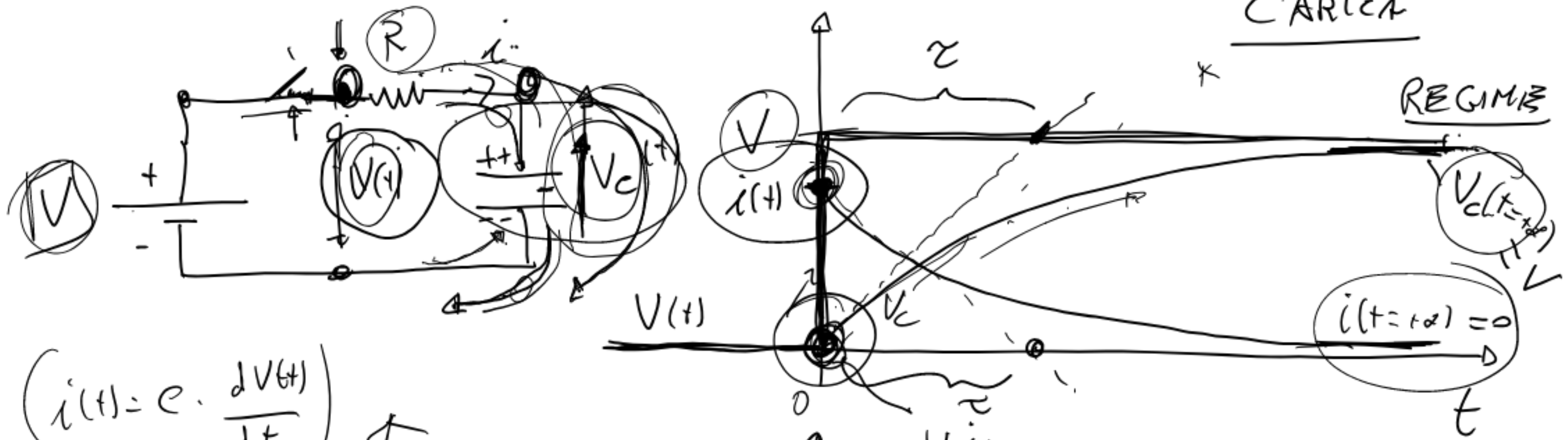

$$i(t) = C \cdot \frac{dV(t)}{dt}$$

$$R_c = 0$$

$$i(t=0) = \frac{V}{R}$$


$$\tau = R \cdot C$$

$$\left. \begin{aligned} V_c(t) &= V \left( 1 - e^{-\frac{t}{\tau}} \right) \\ i(t) &= \frac{V}{R} e^{-\frac{t}{\tau}} \end{aligned} \right\}$$


REGIME  
4/5  $\tau$

# RC SCARICA

4

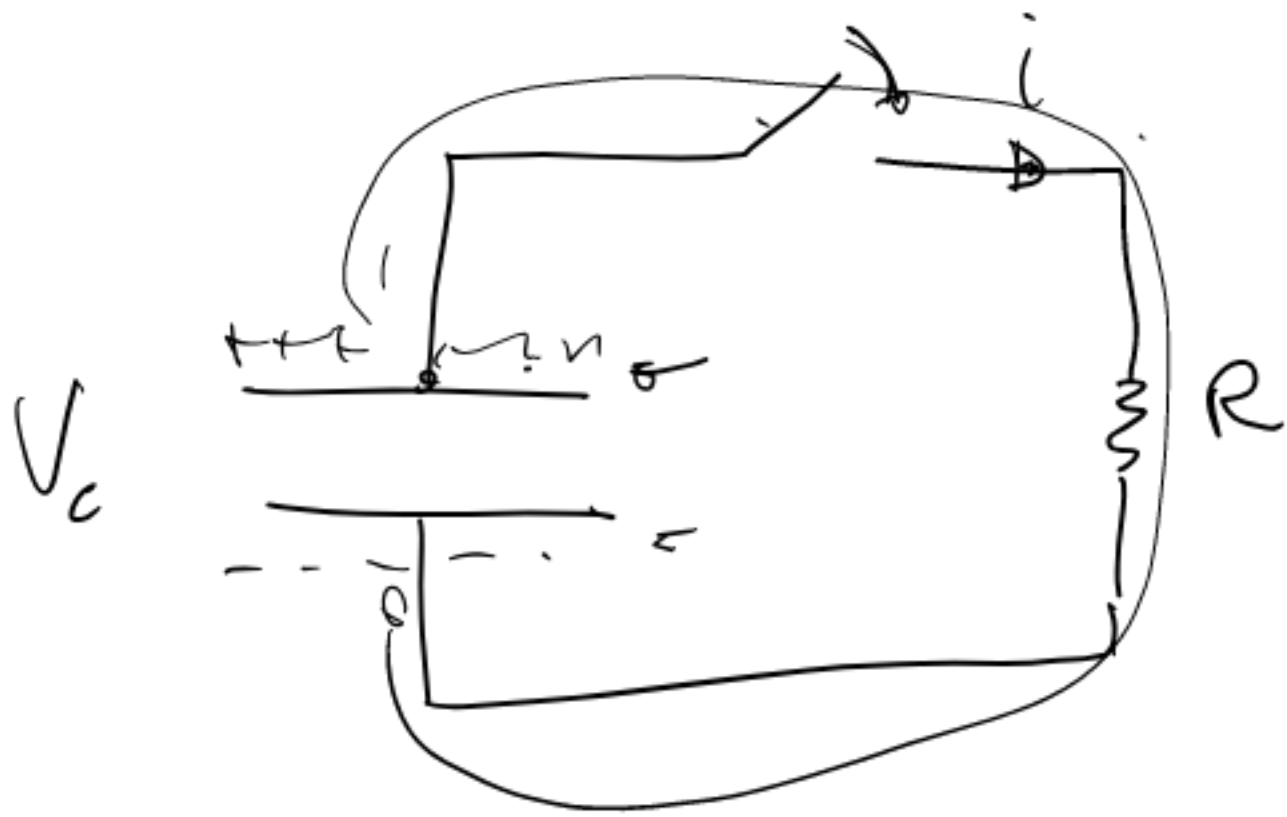


$$V_R = R \cdot i$$

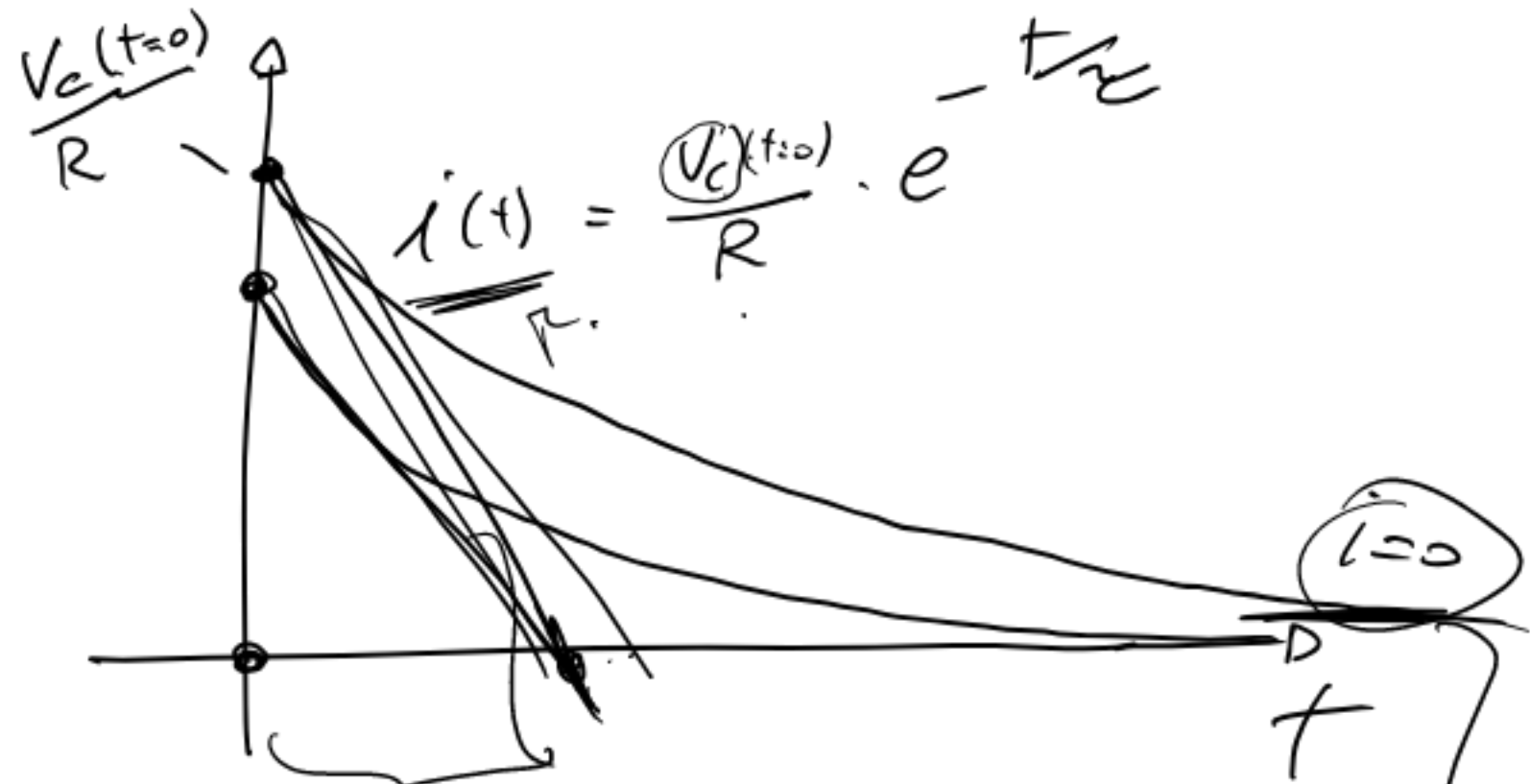

$$V_c(t) = V_c(0) \cdot e^{-\frac{t}{\tau}}$$

4/5 tau

# INDUTTANZA

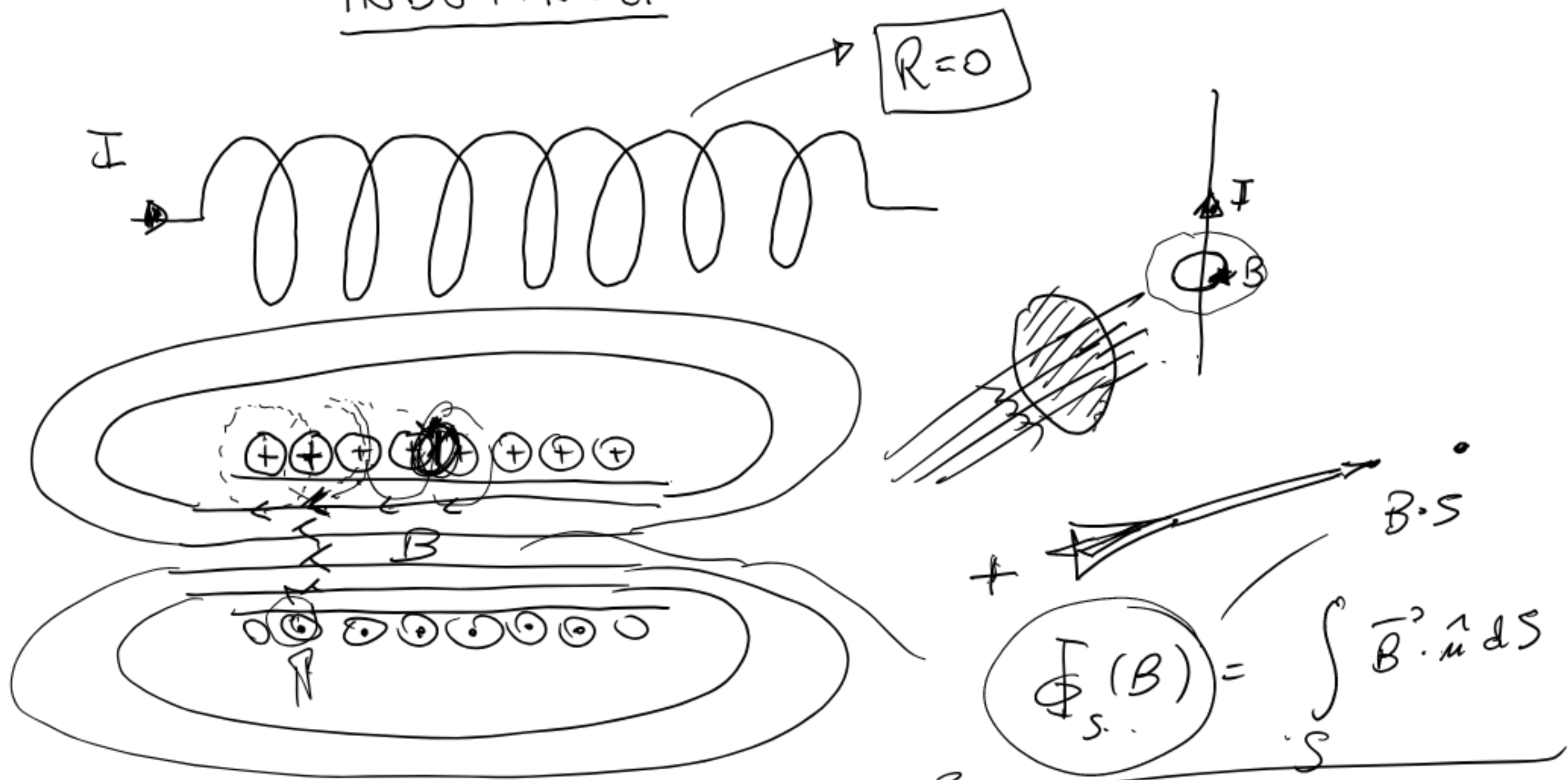

$R=0$

## COEFFICIENTE DI AUTOINDUZIONE

$$\Phi(B) = L \cdot I$$



$L$

Henry [H]

$i(t) \Rightarrow B(t) \Rightarrow \phi_B(t)$

LEGGE DI NEUMAN - FARADAY - LENZ

$\mathcal{E} = - \frac{d\phi_B}{dt}$

$\phi_B = L \cdot i$

SI OPPONE ALLA VARIAZIONE

fem. autoindotta

$i(t) \Rightarrow \phi_B$


$\frac{d\phi}{dt} < 0 \Rightarrow \mathcal{E} > 0$

$> 0 \Rightarrow \mathcal{E} < 0$

$V_L(t) = -L \frac{di(t)}{dt}$

$i(t) = C \cdot \frac{dV(t)}{dt}$

# TRANSITORIO RL

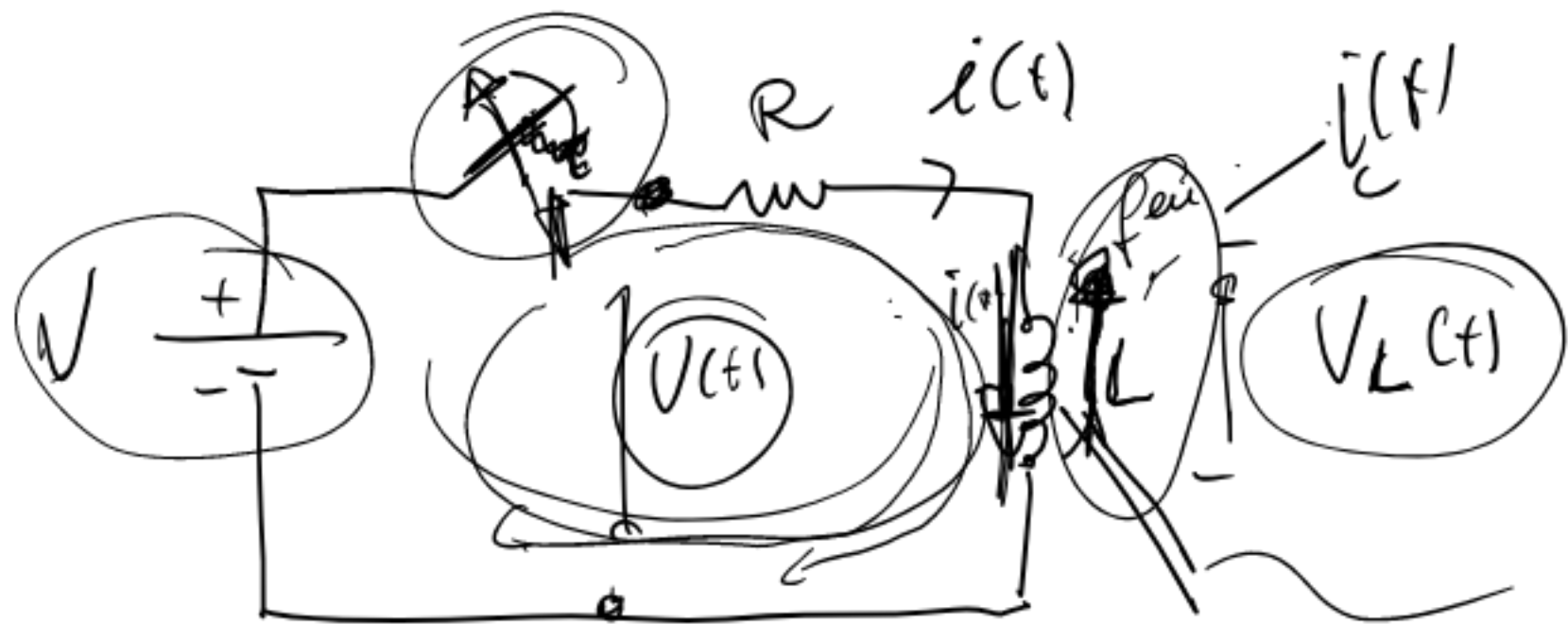

$$W = \frac{1}{2} L I^2$$


$$i(t = +\infty) = \frac{V}{R}$$

$$i(t) = \frac{V}{R} \left( 1 - e^{-\frac{t}{\tau}} \right)$$

$$\tau = \frac{R}{L}$$

L si oppone alle variazioni

$$R_L = 0$$

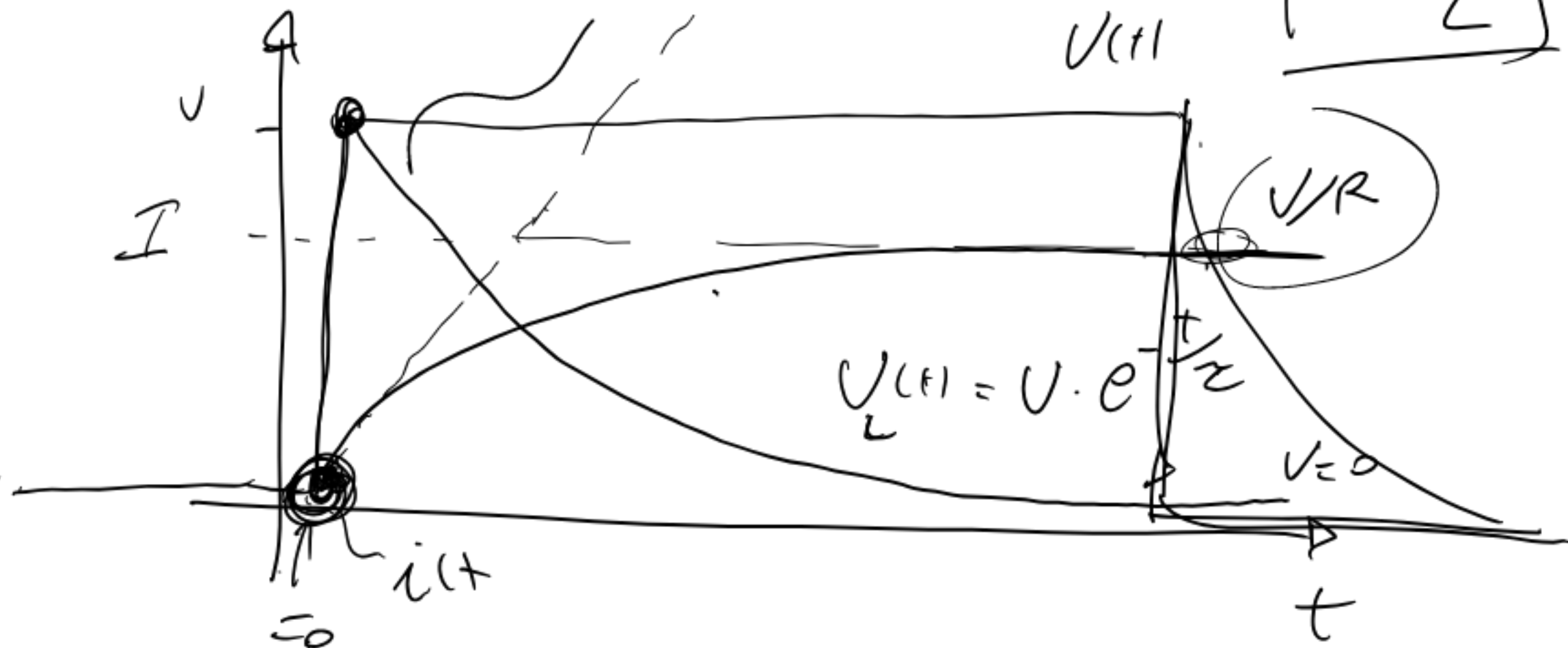

# REGIME SINUSOIDALE R, L, C

$$V(t) = V_0 \sin(\omega t)$$

8


R

$$V(t) = R \cdot i(t)$$

$$i(t) = \frac{V_0}{R} \cdot \sin \omega t$$

$$\begin{aligned} \bar{V} &= V_0 \\ \bar{I} &= \frac{V_0}{R} \end{aligned}$$

V R sono in fase

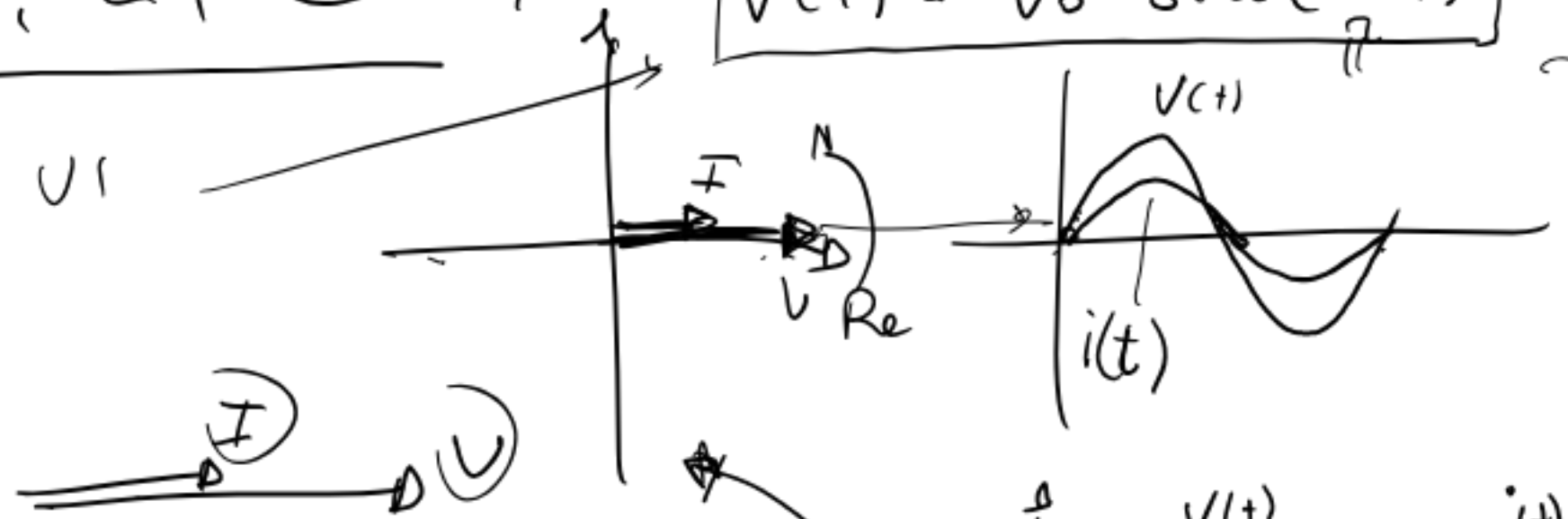


C

$$i(t) = C \cdot \frac{dV(t)}{dt} = \omega C \cdot V_0 \cdot \cos(\omega t)$$

$$\begin{aligned} \bar{V} &= V_0 \\ \bar{I} &= j \omega C \cdot V_0 \end{aligned}$$

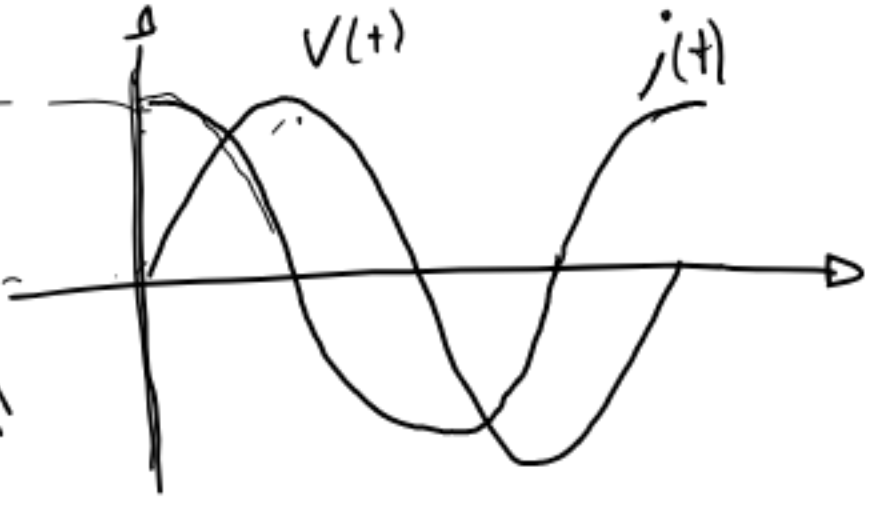I ANTICIPO DI  $\frac{\pi}{2}$  Rispetto a V SFASATA




L



$$\begin{aligned} i(t) &= i_0 \sin \omega t \\ V(t) &= + \omega L i_0 \cos \omega t \end{aligned}$$

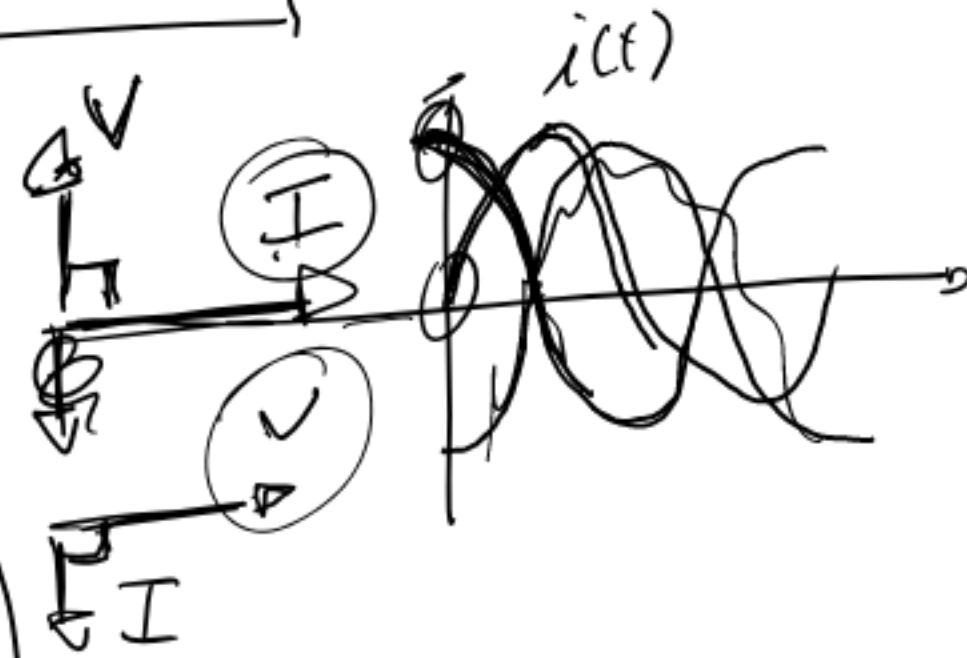I RITARDO DI  $\frac{\pi}{2}$  RISPETTO a V



forme autorisolate



R

$$\bar{V} = R \bar{I}$$

$$\bar{V} = \bar{Z} \cdot \bar{I}$$

IMPEDENZA

C

$$\bar{V} = V_0$$
$$\bar{I} = j\omega C V_0$$

$$\bar{I} = \left[ \frac{1}{\bar{Z}} \right] \bar{V}$$

capacitance

$$\bar{V} = \frac{\bar{I}}{j\omega C} = \bar{Z} \cdot \bar{I}$$

$$\bar{Z}_C = \frac{1}{j\omega C} = -j X_C$$

$X_C$  REATTANZA CAPACITIVA

$$X_C = \frac{1}{\omega C}$$

L



$$i(t) = I_0 \sin \omega t$$
$$v(t) = \omega L I_0 \cos \omega t$$



$$\bar{I} = I_0$$
$$\bar{V} = j\omega L I_0 \Rightarrow$$

$$\bar{V} = [j\omega L] \bar{I} = \bar{Z}_L \cdot \bar{I}$$

$$\bar{Z}_L = j\omega L = j X_L$$


$$X_L = \omega L$$

Reattanza induttiva

impedance puramente induttiva.



$$\bar{Z}_R = R \quad \bar{Z}_L = jX_L$$

$$\bar{Z}_C = -jX_C$$

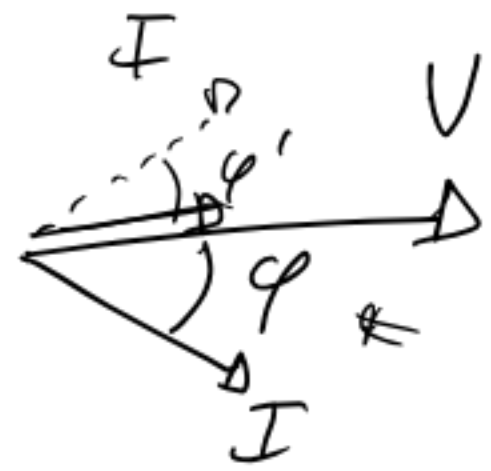

(10)


R serie / parallelo

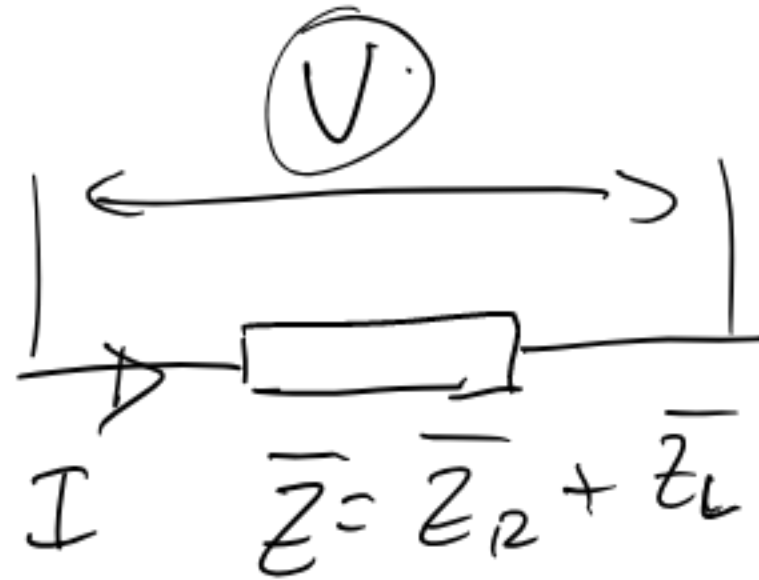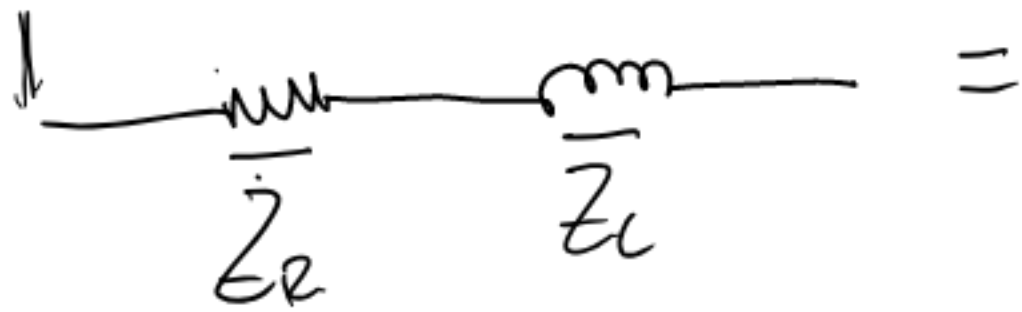

$$\bar{Z} = \bar{Z}_R + \bar{Z}_L = R + jX_L$$



$$\bar{Z} = R - jX_C$$

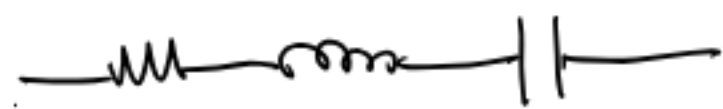

$$\bar{Z} = R + jX_L - jX_C = R + jX$$

$$\bar{Z} = R + jX$$

↑ Resistance
 ↑ REATTIVA




SFASAMENTO

si I rispetto a V

$$\varphi = \arctg \frac{X}{R}$$

data  $\bar{Z} = R + jX$


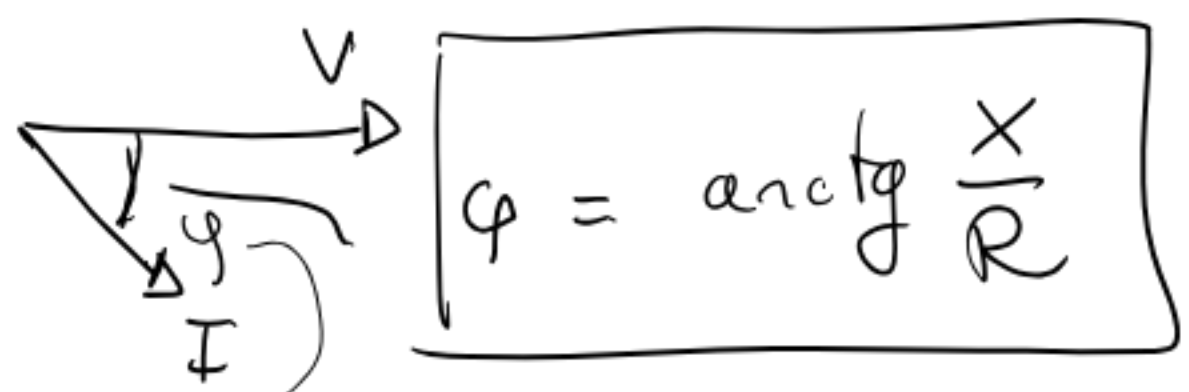


$\bar{V} = V_0$

$\bar{V} = \bar{Z} \cdot \bar{I} \Rightarrow$

$|\bar{I}| = \frac{V}{Z}$  ?

Regime sinusoidale Serie R

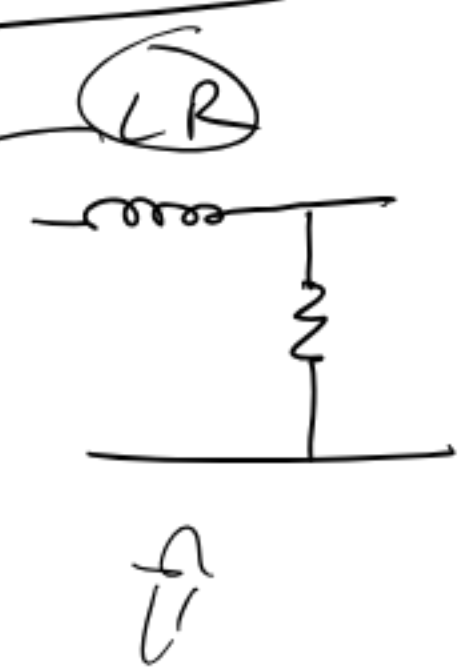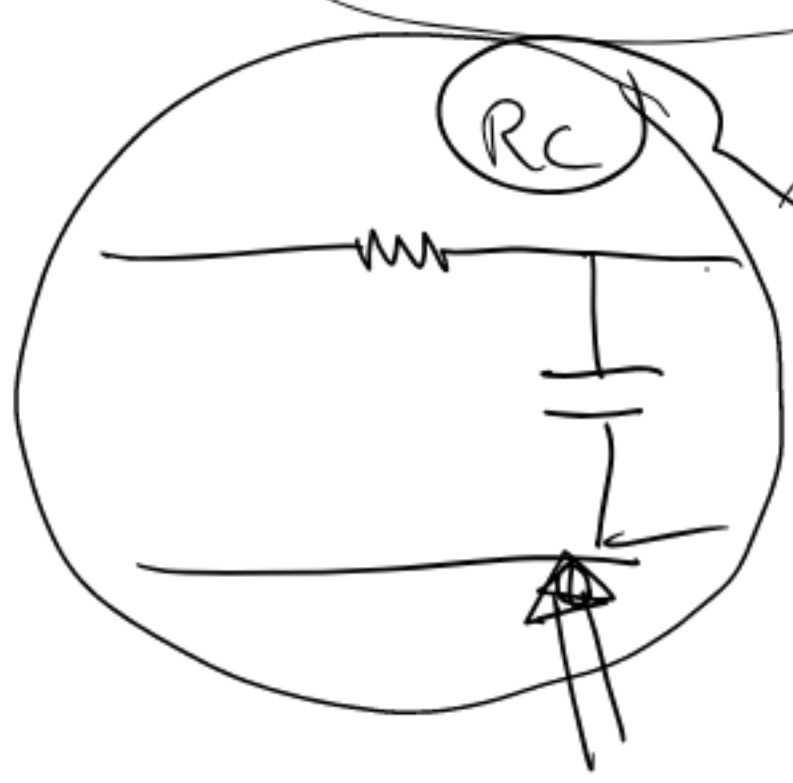

FILTRI