

# FILTRI RC/CR (RL/LR)

Riepilogo

Regime sinusoidale.

② IMPEDENZA

$$Z = R + j \underset{\uparrow}{X}$$

Reattanza

$> 0 \Rightarrow X_L$   
 $< 0 \Rightarrow X_C$

$$Z = R + jX_L - jX_C$$

$$= R + jX$$

$$X = X_L - X_C$$

Hz

$$V = V_0 \sin(\omega t)$$

$$X_L = \omega L$$






$$X_C = \frac{1}{\omega C}$$

$$\omega = 2\pi f$$


RC  $\leftrightarrow$  CR  
 RL  $\leftrightarrow$  LR

I, II KIR...

$$V = Z \cdot I$$

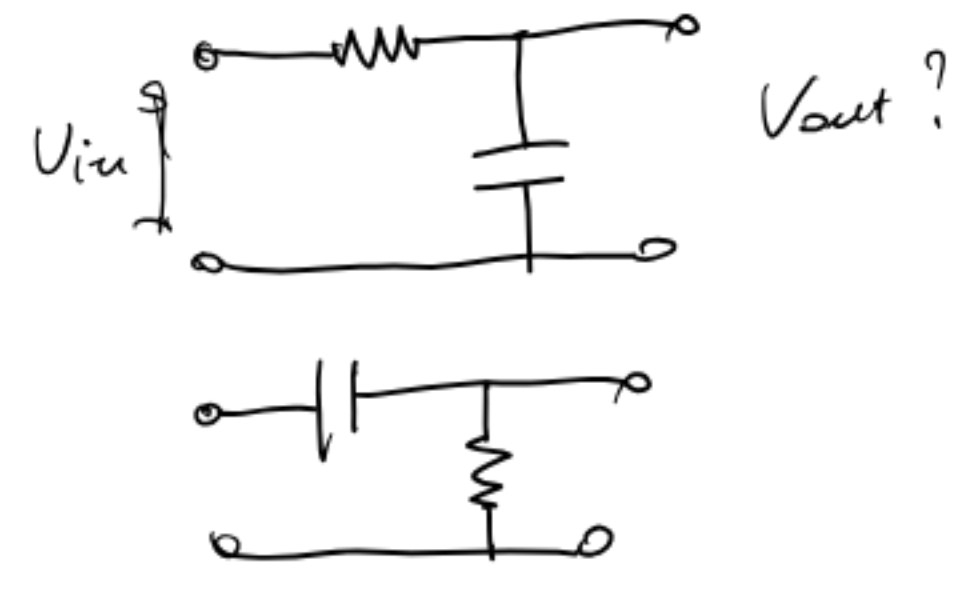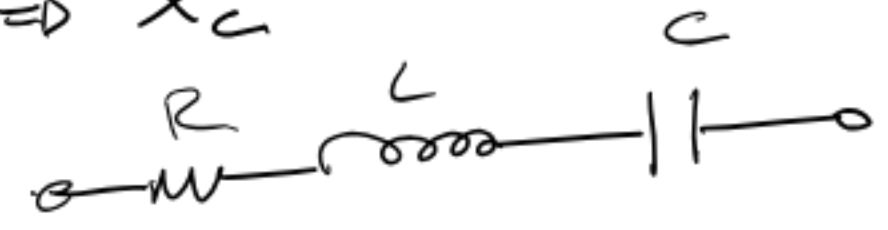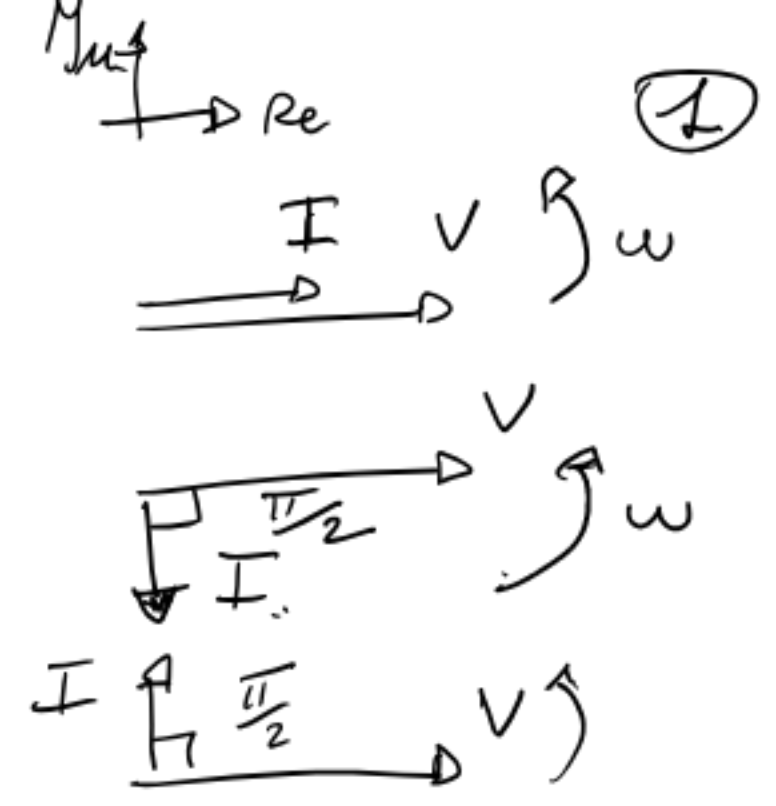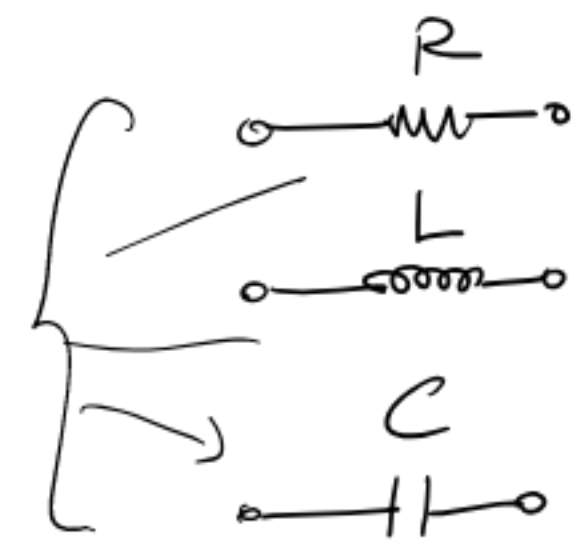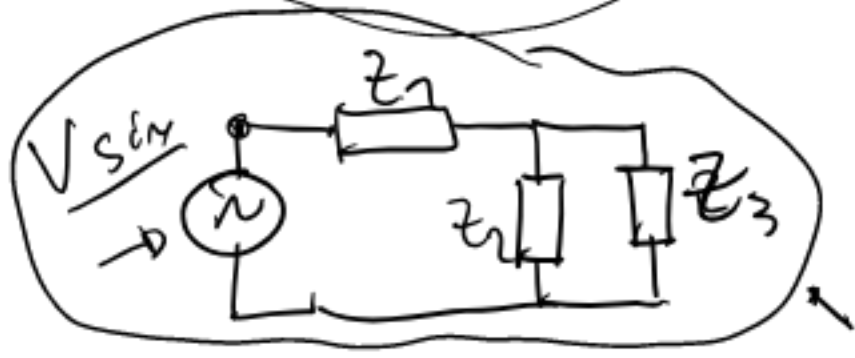

# FILTRO RC

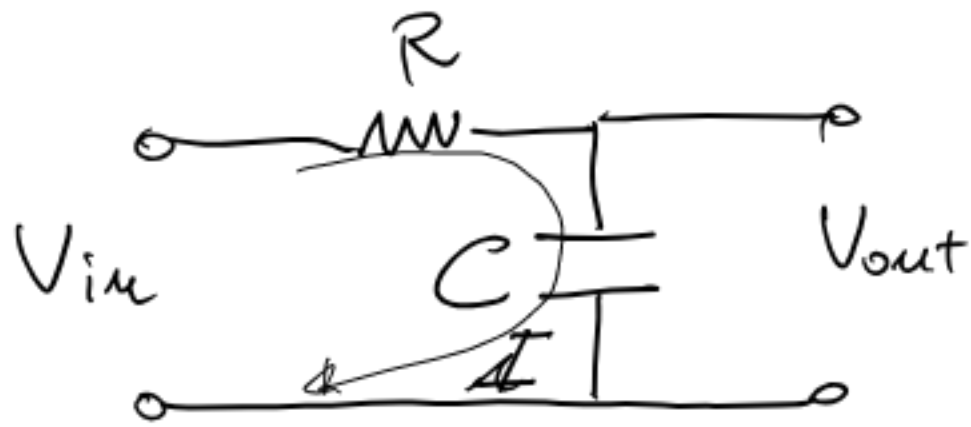

$$V_{out} = Z_C \cdot I$$

$$V_{in} = (Z_R + Z_C) \cdot I \Rightarrow I = \frac{V_{in}}{Z_R + Z_C}$$

$$T = \left| \frac{V_{out}}{V_{in}} \right| = \left| \frac{Z_C}{Z_R + Z_C} \right| \quad Z_R = R \quad Z_C = -jX_C \quad (X_C = \frac{1}{\omega C})$$


$$\frac{Z_C}{Z_R + Z_C} = \frac{-jX_C}{R - jX_C} = \frac{-jX_C (R + jX_C)}{R^2 + X_C^2} = \frac{X_C^2 - jRX_C}{R^2 + X_C^2} = \frac{X_C}{R^2 + X_C^2} (X_C - jR)$$

$$|T| = \frac{X_C}{\sqrt{R^2 + X_C^2}} = \frac{X_C}{\sqrt{R^2 + X_C^2}} = \frac{1}{\sqrt{(\omega RC)^2 + 1}}$$

$$V_{iu} = \underline{V_{in}} \quad \text{Yield } I_{Dro} \quad \boxed{\text{D}}$$

$$V_{out} = f(V_{iu})$$

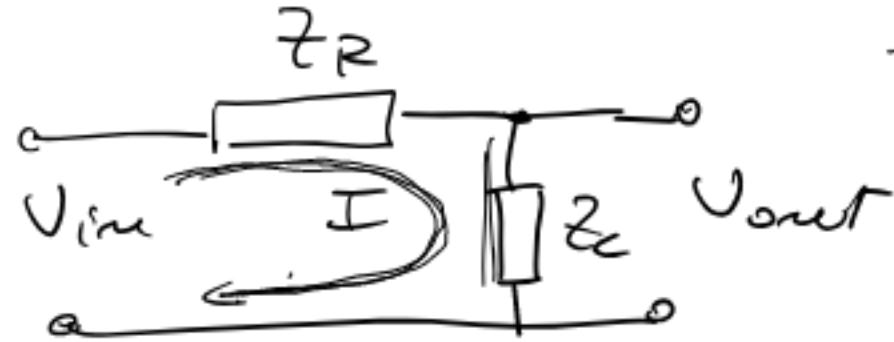Funzione di trasferimento  $T = \left\{ \frac{V_{out}}{V_{in}} \right\}$






$$V_{out} = \frac{Z_C}{Z_R + Z_C} \cdot V_{in}$$

$|T| = \frac{1}{\sqrt{1 + (\omega RC)^2}}$

$\omega \rightarrow 0 \rightarrow 1 \rightarrow |V_{out}| \approx |V_{in}|$

$\omega \rightarrow +\infty \rightarrow 0 \rightarrow |V_{out}| \approx 0$




FILTRO PASSA-BASSO (RC)

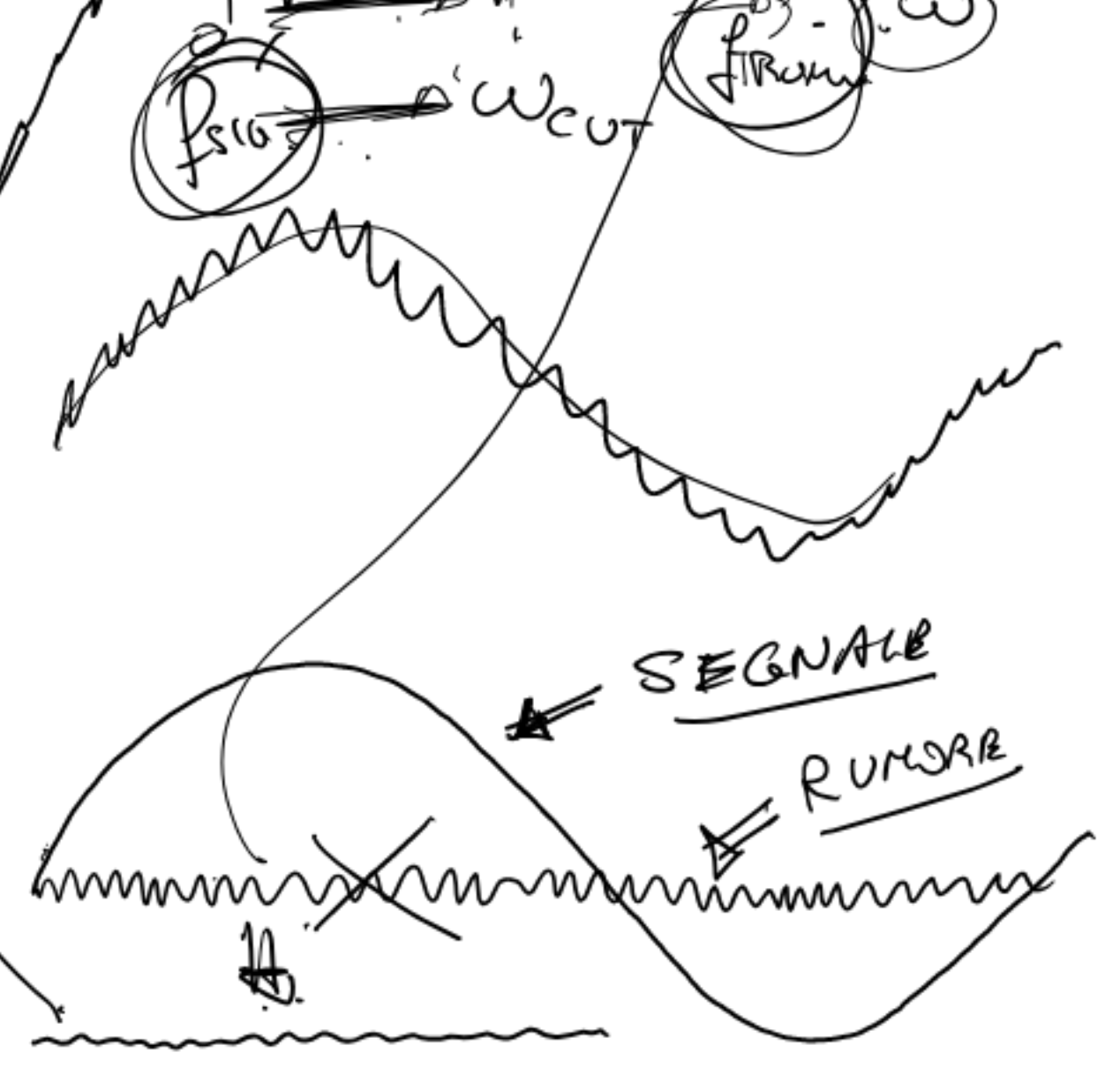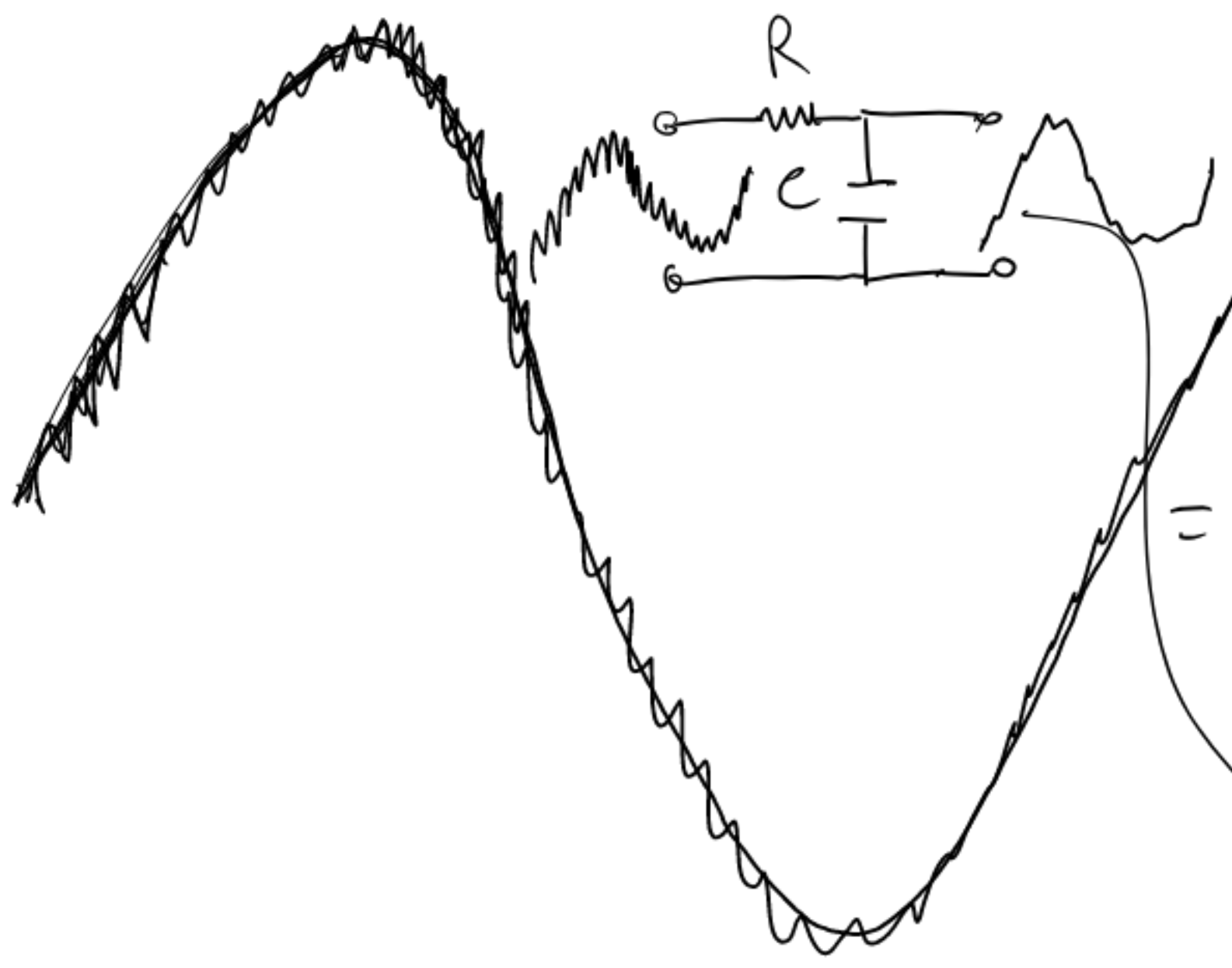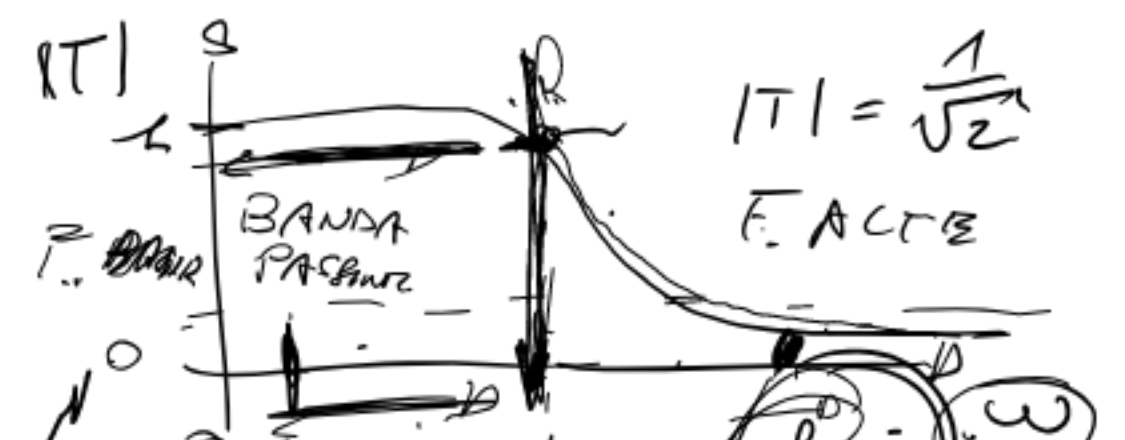

$$\frac{V_{out}}{V_{in}} = \frac{Z_C}{Z_R + Z_C} = \frac{X_C}{R^2 + X_C^2} (X_C - iR)$$

$\frac{V_{out}}{V_{in}}$  sfasato rispetto ④
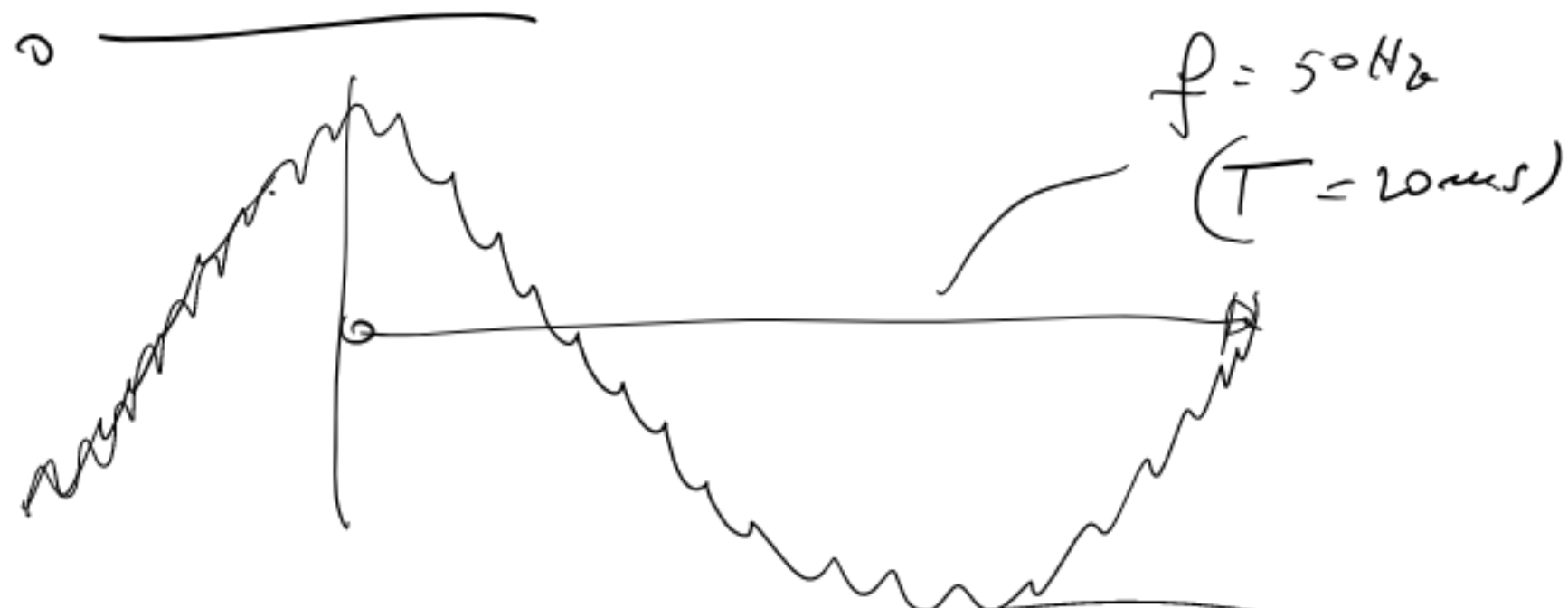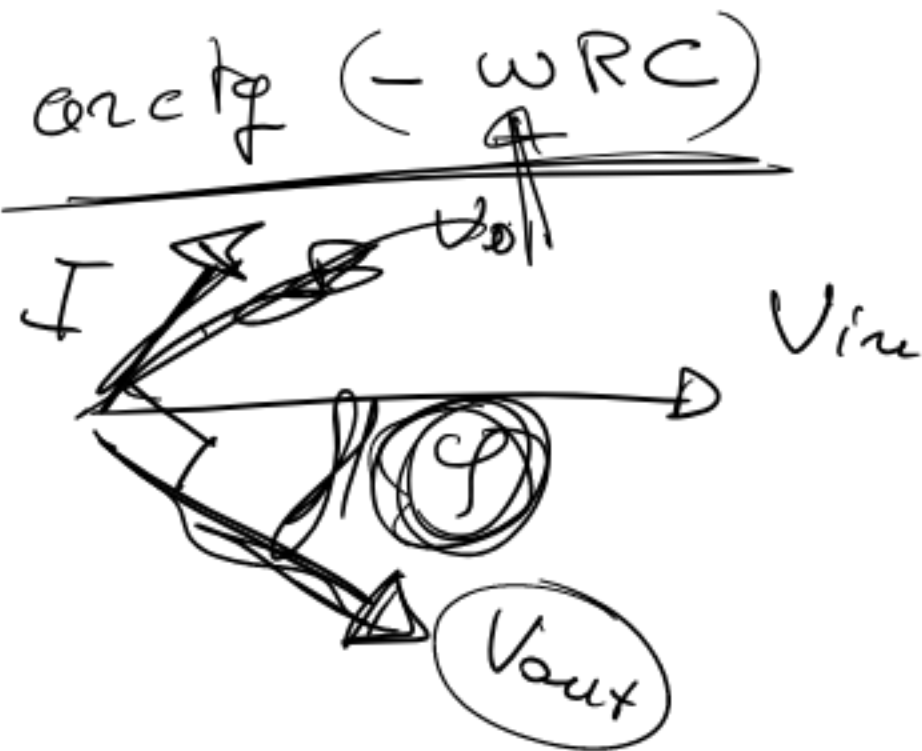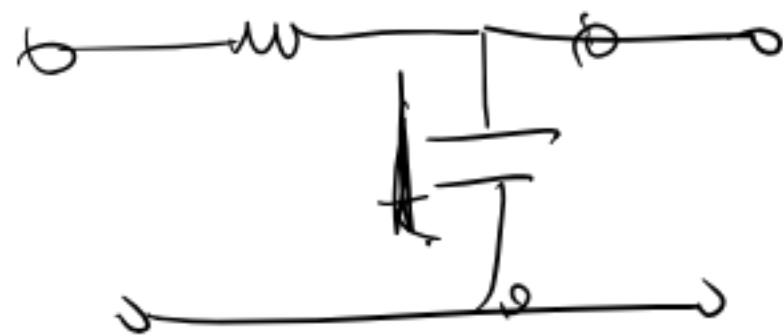
$$\phi = \arctg \frac{-R}{X_C} = \arctg(-\omega RC)$$




~~PASSA~~

FILTRO  
PASSA-ALTO

f ≈ 50 Hz  
RETR

FALTA S'INDICARE

# FILTRO CR - PASSA ALTO

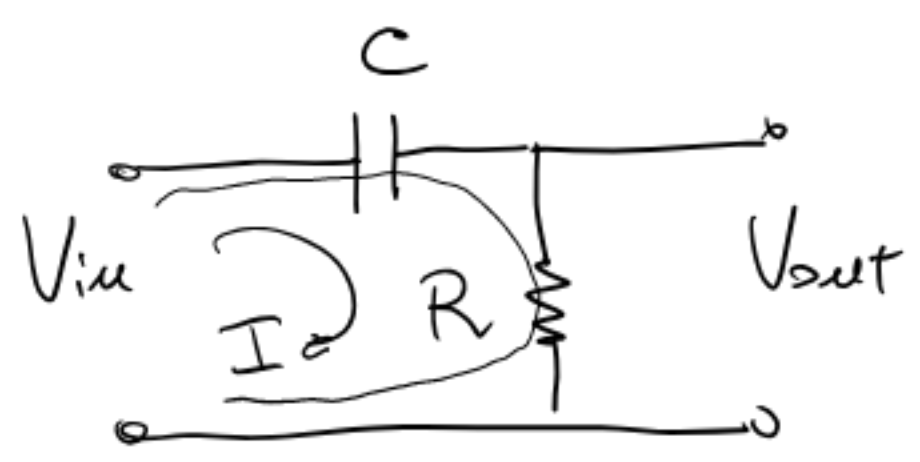

$$T = \frac{V_{out}}{V_{in}} \quad V_{in} \quad R_e$$


$$V_{out} = z_R \cdot I = R \cdot I$$

$$V_{in} = (z_R + z_C) \cdot I \Rightarrow I = \frac{V_{in}}{z_R + z_C}$$

$$T = \frac{V_{out}}{V_{in}} = \frac{R}{z_R + z_C} = \frac{R}{R - jX_C} = \frac{R(R + jX_C)}{R^2 + X_C^2} = R \frac{R + jX_C}{R^2 + X_C^2}$$

$$X_C = \frac{1}{\omega C}$$

$$|T| = \frac{R}{R^2 + X_C^2} \sqrt{R^2 + X_C^2} = \frac{R}{\sqrt{R^2 + X_C^2}} = \frac{1}{\sqrt{1 + \frac{X_C^2}{R^2}}}$$

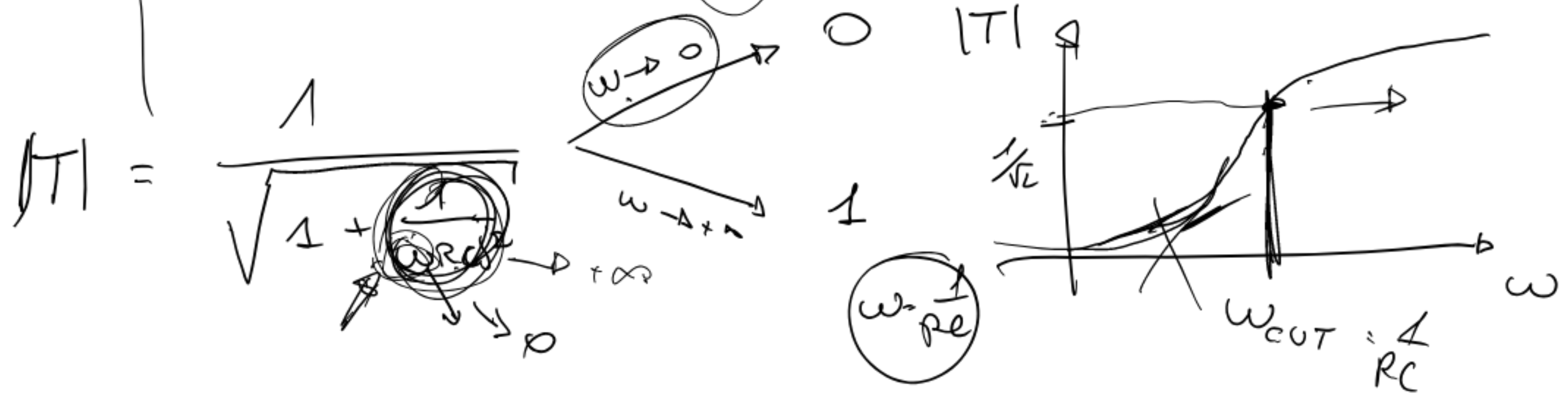


FILTRA PASSA BANDA

$f_{sig} = 1 \text{ kHz}$

$1 \text{ MHz}$


$50 \text{ Hz}$

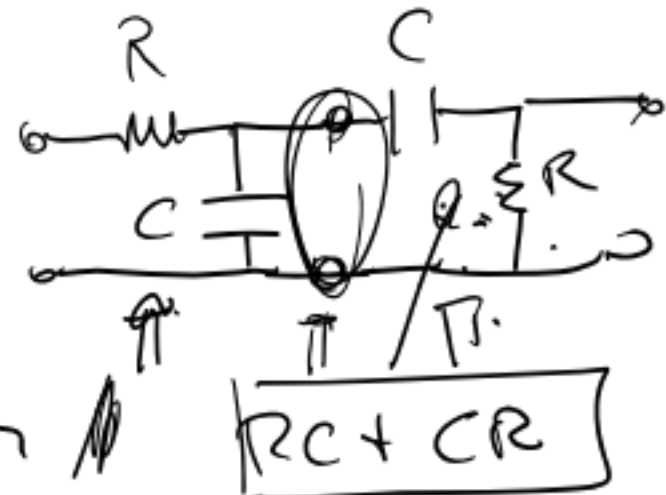

$RC + CR$  or

REL. LOW FREQ


$CR + RC$  ???

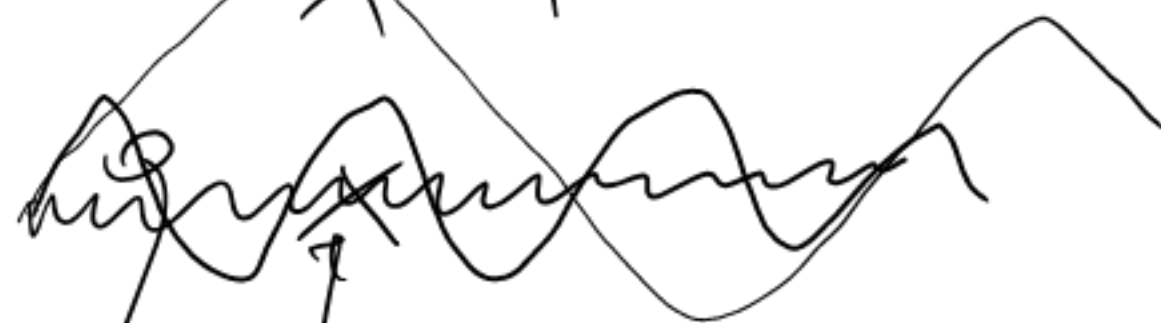


RUMORIE HIGH FREQ

RC

CR

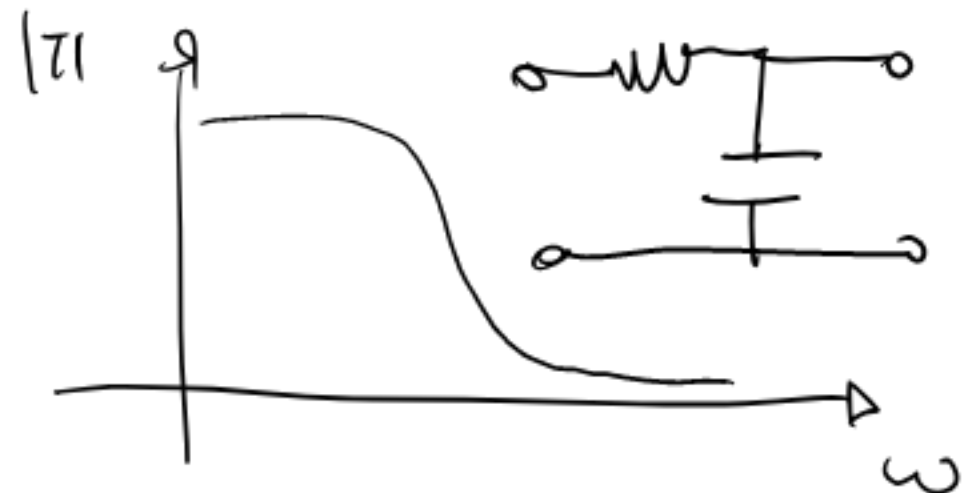




$V_{in}$

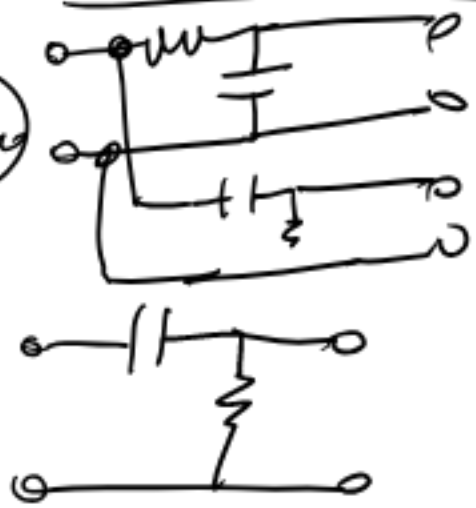

# FILTRO PASSA-BANDA

RC + CR

CR + RC

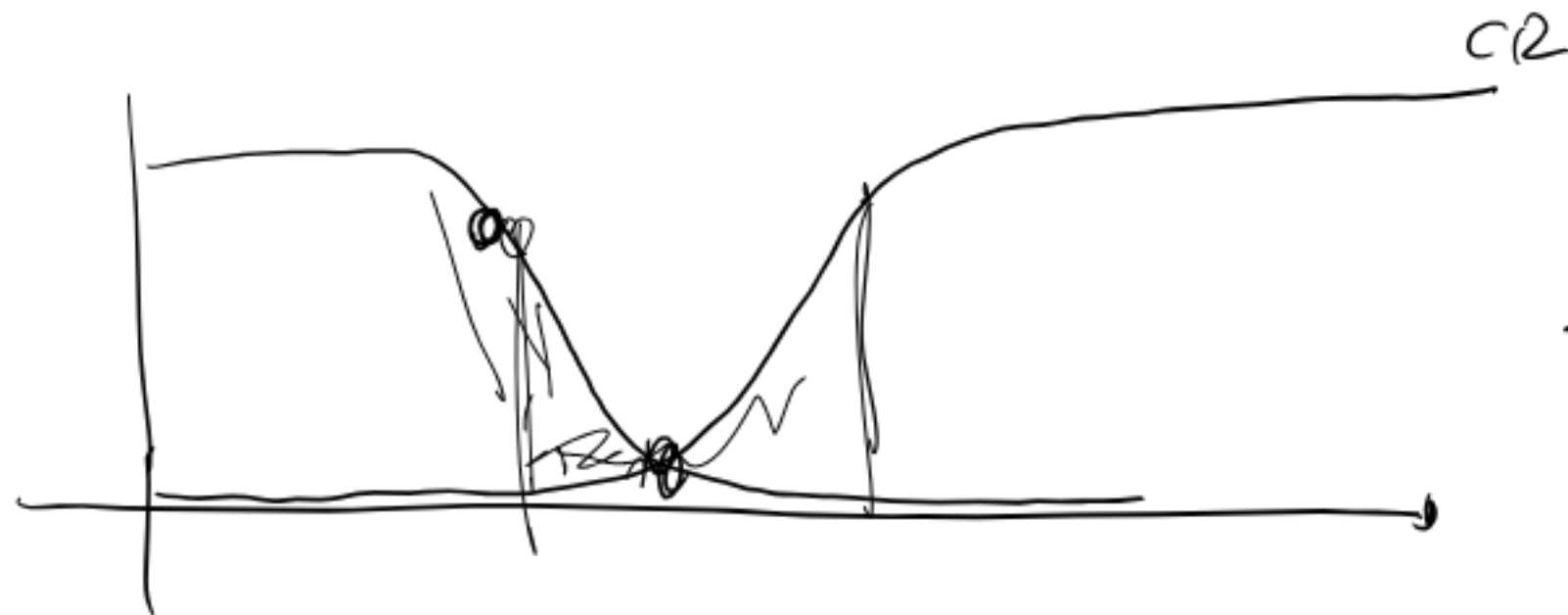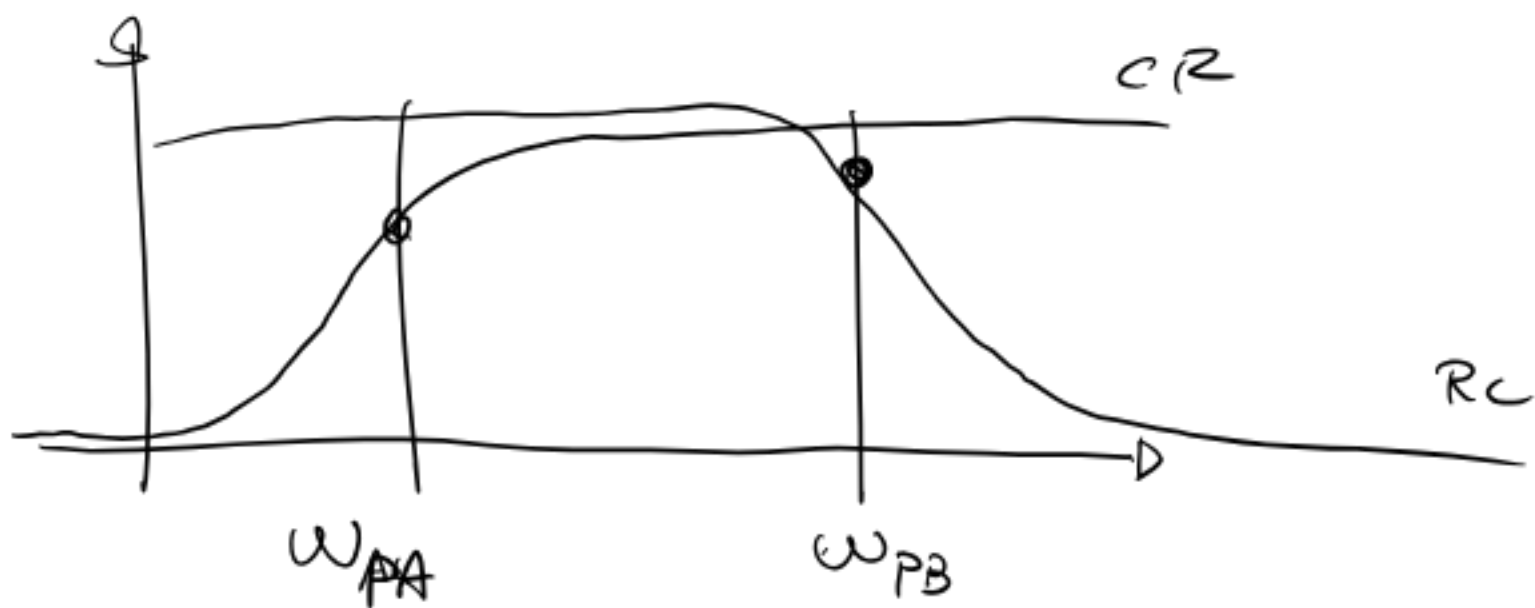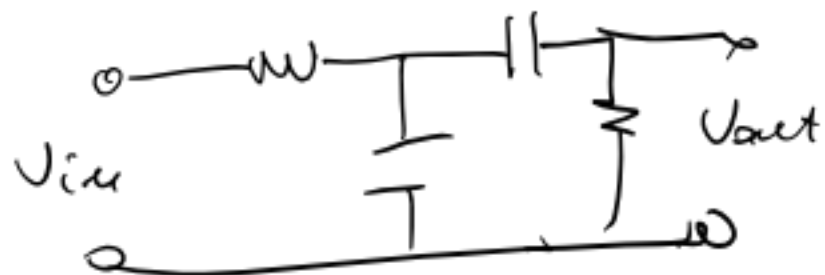

$$T = \frac{R}{R^2 + X_C^2} \frac{R + jX_C R}{R + jX_C R} \quad (7)$$

$$\varphi = \arctan \left( \frac{X_C}{R} \right) - \arctan \left( \frac{X_C}{R} \right)$$

$V_{out} / V_{in}$   
 $I$   
 $V_{in}$



$$\frac{1}{Z_{eq}} = \frac{1}{Z_R} + \frac{1}{Z_C}$$

$$\omega_{PB} > \omega_{PA}$$

CR

∩



$$X_L = \omega L$$

$$X_C = \frac{1}{\omega C}$$

~~$$\omega_{PB} < \omega_{PA}$$~~

FILTRO PARTITORE COMPENSATO

# OSCILLOSCOPIO

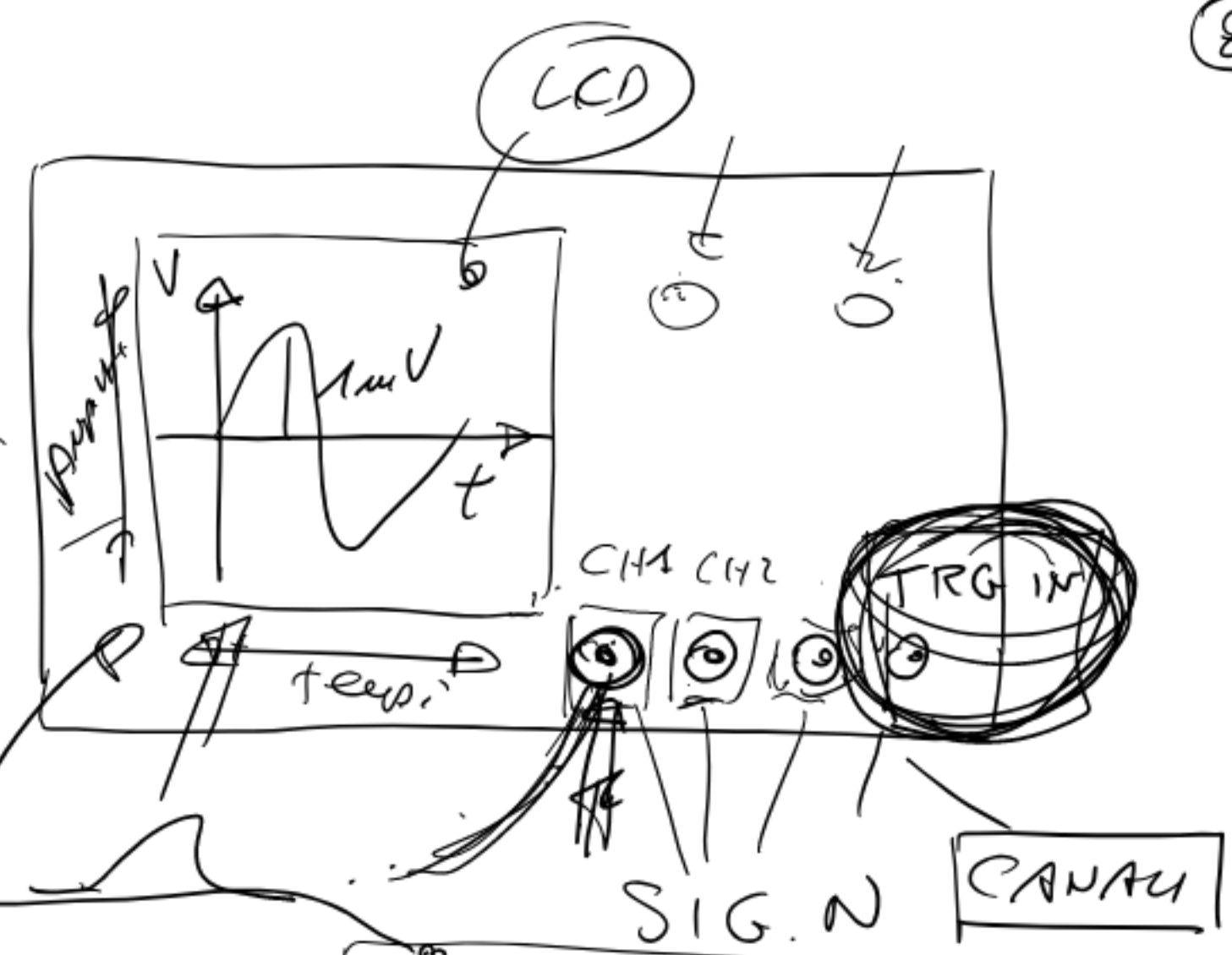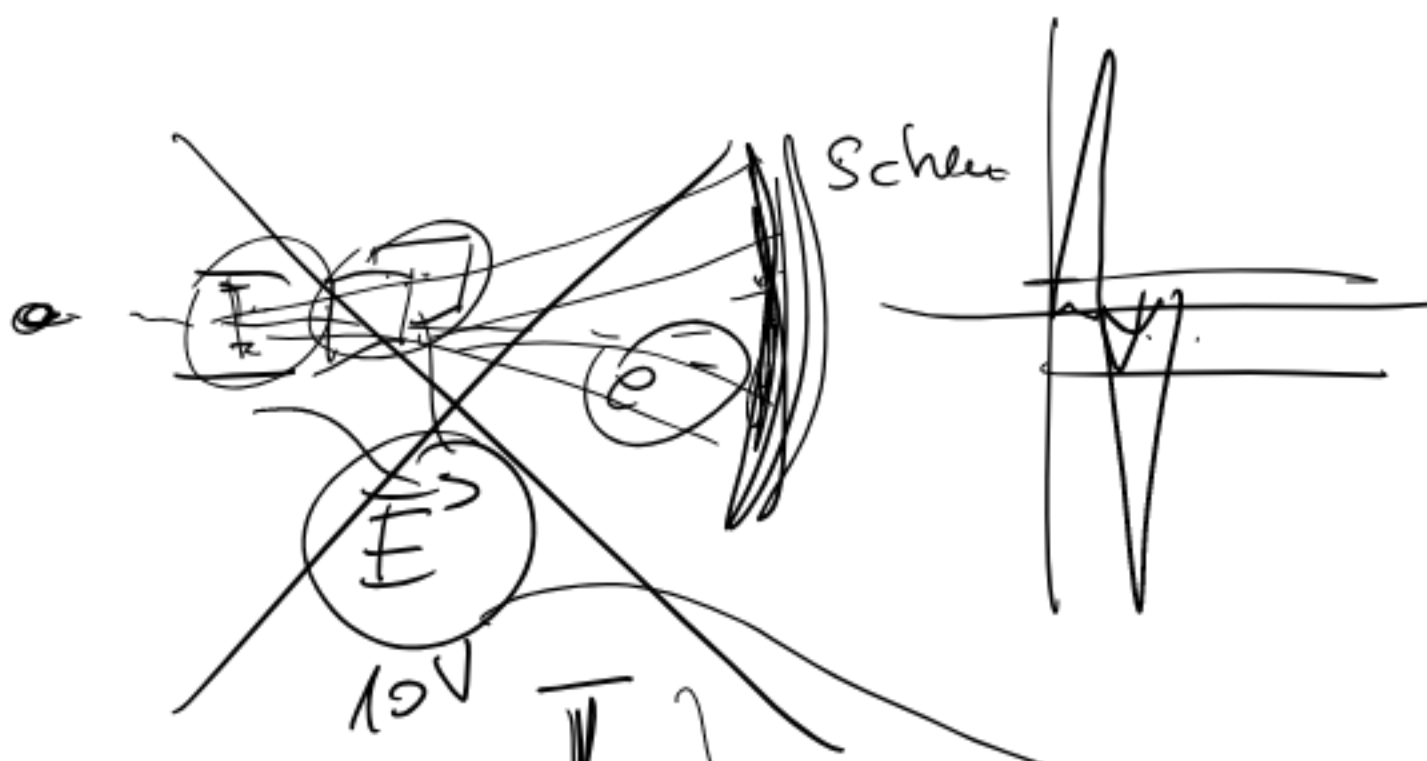

BAND  
 8 BIT  
 10  
 12 ←  
 14



CH1 VS. CH2

25 GS/S

$$\frac{1}{25} \mu s = 0,04 \mu s = 40 ps$$

TRIGGER



TRIGGER

~~TRIG~~  
CONDIZIONE FA PARTIRE L'ACQ.

