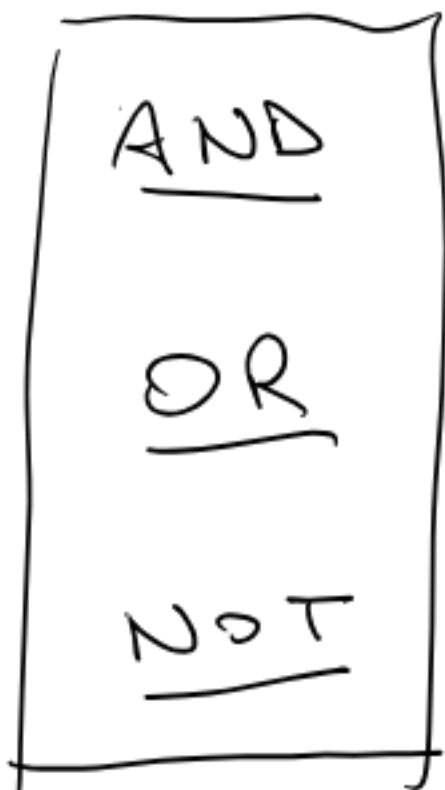


ALGEBRA BOOLEA

A, B, C



$A \cdot B = 1 \iff A = 1 \text{ e } B = 1$

$A + B = 1$ se almeno A o $B = 1$

\bar{A} inverte lo stato delle variabile.

A	B	AND A · B	OR A + B
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	1

A	\bar{A}
0	1
1	0

2^2 combinazioni

2^{NVAR}


TEOREMA DI DE MORGAN

$$1) \overline{A+B} = \bar{A} \cdot \bar{B}$$


$$2) \overline{A \cdot B} = \bar{A} + \bar{B}$$

SIGNIFICATO
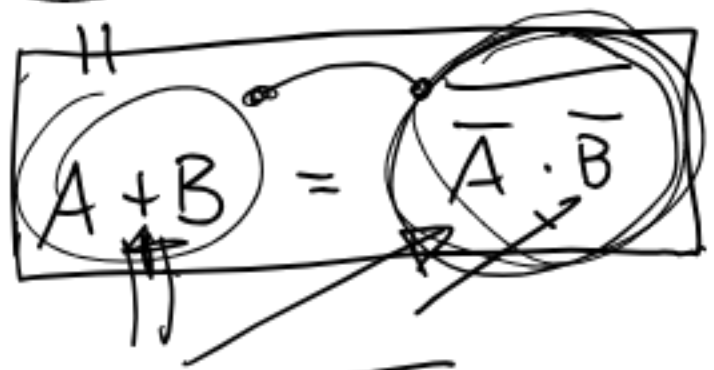
$$1) \overline{A+B} = \bar{A} \cdot \bar{B}$$


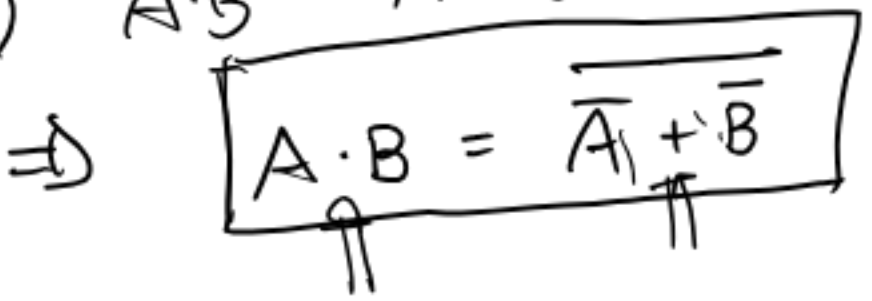
$$2) \overline{A \cdot B} = \bar{A} + \bar{B}$$



$$F = A \oplus (B \cdot C) \oplus D$$

OR *come combinatorie*
AND e NOT

AND *combinazione*
OR e NOT

AND e NOT

oppure
PORTA UNIVERSALI

OR e NOT

T. DE MORGAN

$$\overline{A+B+C+\dots+F} = \bar{A} \cdot \bar{B} \cdot \bar{C} \cdot \dots \cdot \bar{F}$$

$$\overline{A \cdot B \cdot C \cdot \dots \cdot F} = \bar{A} + \bar{B} + \bar{C} + \dots + \bar{F}$$

$A+B = \bar{A} \cdot \bar{B}$

$\overline{A \cdot B} = \bar{A} + \bar{B}$

	A	B	$A+B$	$\bar{A} \cdot \bar{B}$
→	0	0	1	1
↗	0	1	0	0
↘	1	0	0	0
↖	1	1	0	0

$\overline{A+B} = \bar{A} \cdot \bar{B}$


$X \cdot X = 0$

$X = \bar{A} \cdot \bar{B}$





$\bar{X} = \overline{\bar{A} \cdot \bar{B}}$

$$\bar{A} \cdot \bar{B} \cdot (\overline{\bar{A} + \bar{B}}) = \bar{A} \bar{B} (A+B) = \bar{A} \bar{B} A + \bar{A} \bar{B} B = 0 + 0 = 0$$

PORTE LOGICHE

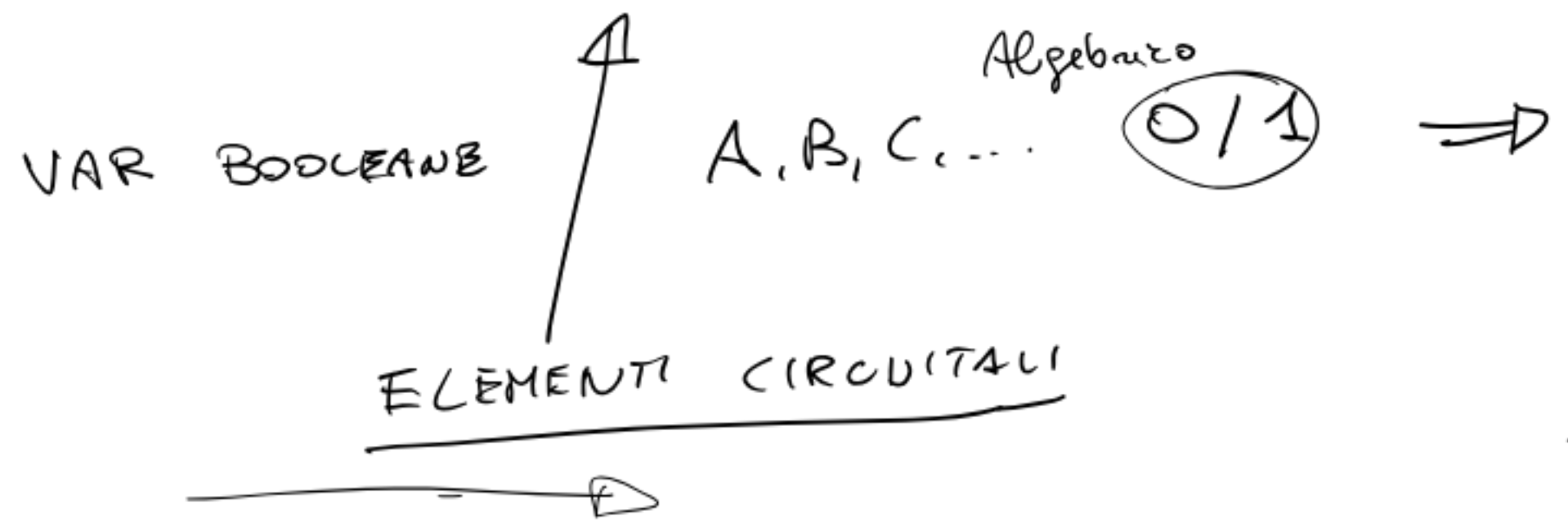


AND

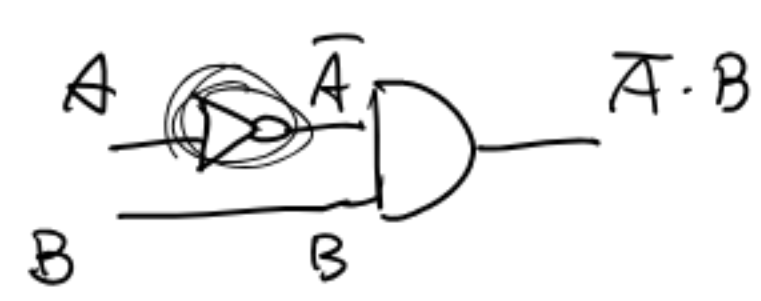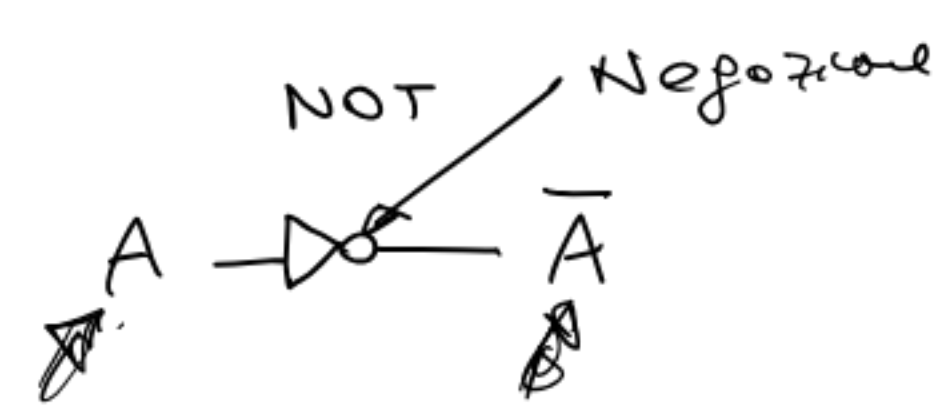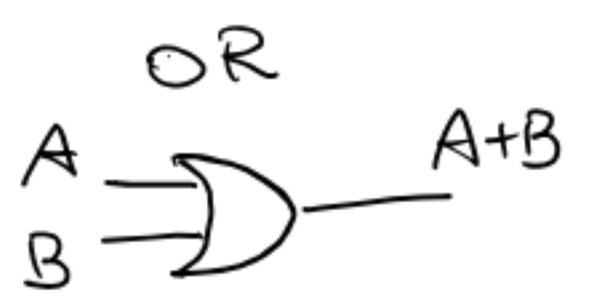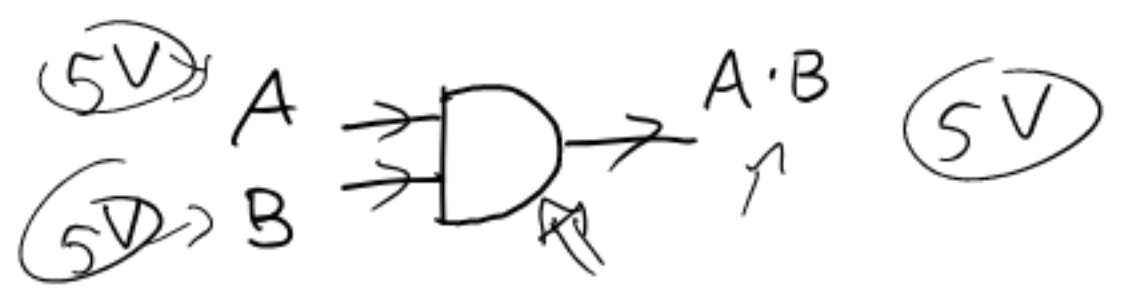

IDENTITA'

TTL

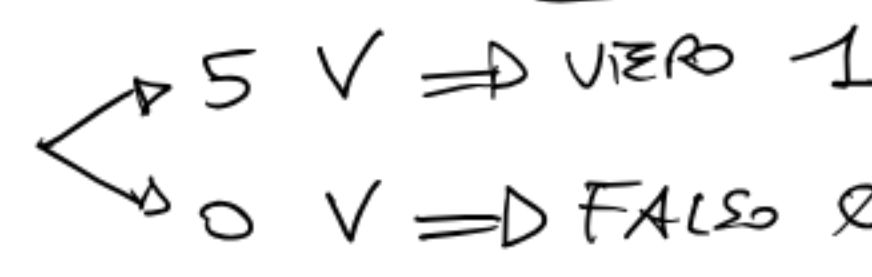

0,12 V

NIM

0, -800 mV

0,24 V



(TTL)

→ 0,3.3 V



PORTE UNIVERSALI

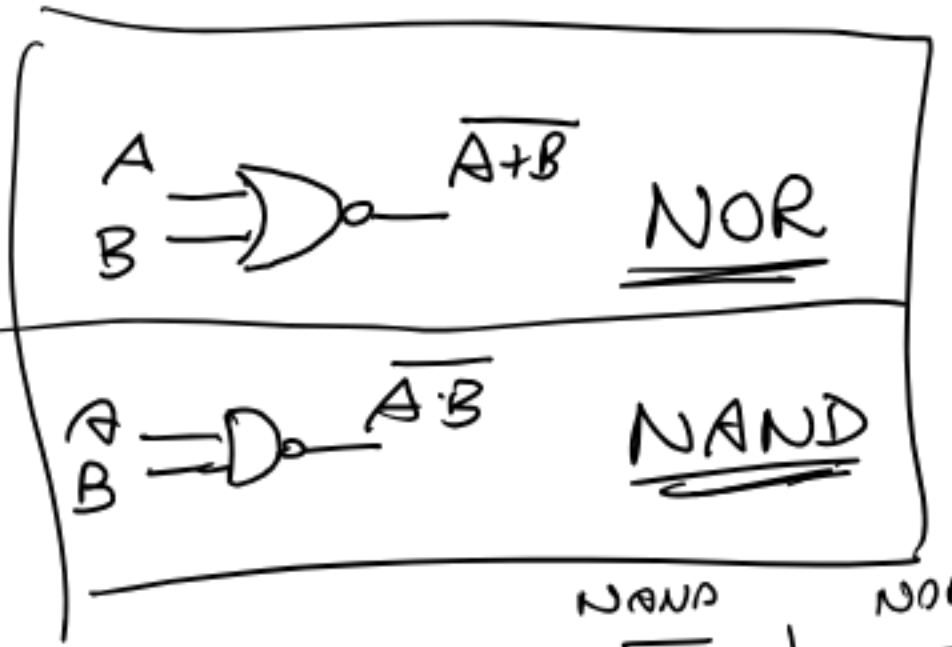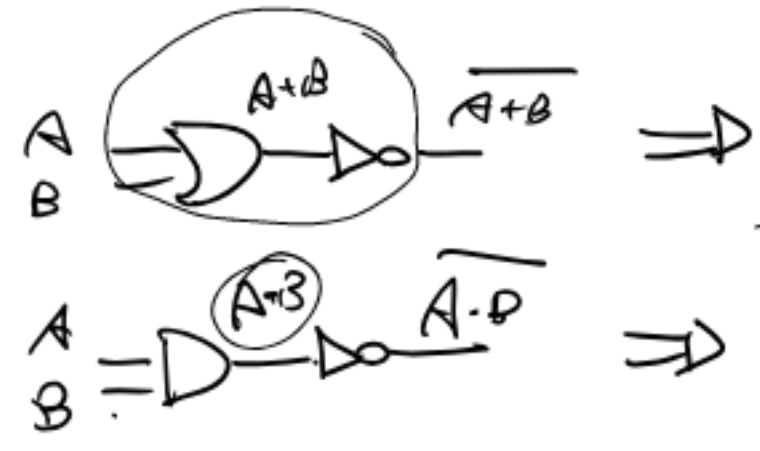
$\overline{A+B} = \bar{A} \cdot \bar{B}$
 $\overline{A \cdot B} = \bar{A} + \bar{B}$



$\overline{\overline{A+B}} = \overline{\bar{A} \cdot \bar{B}}$





$A+B = \overline{\bar{A} \cdot \bar{B}}$


PORTE AND, NOT.

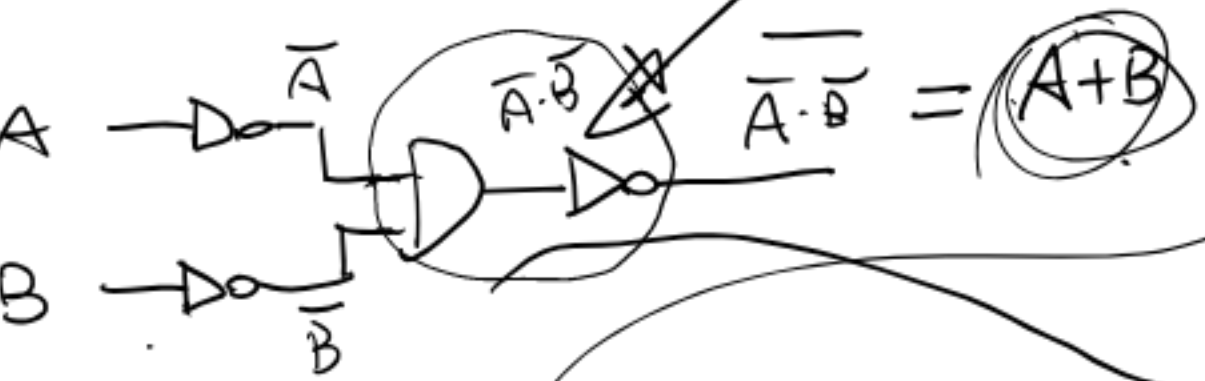



3 PORTE NOT } 1 PORTA OR
1 PORTA AND }

A	B	NAND $\overline{A \cdot B}$	NOR $\overline{A+B}$
0	0	1	1
0	1	1	0
1	0	1	0
1	1	0	0

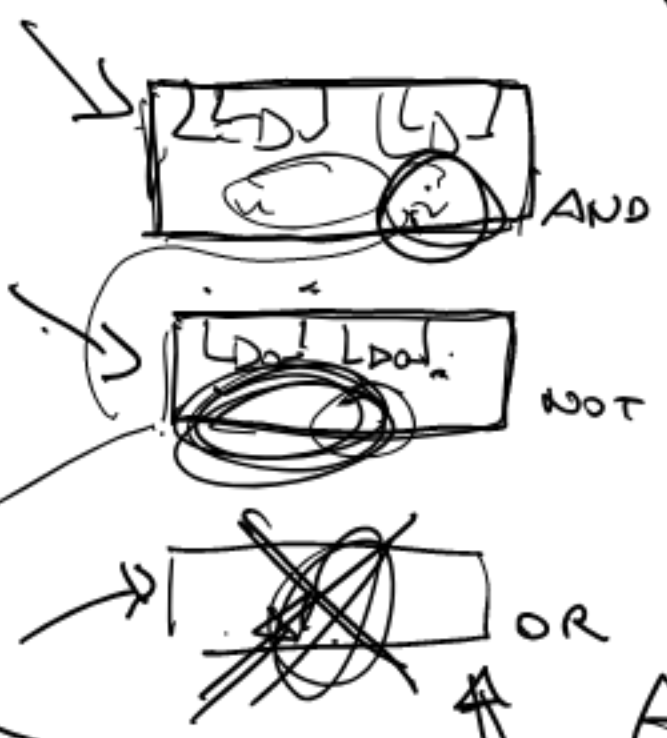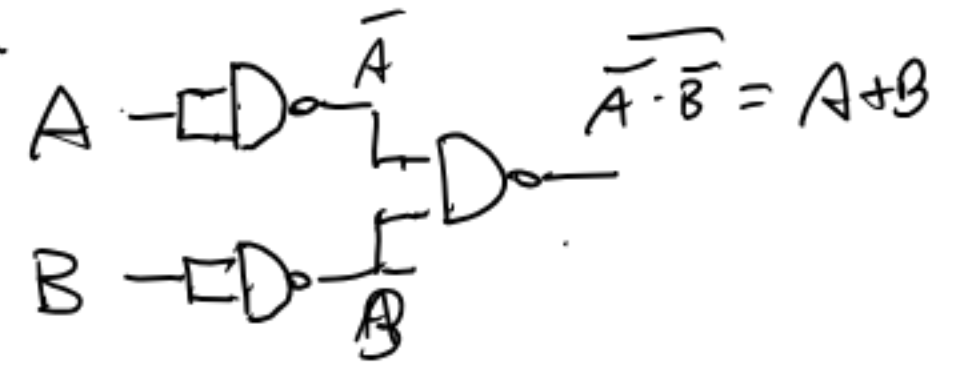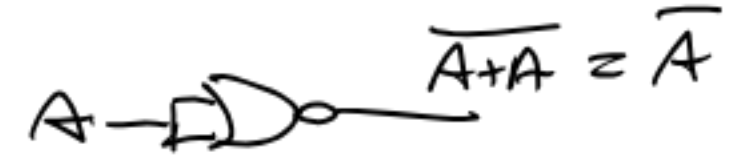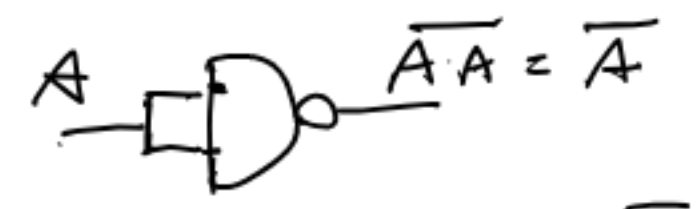

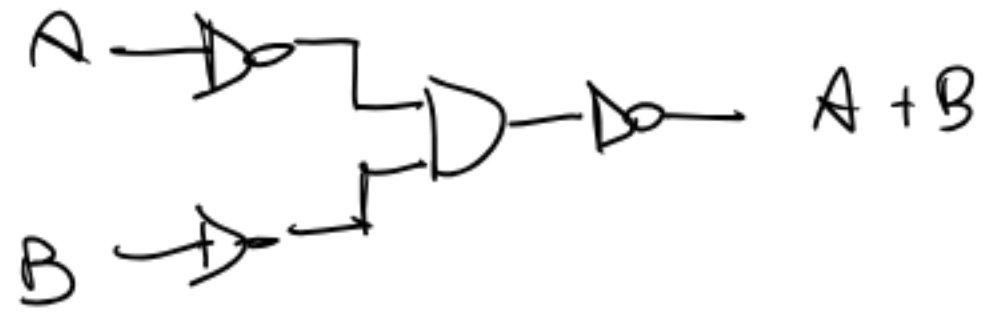

3 NOT } ⇒ 2 C.F.
 1 AND }

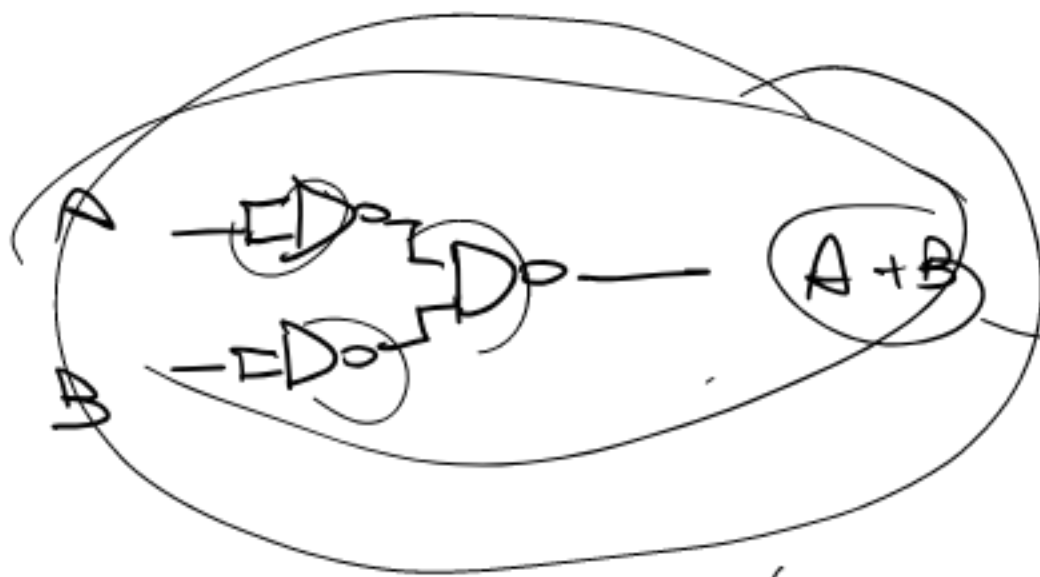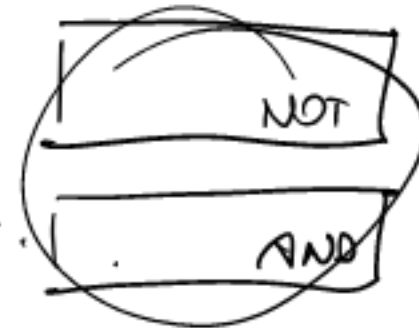

→ 3 NAND



FPGA



OP. LOG. BASR

AND \Rightarrow 


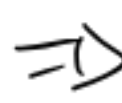
OR \Rightarrow 


NOT \Rightarrow 

T. De Morgan. AND, NOT / OR, NOT

(7)

PORTE UNIVERSALI

NAND $\begin{matrix} A \\ B \end{matrix} \Rightarrow$  $\overline{A \cdot B} \Rightarrow$  $\overline{A=B}$

NOR $\begin{matrix} A \\ B \end{matrix} \Rightarrow$  $\overline{A+B}$


NOT $\overline{A=B}$

Val 1 se solo una delle due vari è vera

XOR (EXCLUSIVE OR)

XNOR

$A \oplus B$
 $\begin{matrix} A \\ B \end{matrix} \Rightarrow$  $A \oplus B$

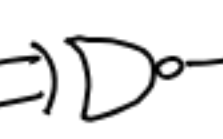$\overline{A \oplus B}$
 $\begin{matrix} A \\ B \end{matrix} \Rightarrow$  $\overline{A \oplus B}$

A	B	$A \oplus B$	$\overline{A \oplus B}$
→ 0	0	0	1
→ 0	1	1	0
→ 1	0	1	0
→ 1	1	0	1


~~XOR~~ = AND, OR, NOT ?

SI ! SI RIESCE

COME ???

ES1) $A + B = \overline{\overline{A} \cdot \overline{B}}$

$F = \overline{\overline{A} \cdot \overline{B}}$

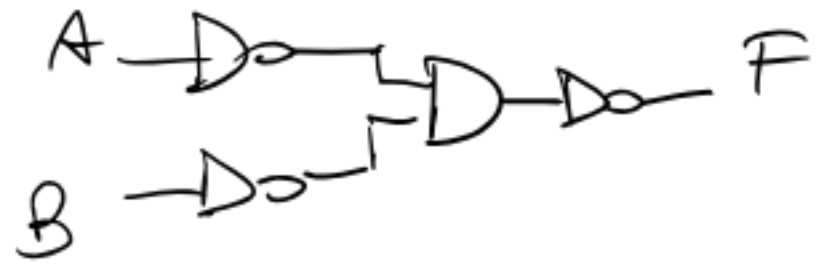


ES2) XOR

A	B	$A \oplus B = F$
0	0	0
0	1	1
1	0	1
1	1	0




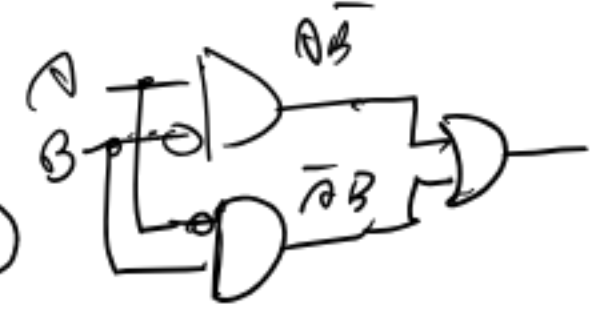$F = A\overline{B} + \overline{A}B$
 $= (A+B) \cdot (\overline{A+B})$



DIK

A	B	C	$F(A,B,C)$
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1

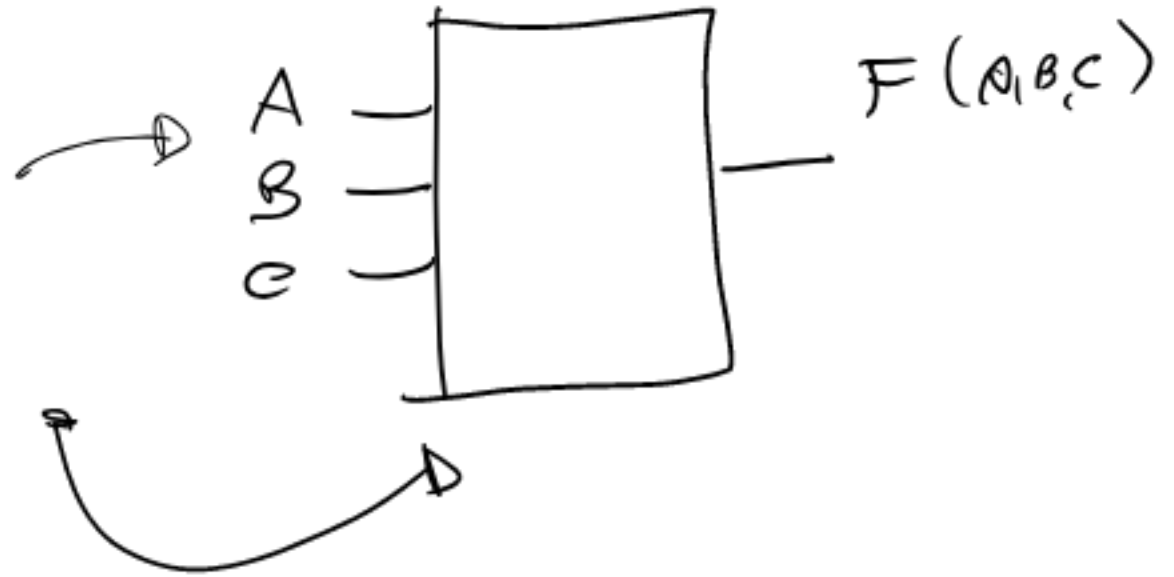

1) Rapp. algebrica $F(A, B, C, \dots)$ \rightarrow Disegnare circuito SCHEMA \rightarrow SIM \rightarrow Ver. TAU. VER

2) F TAU VERITA \rightarrow Rapp. algebrica
SUI LUOGO IN MINTERM O MAXTERM

(A)	(B)	minterm (m)	maxterm (M)	$m_1 = \bar{A} \cdot \bar{B}$	m_2	m_3	m_4	(F)	F
0	0	$\bar{A} \cdot \bar{B} = m_1$	$A+B = M_1$	1	0	0	0	0	F_1
0	1	$\bar{A} \cdot B = m_2$	$A+\bar{B} = M_2$	0	1	0	0	1	F_2
1	0	$A \cdot \bar{B} = m_3$	$\bar{A}+B = M_3$	0	0	1	0	1	F_3
1	1	$A \cdot B = m_4$	$\bar{A}+\bar{B} = M_4$	0	0	0	1	0	F_4

\uparrow

AND fra A e B
 off. 0 neg.
 = 1

\uparrow

OR fra A e B
 off. 0 neg.
 = 0

$$F = \sum_{i=1}^4 m_i \cdot (F_i) = \prod_{i=1}^4 (M_i + F_i)$$

\uparrow Successive OR
 \uparrow TAU VER
 \uparrow Successive AND
 \uparrow AND
 \uparrow OR

SUM OF PRODUCTS / MINITERM / MAXTERM

A	B	m	M	F	F
0	0	$\bar{A}\bar{B} = m_1$	$A+B = M_1$	F_1	0
0	1	$\bar{A}B = m_2$	$A+\bar{B} = M_2$	F_2	1
1	0	$A\bar{B} = m_3$	$\bar{A}+B = M_3$	F_3	1
1	1	$AB = m_4$	$\bar{A}+\bar{B} = M_4$	F_4	0

$$F = \sum_{i=1}^4 F_i \cdot m_i = \prod_{i=1}^4 F_i + M_i$$

$$F = F_1 m_1 + F_2 m_2 + F_3 m_3 + F_4 m_4$$

$$= \underbrace{F_1}_{1} \bar{A}\bar{B} + \underbrace{F_2}_{0} \bar{A}B + \underbrace{F_3}_{1} A\bar{B} + \underbrace{F_4}_{0} AB$$

$F_2 = 0 \implies 0 \cdot \bar{A}B$

$F_1 = 1$

$$1 \cdot \bar{A}\bar{B} = \bar{A}\bar{B} = m_1$$

$F_i \neq 0$

$$= \sum_{i=1}^4 m_i$$

$(F_i = 1)$

$$= \prod_{i=1}^4 M_i$$

$F_i = 0$

$$F = \bar{A}\bar{B} + A\bar{B}$$

$$= (A+B)(\bar{A}+\bar{B})$$

$$= \bar{A}\bar{B} + A\bar{B} + B\bar{A} + B\bar{B}$$

$$= \bar{A}\bar{B} + A\bar{B}$$

$$F = (\cancel{F_1 + M_1}) \cdot (\cancel{F_2 + M_2}) \dots$$

$M_2 = A+B$

SUMME Minterm / Minterm


$$F = \sum_{i=1}^{2^{nVAR}} m_i = \prod_{i=1}^{2^{nVAR}} M_i$$

$F_i = 1$ $F_i = 0$

A	B	C	
0	0	0	$\bar{A}\bar{B}\bar{C}$
0	0	1	$\bar{A}\bar{B}C$
0	1	1	$\bar{A}BC$
			⋮

A	B	F	m
0	0	0	$\bar{A}\bar{B}$
0	1	1	$\bar{A}B$
1	0	1	$A\bar{B}$
1	1	0	AB


$F = \bar{A}B + A\bar{B}$

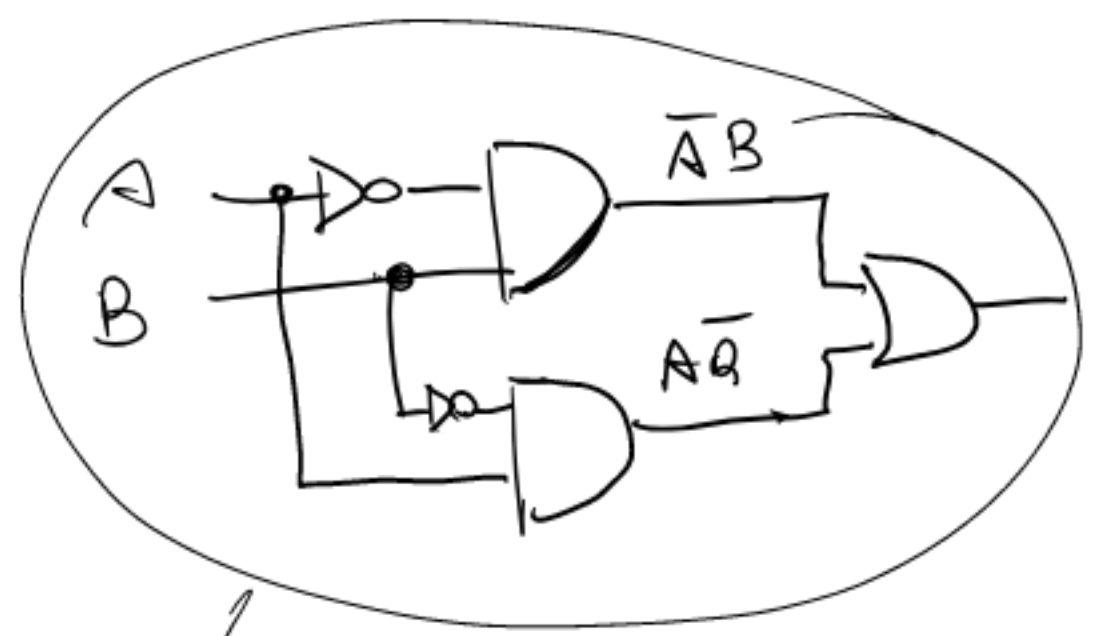

$F = A \oplus B$

NAND / NOR ?
AND ↔ OR ?

MUX (MULTI PLEXER)

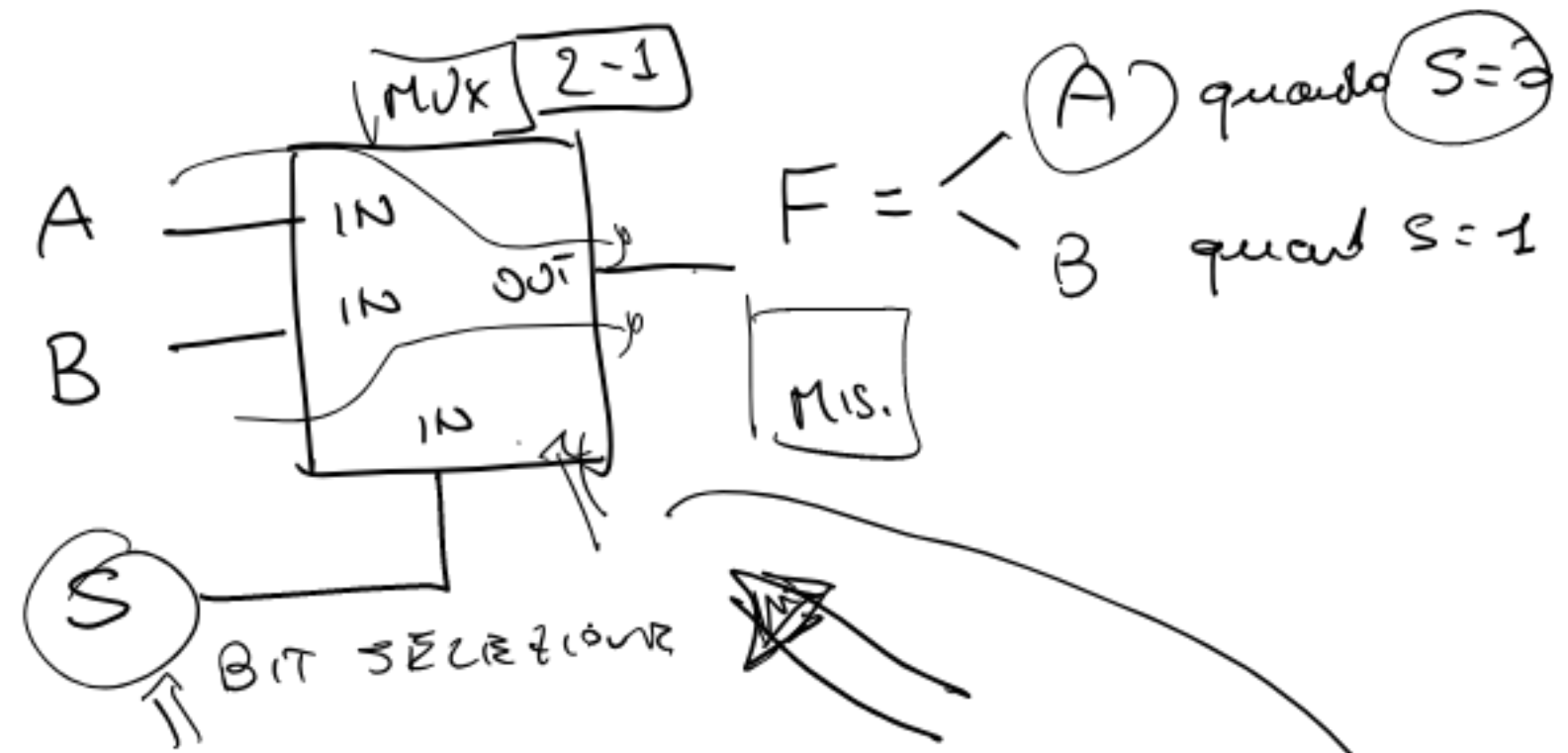

S	A	B	F	
0	0	0	0	
0	0	1	0	
0	1	0	1	$\bar{S}A\bar{B}$
0	1	1	1	$\bar{S}AB$
1	0	0	0	
1	0	1	1	$S\bar{A}B$
1	1	0	0	
1	1	1	1	SAB

$$F = \bar{S}A\bar{B} + \bar{S}AB + S\bar{A}B + SAB$$

$$= \bar{S}A(\bar{B} + B) + SB(\bar{A} + A)$$

$$F = \bar{S}A + SB$$

MUX

