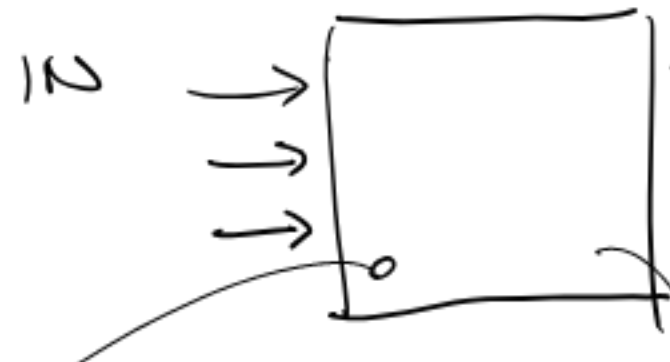


CIRCUITO DIGITALI




Repp. algebra F

$F = A \cdot B + C$



Descritto TAU. VER.

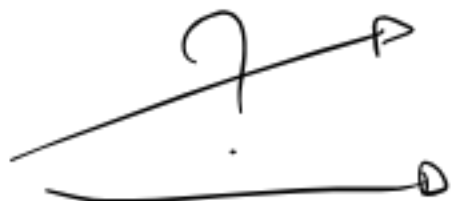

Svilup. minterm maxterm → Repp. Alg. → CIRCUITO SIM


A	B	m	M	F
0	0	$\bar{A}\bar{B}$	$A+B$	F_1
0	1	$\bar{A}B$	$A+\bar{B}$	F_2
1	0	$A\bar{B}$	$\bar{A}+B$	F_3
1	1	AB	$\bar{A}+\bar{B}$	F_4
		\uparrow m_i	\uparrow M_i	\uparrow

$F = \sum_{i=1}^{2^{NVAR}} m_i \cdot F_i = \prod_{i=1}^{2^{NVAR}} (M_i + F_i)$

$F_i = 1$ $F_i = 0$

$F = \sum_{i=1}^{2^{NVAR}} m_i \quad F_i = 1 = \prod_{i=1}^{2^{NVAR}} M_i \quad F_i = 0$

LOGICA COMBINATORIA

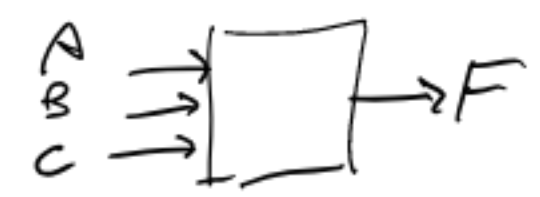


②

1) Lo stato di F è univocamente determinato dalla COMBINAZIONE VAR IN A, B, C, ...

2) NON C'È DIPENDENZA DAL TEMPO

ABILITAZIONE

ENABLE


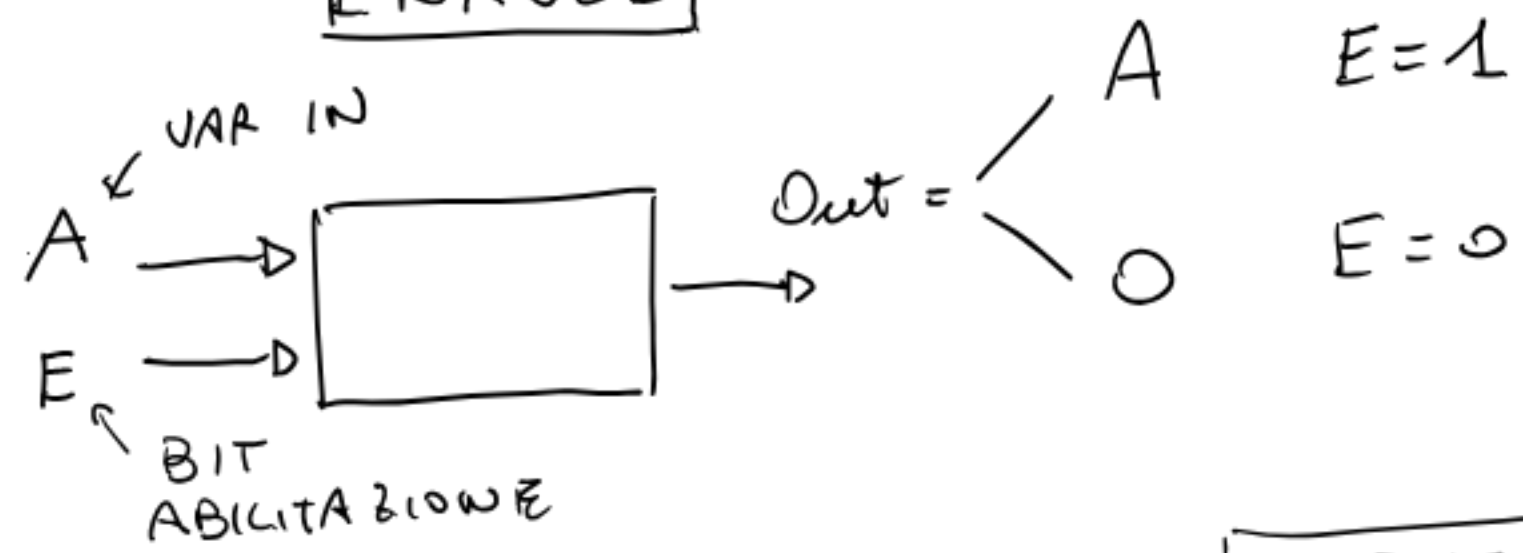


(7) $Out = E \cdot A$




E	A	Out = E · A
0	0	0
0	1	0
1	0	0
1	1	1

0
1
0
0

I · A

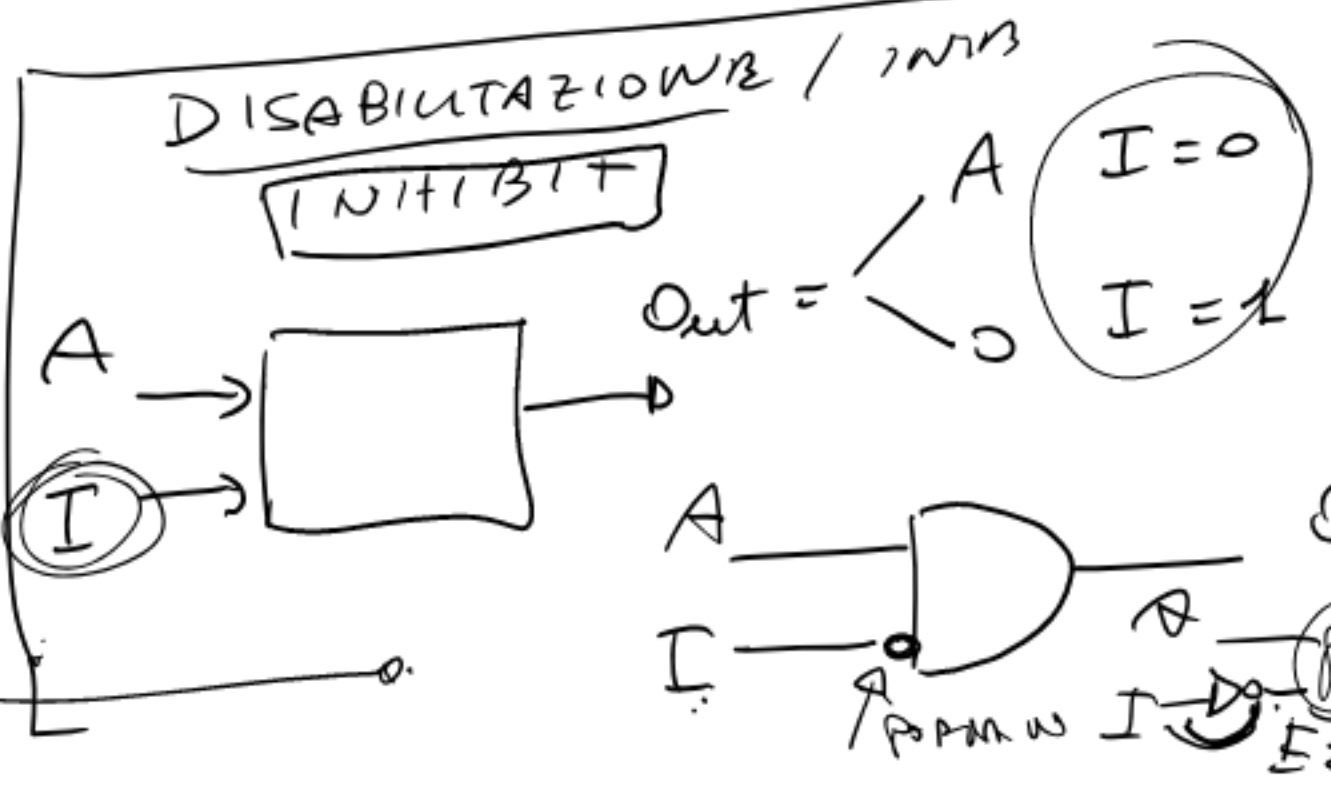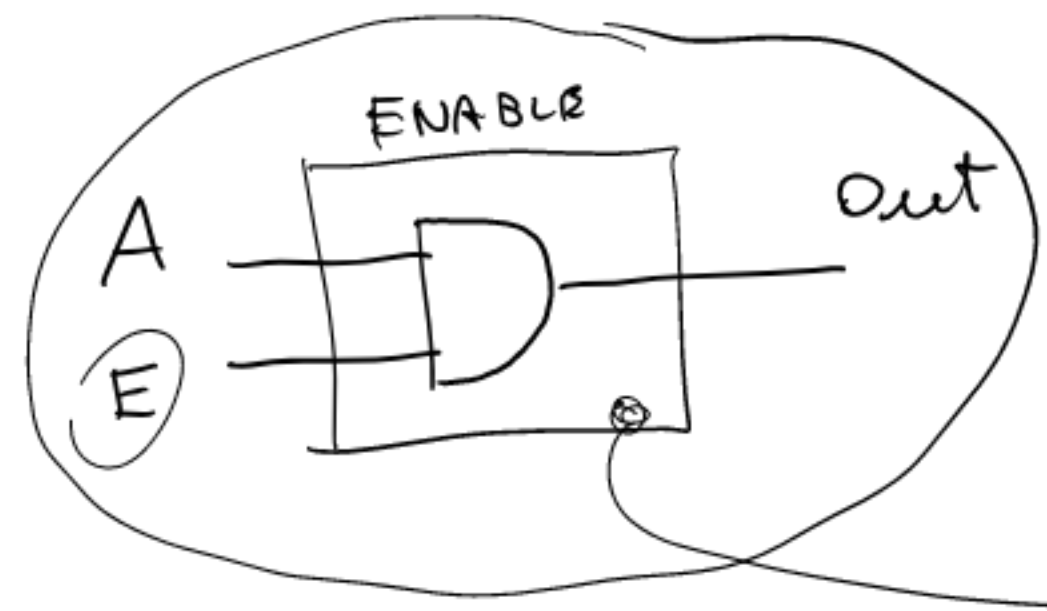


TRUE/FALSE

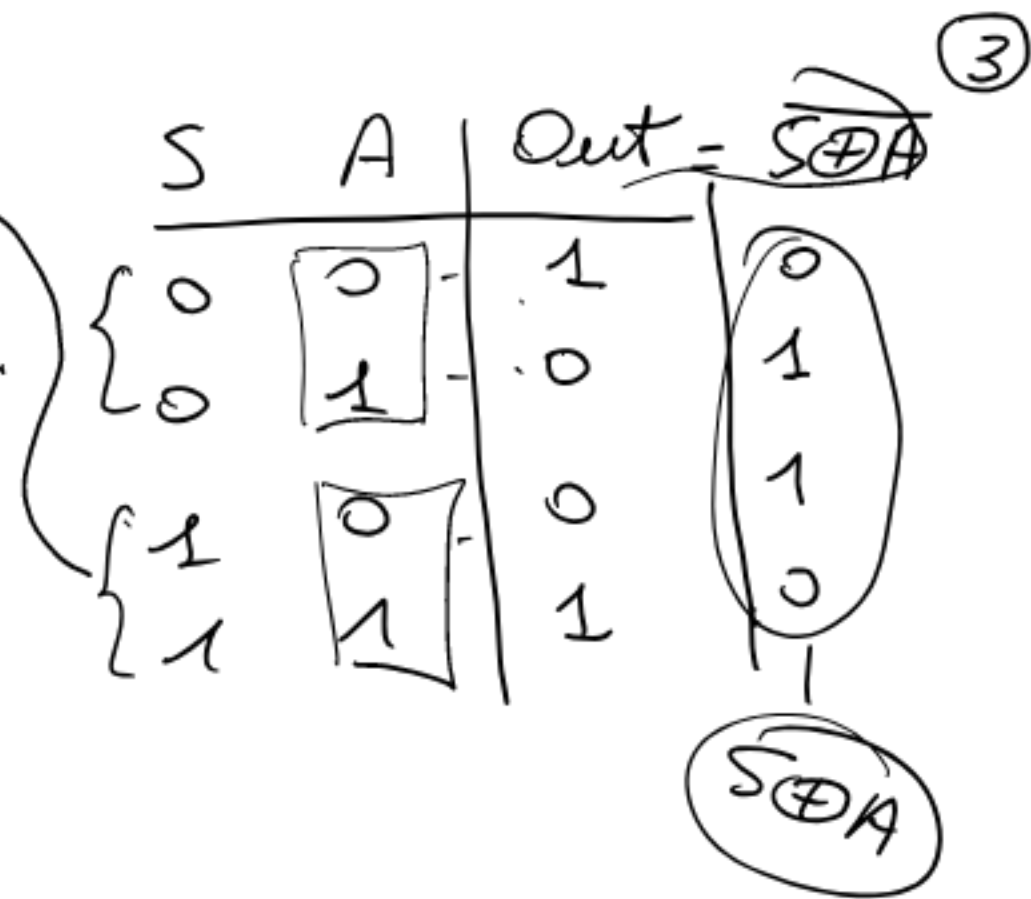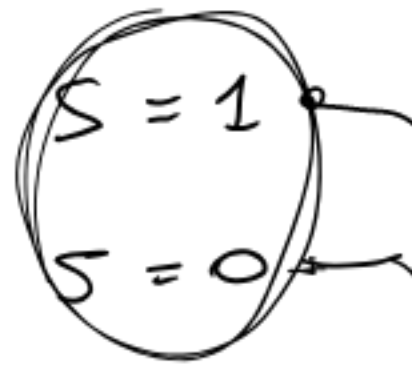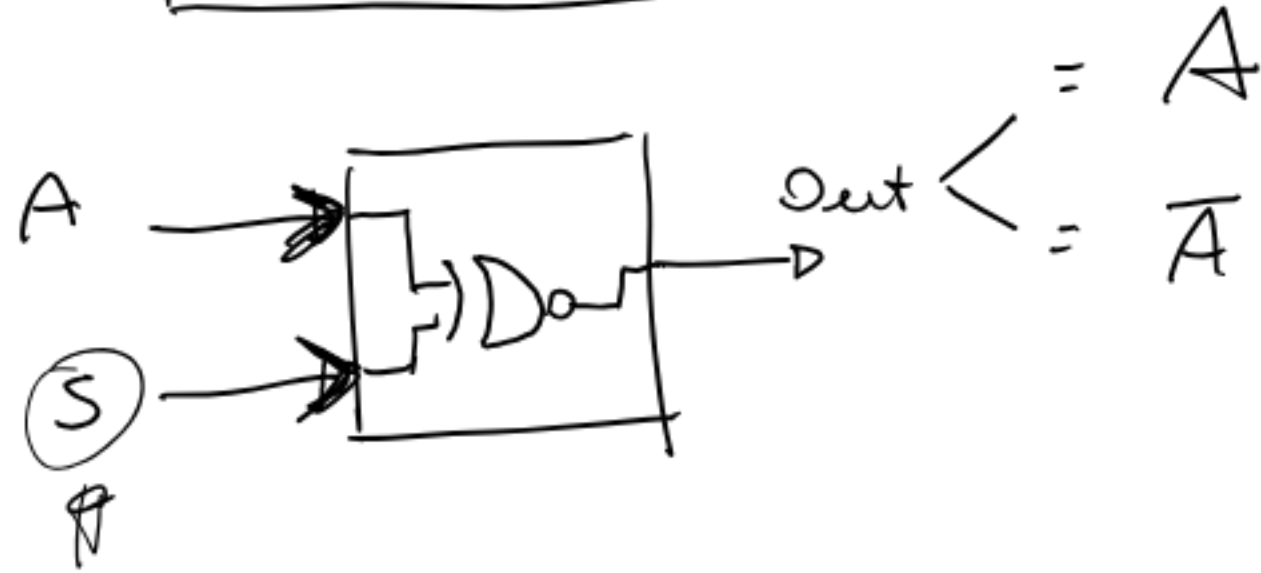

XOR XOR

UGUAGLIANZA

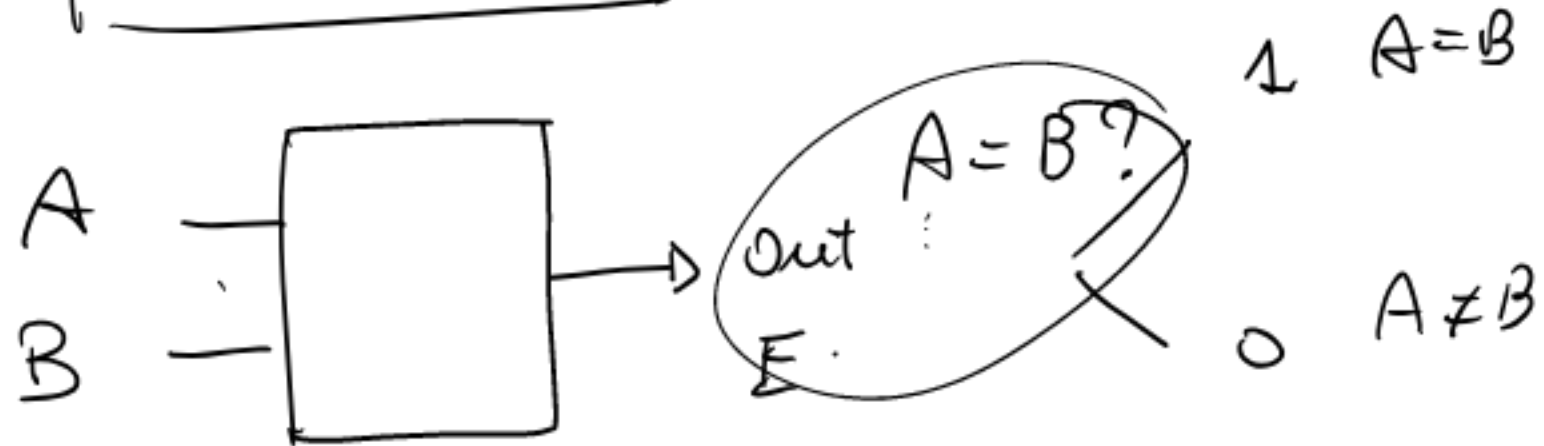

$E = \overline{A \oplus B}$

A	B	E	D
0	0	1	0
0	1	0	1
1	0	0	1
1	1	1	0



$D = A \oplus B$

MUX

4-1 / 8-1 / 16-1 / 32-1




$$\frac{32 + 5}{37 \text{ VAR ROLU37w}}$$

NBITS = 5

$$2^{37}$$

$$2^5 = 32$$


$$2^{NBITS} \geq NVAR$$

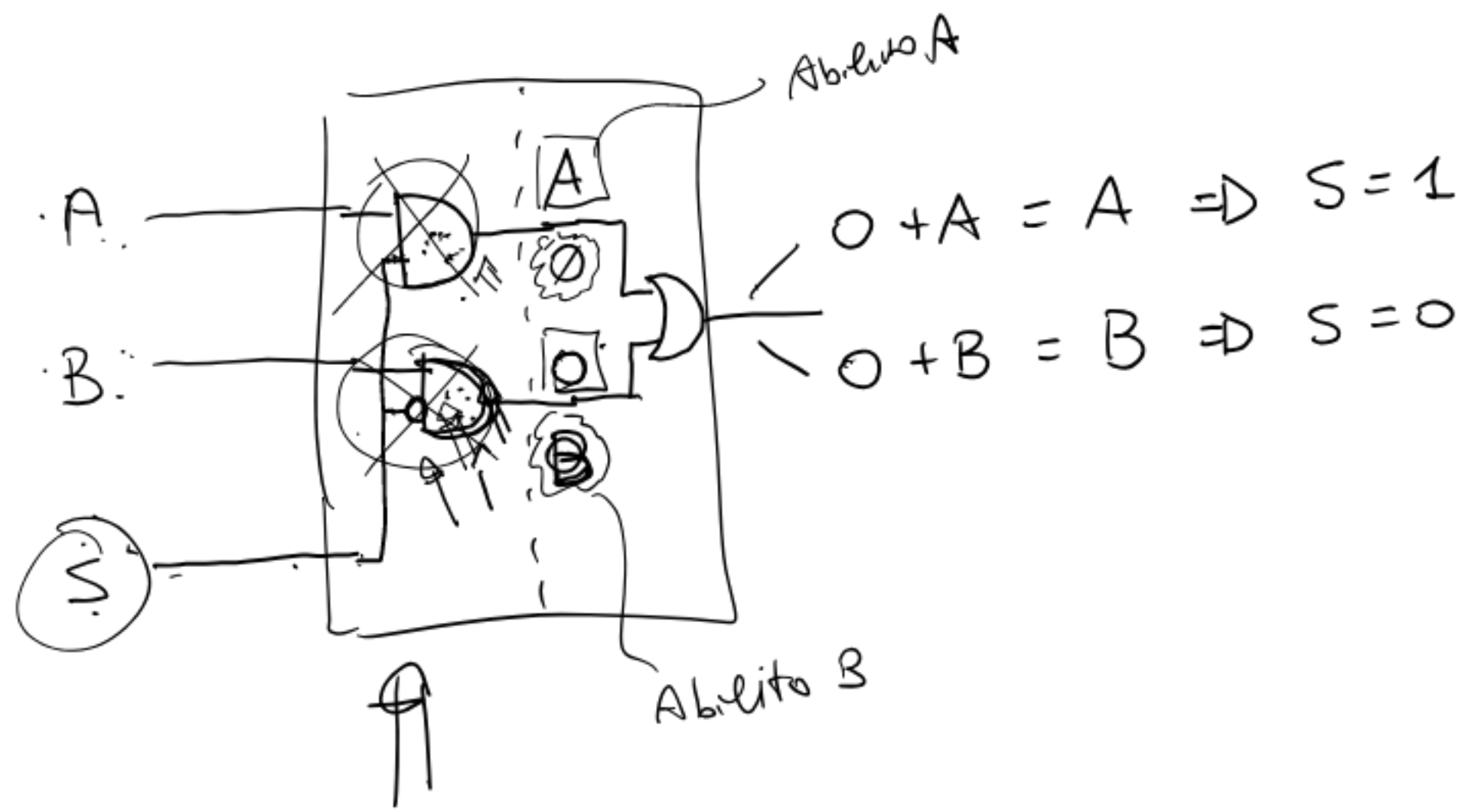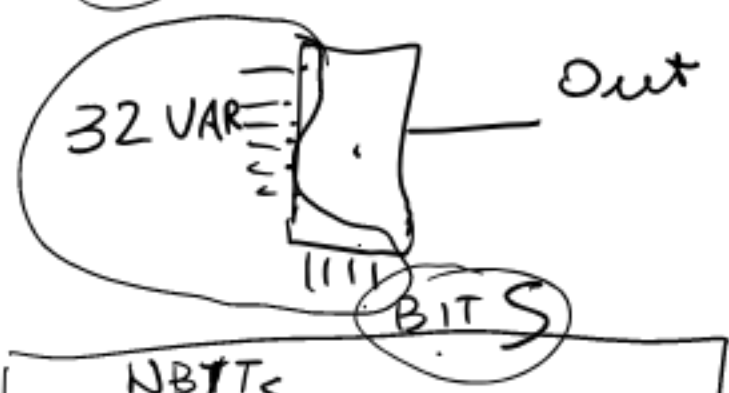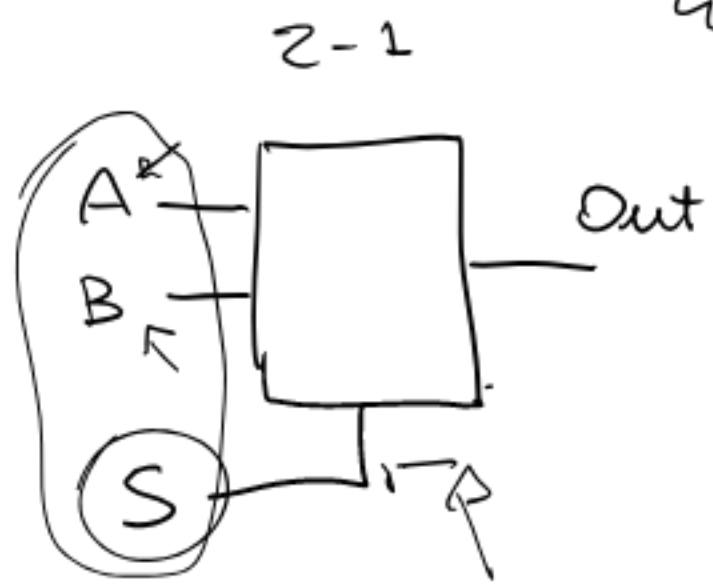

MUX 8-1

3 SELETTORI


$2^3 = 8$

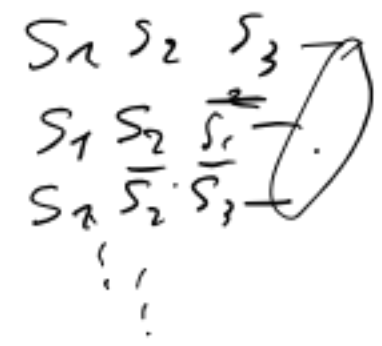

8 VAR + 3 BIT
 11 VAR
 16 VAR

Out 4-1

MUX 4-1

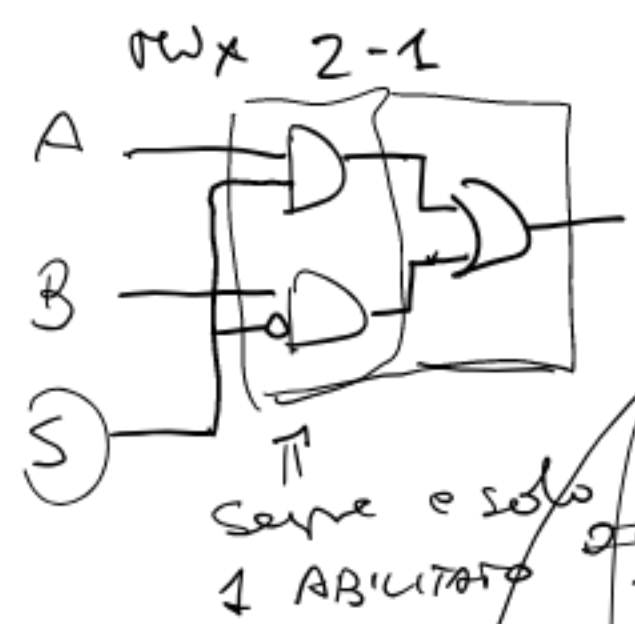





4 VAR

~~1 BIT S~~

2 BITS ?

$2^2 = 4$ combi

AND 3 IN

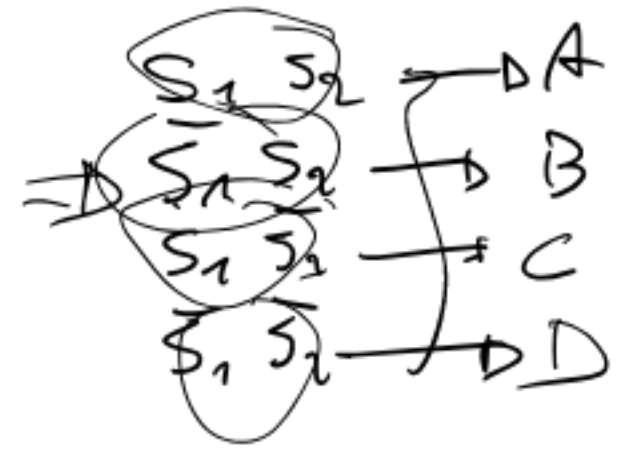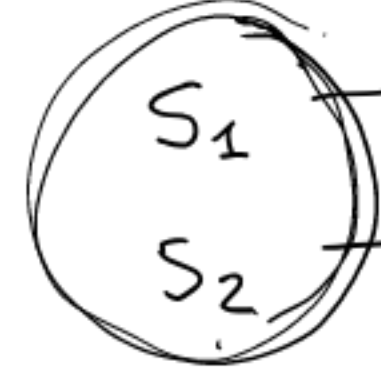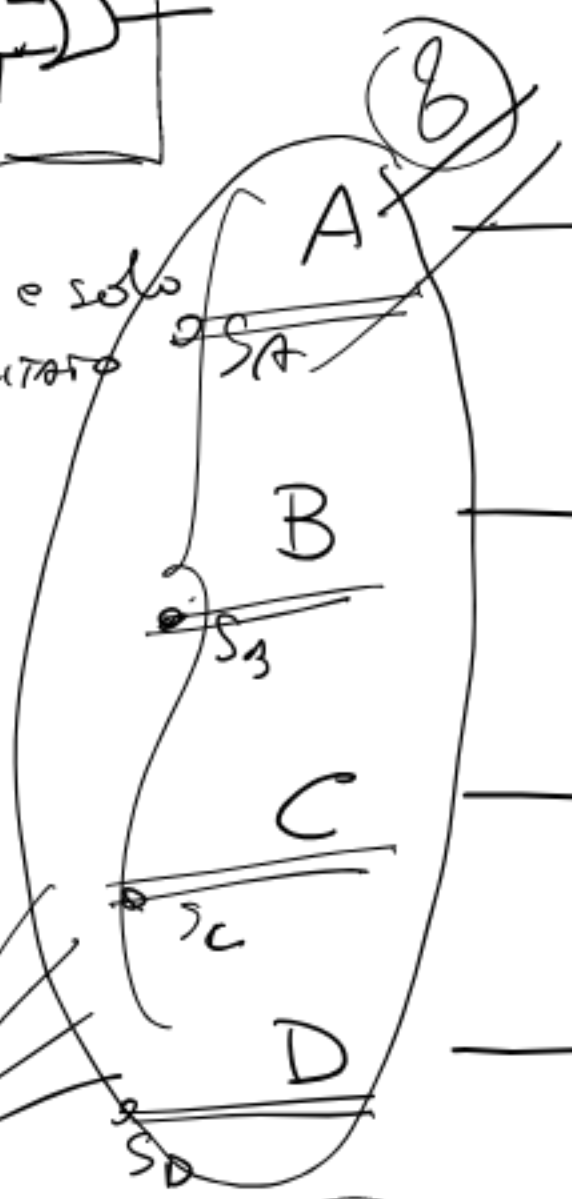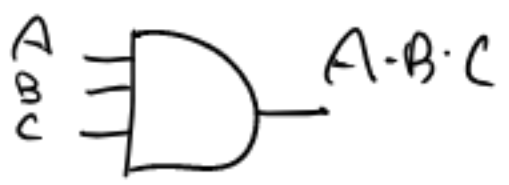

6


MUX 4-1

4 VAR + 2 SEC =


6 VAR IN


$2^6 = 64$ COMBINATIONS

MUX 2-1

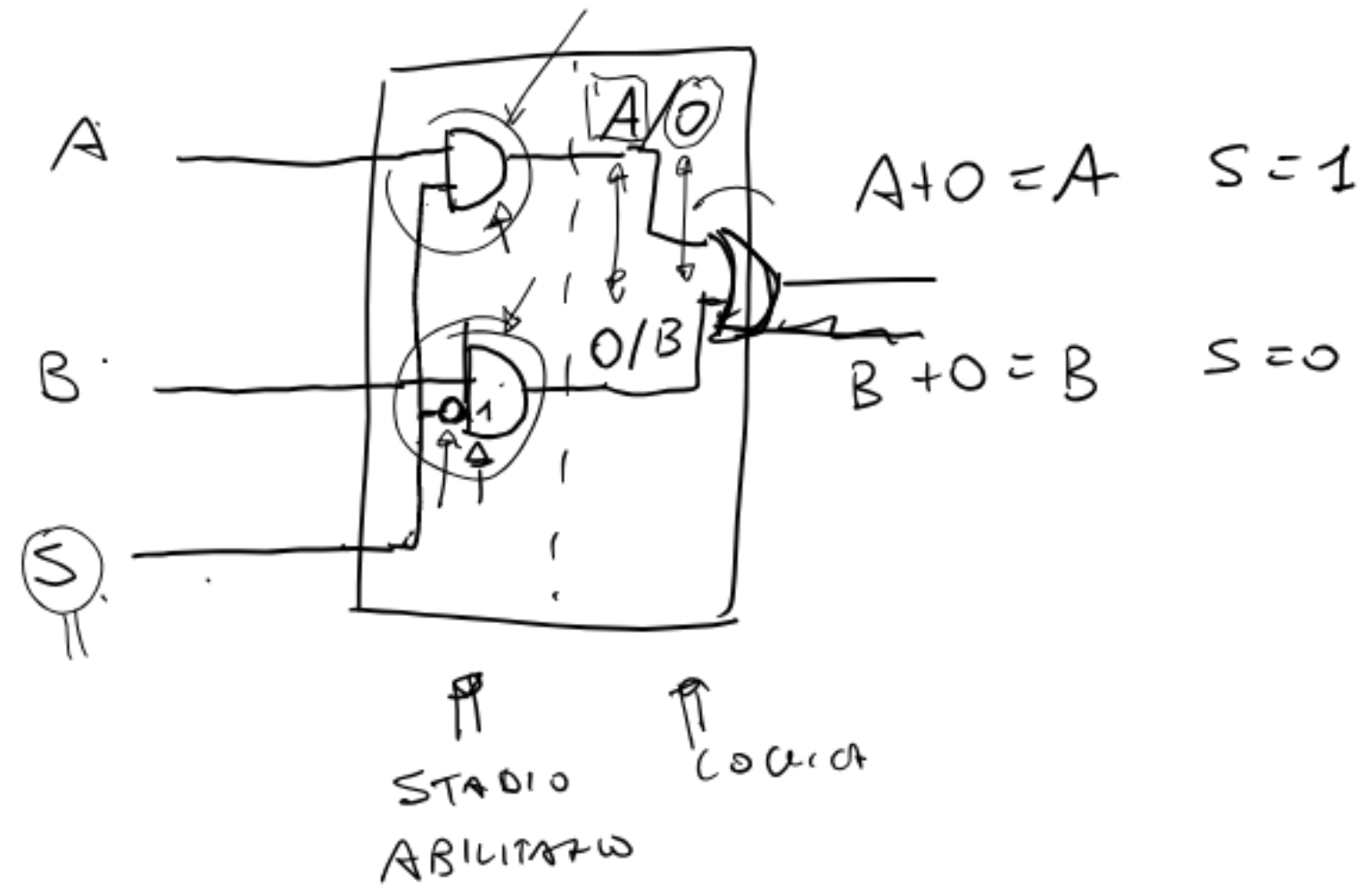

MUX 4-1

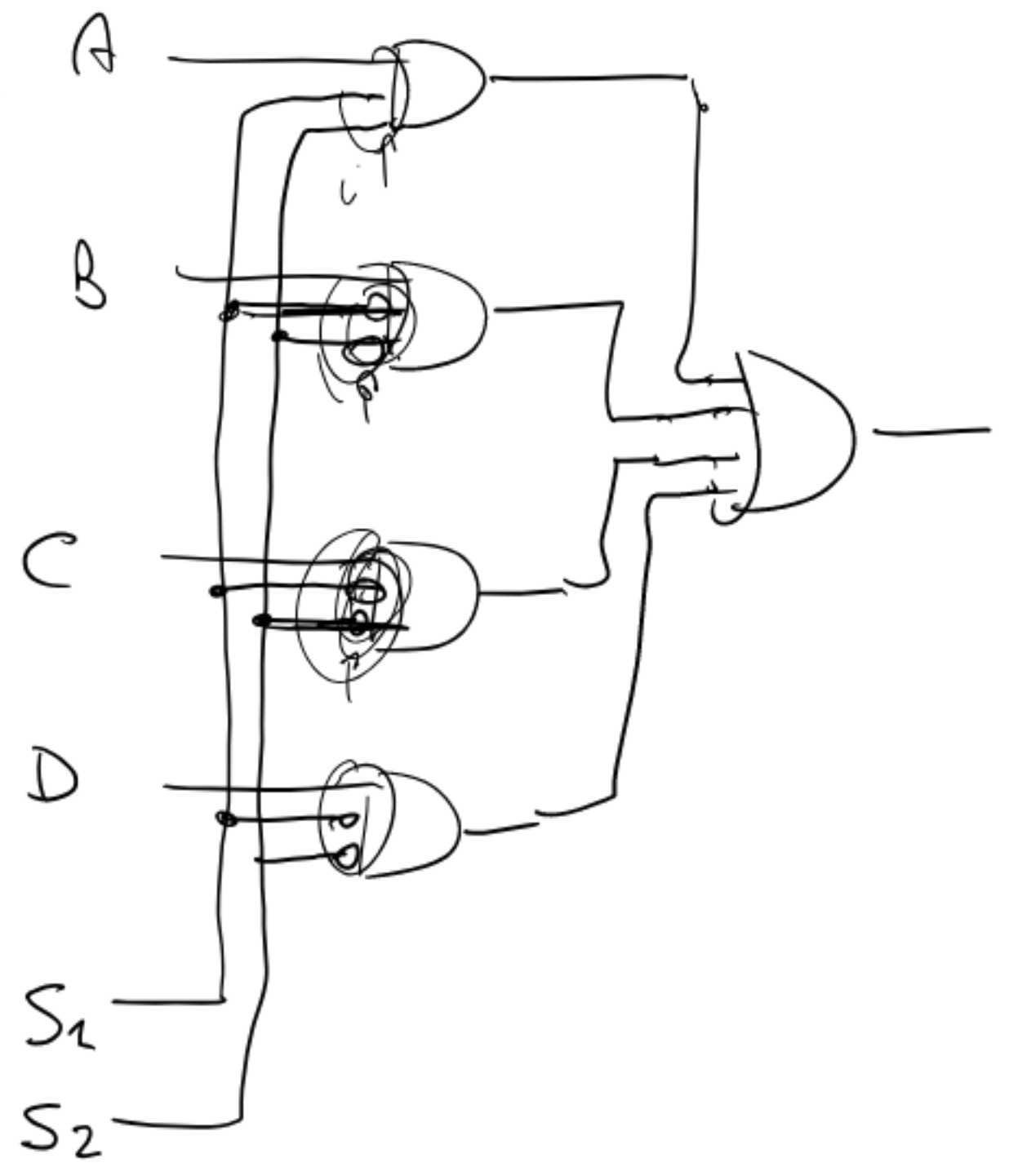


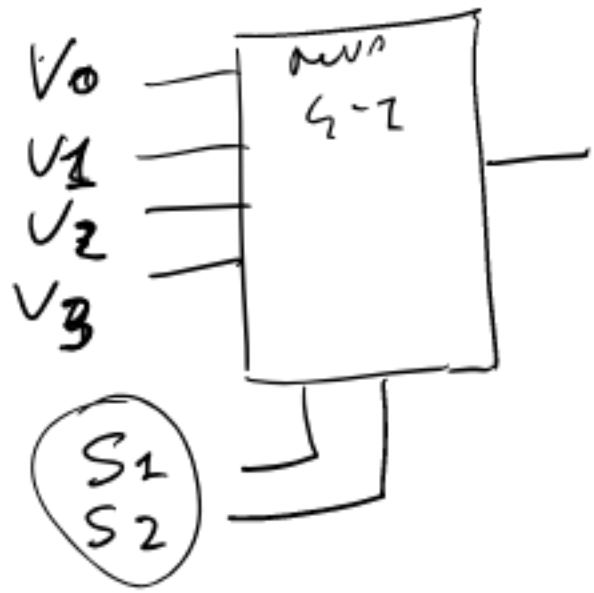


PIO-SIG MEMO SIG.



↓ ↓

dec	S_2	S_1	
0	0	0	V_0
1	0	1	V_1
2	1	0	V_2
3	1	1	V_3


BIN

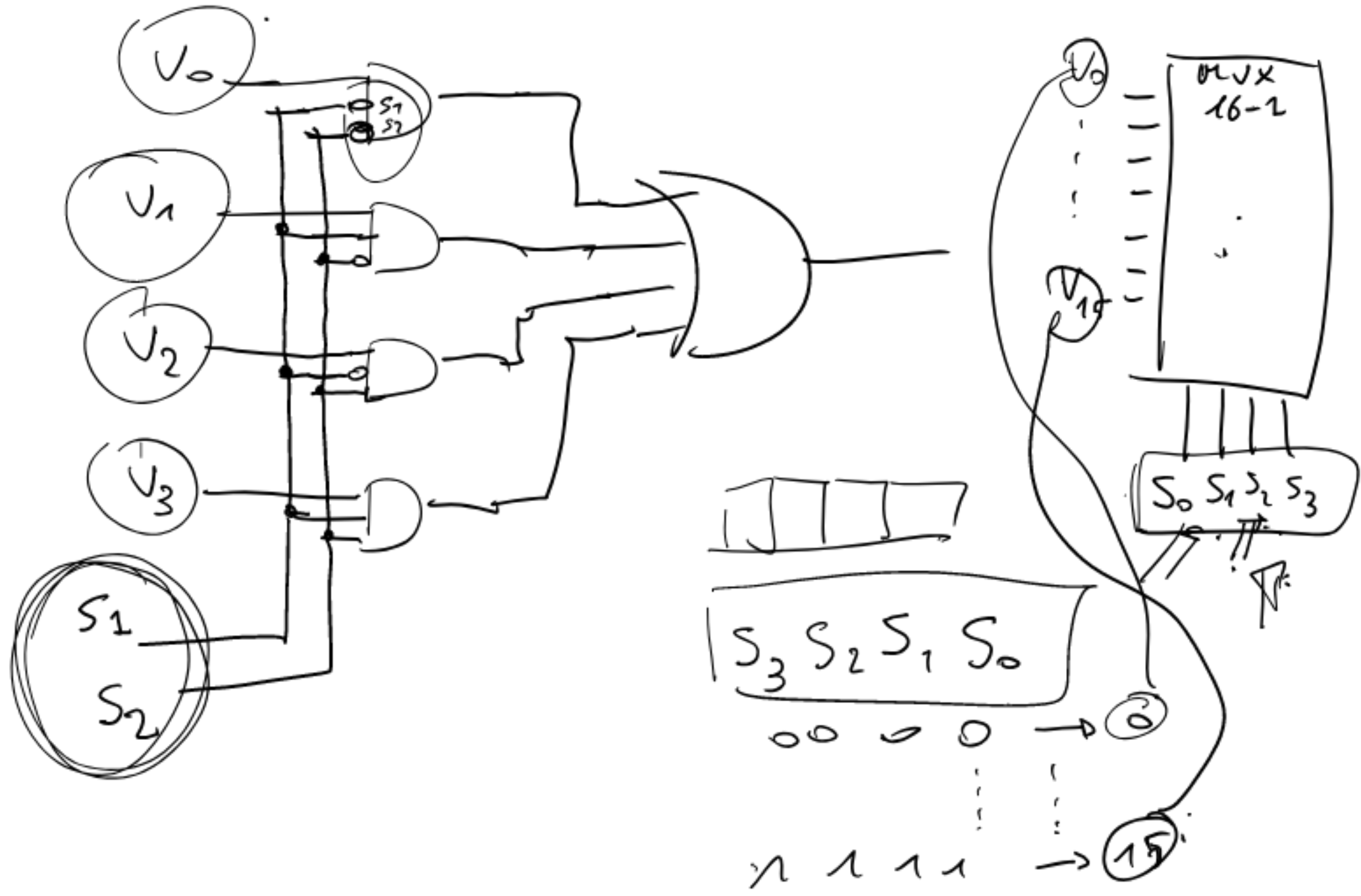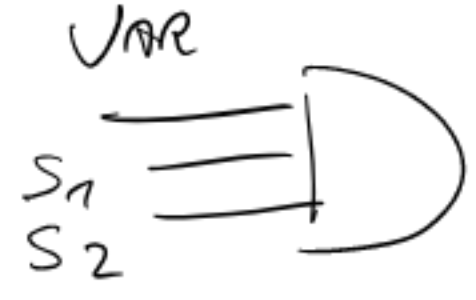

DEMUX

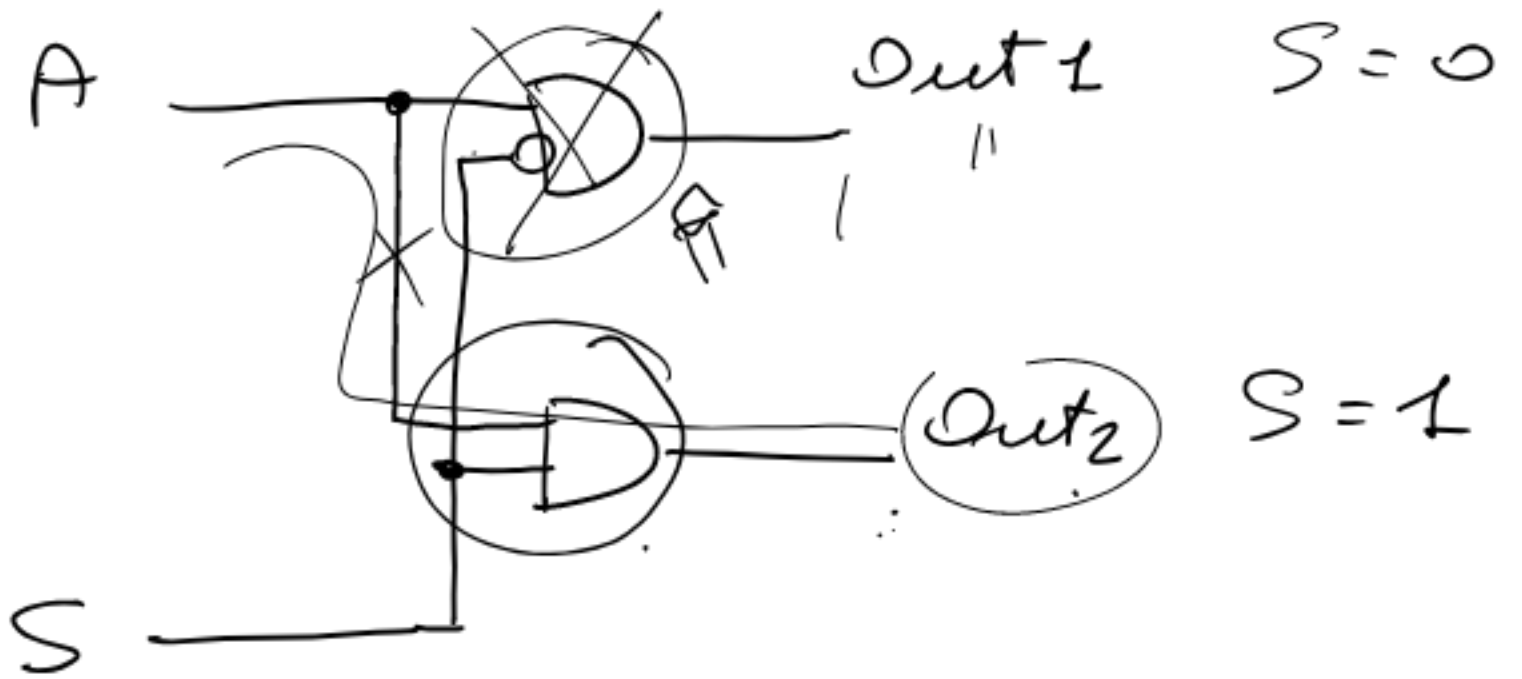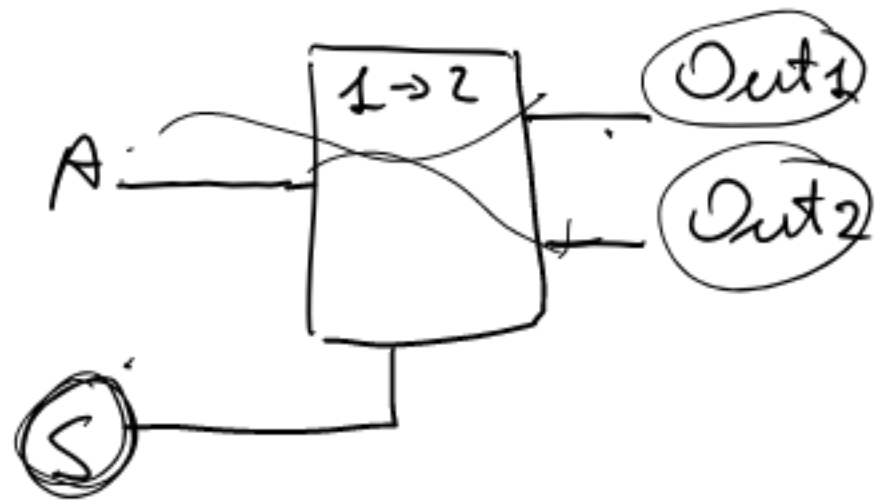


DEMUX 1 to 4

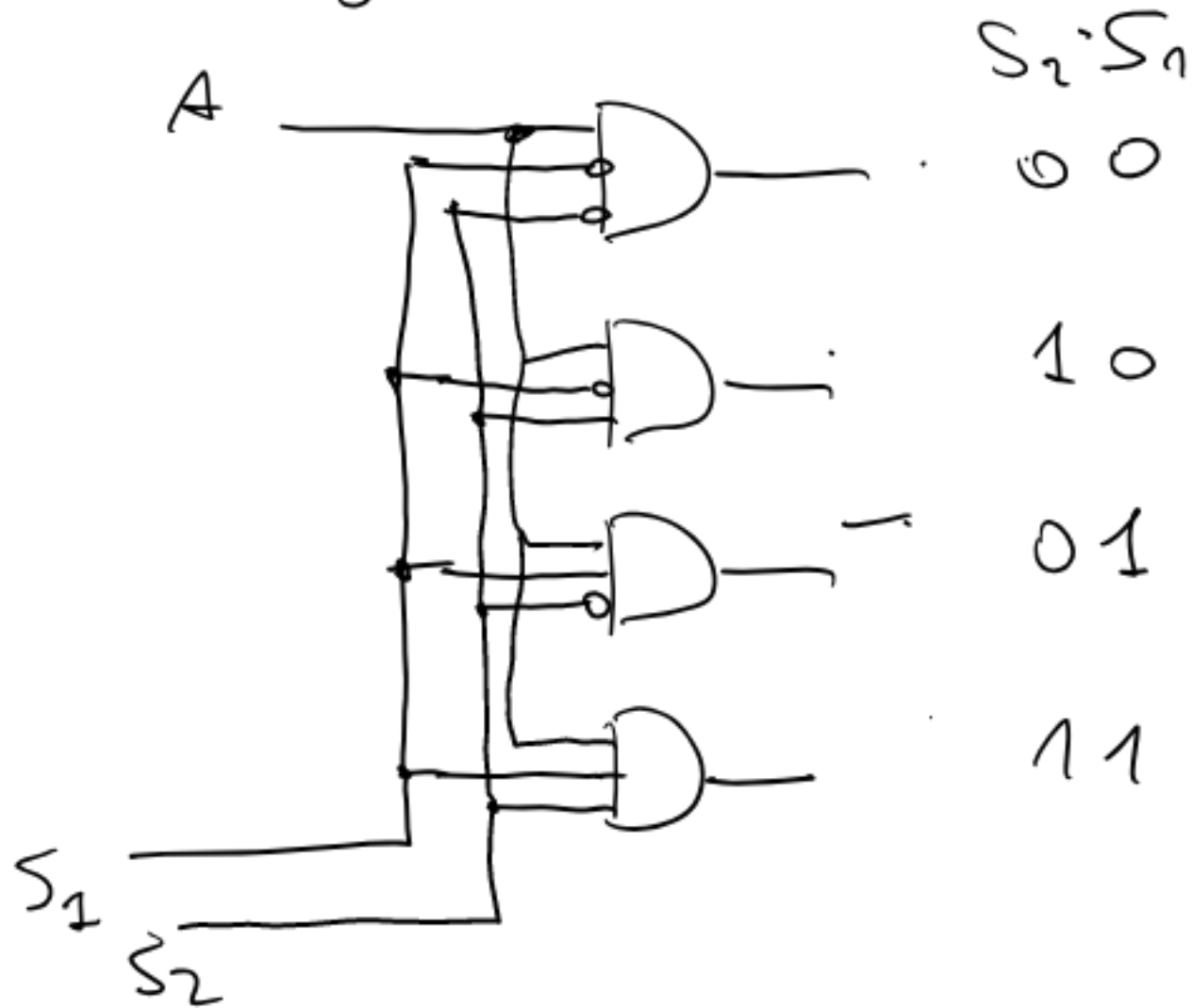

SOMMATORE (?)

$A_0 \oplus A_2$



CARRY RIPORTO

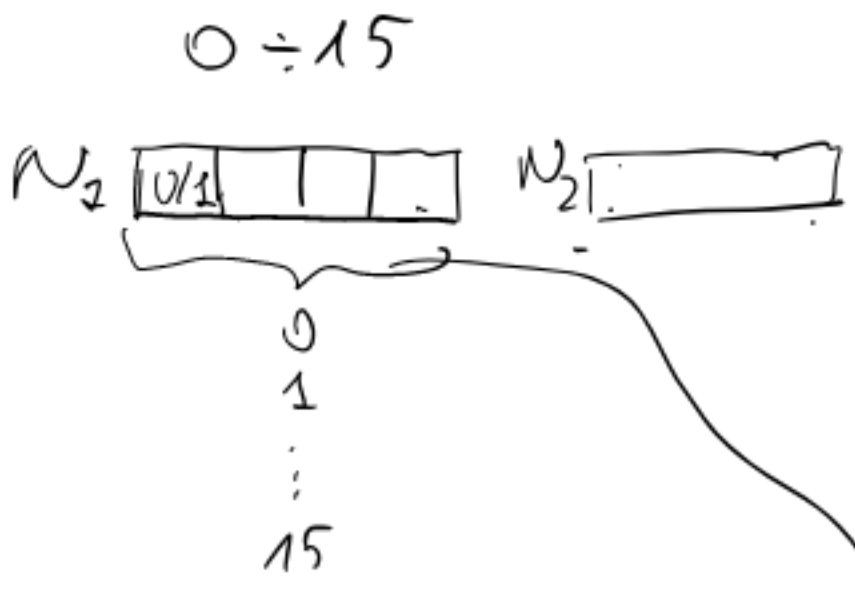


B_0	A_0	S	C
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

$C = A_0 \cdot B_0$
 $S = A_0 \oplus B_0$



$N_1 + N_2 = S$
 Addend

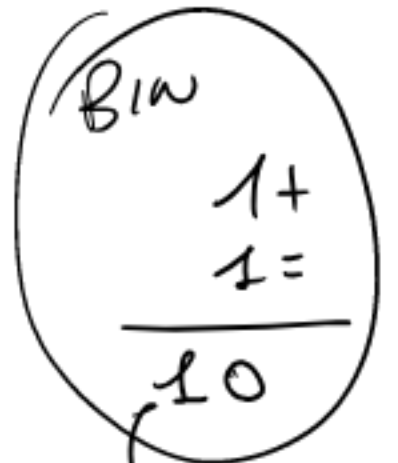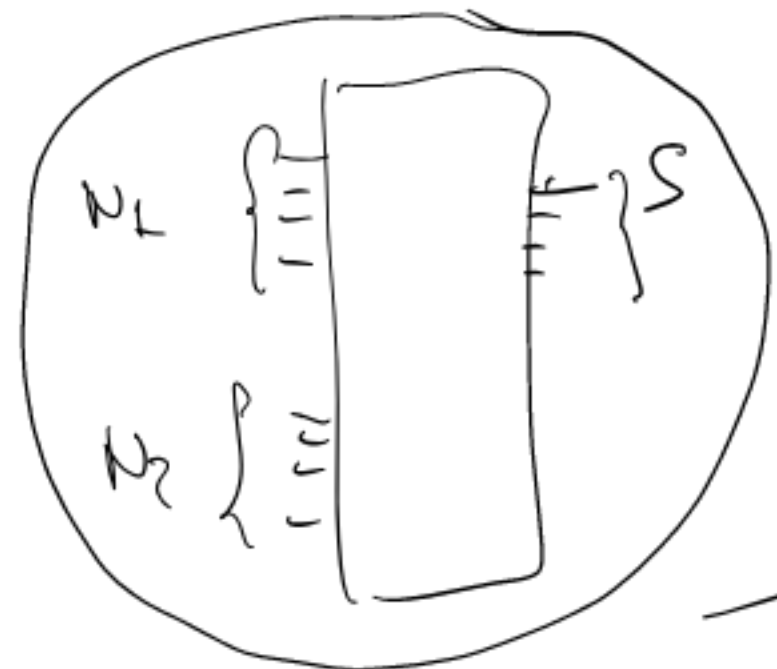


Dec. 2

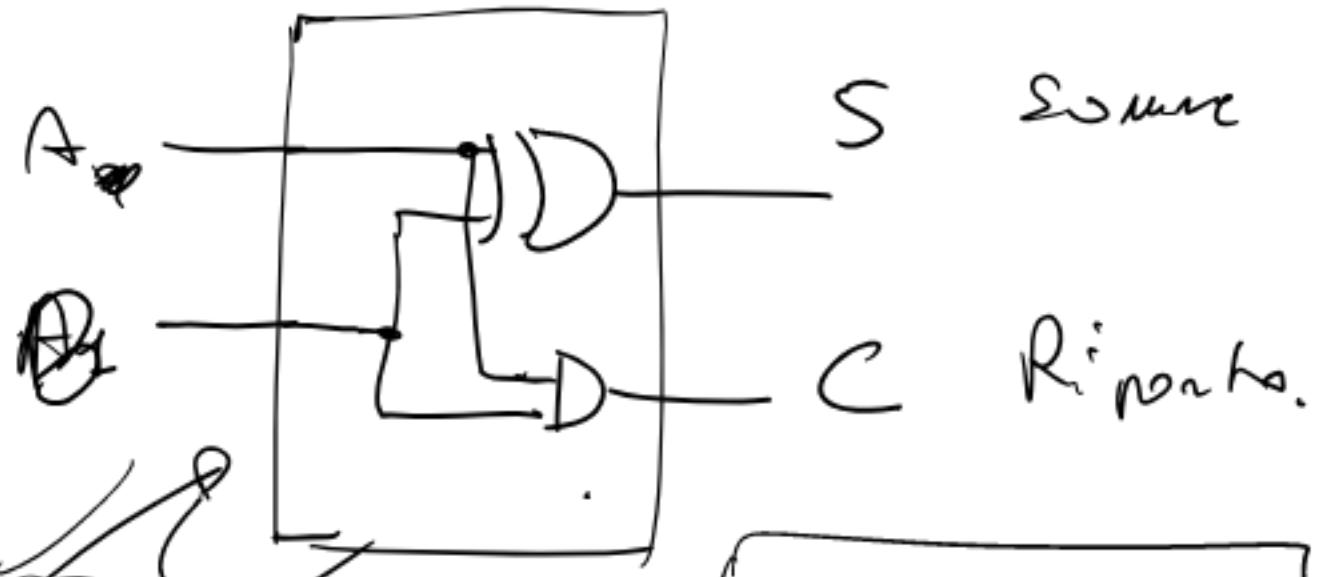

HALF-ADDER

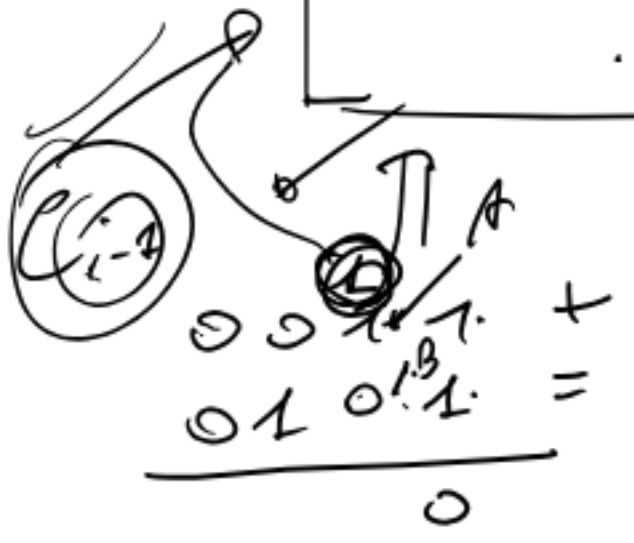
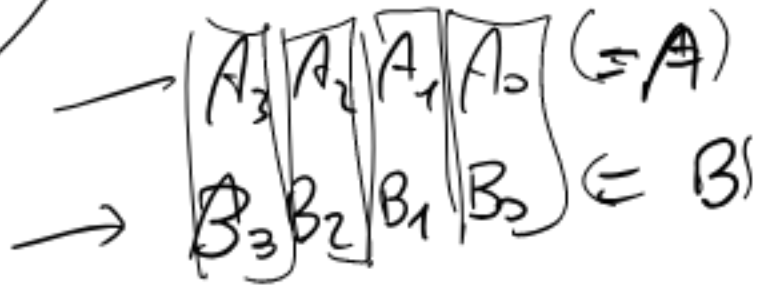


SOMMATORI

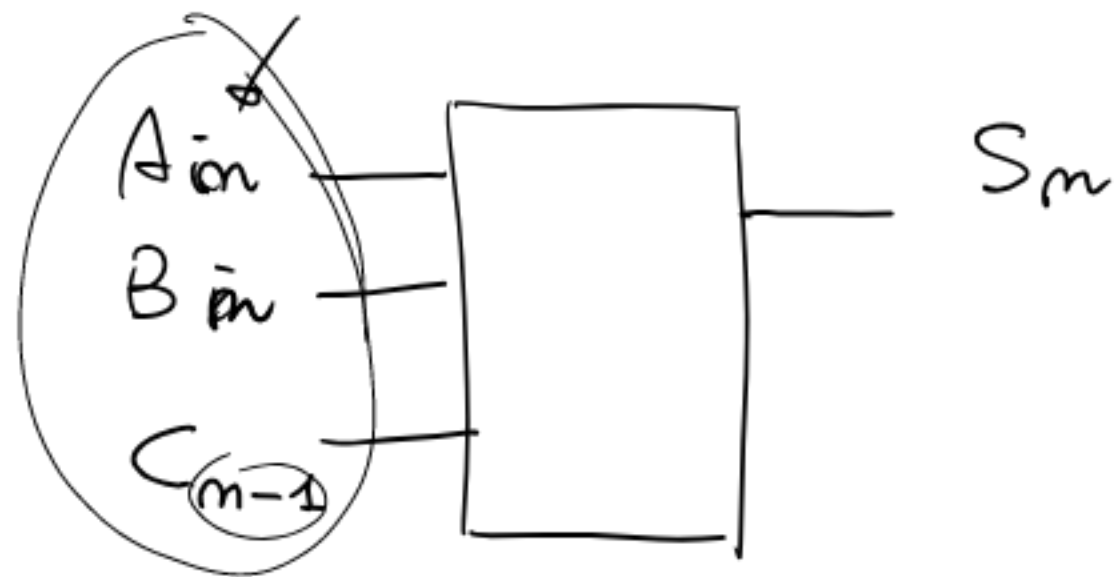


C_{m-2}	A_m	B_m	S_m^H	S	C_0	C_1	C_m
0	0	0	0	0	0	0	0
0	0	1	1	1	0	0	0
0	1	0	1	1	0	0	0
0	1	1	0	0	1	0	0
1	0	0	0	1	0	1	1
1	0	1	1	0	0	1	1
1	1	0	1	0	0	1	1
1	1	1	0	1	1	0	0

$S_m^H \oplus C_{m-2}$

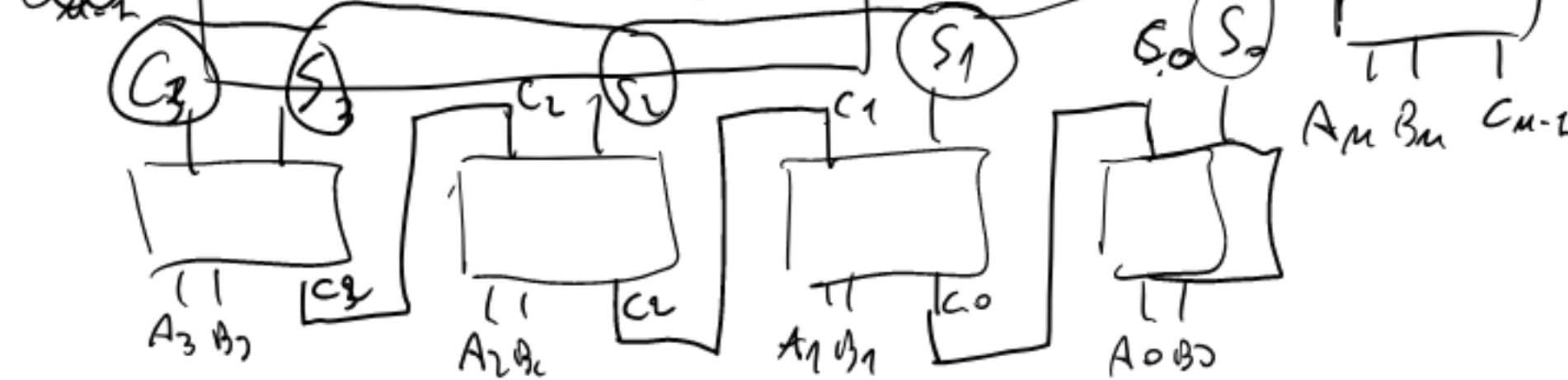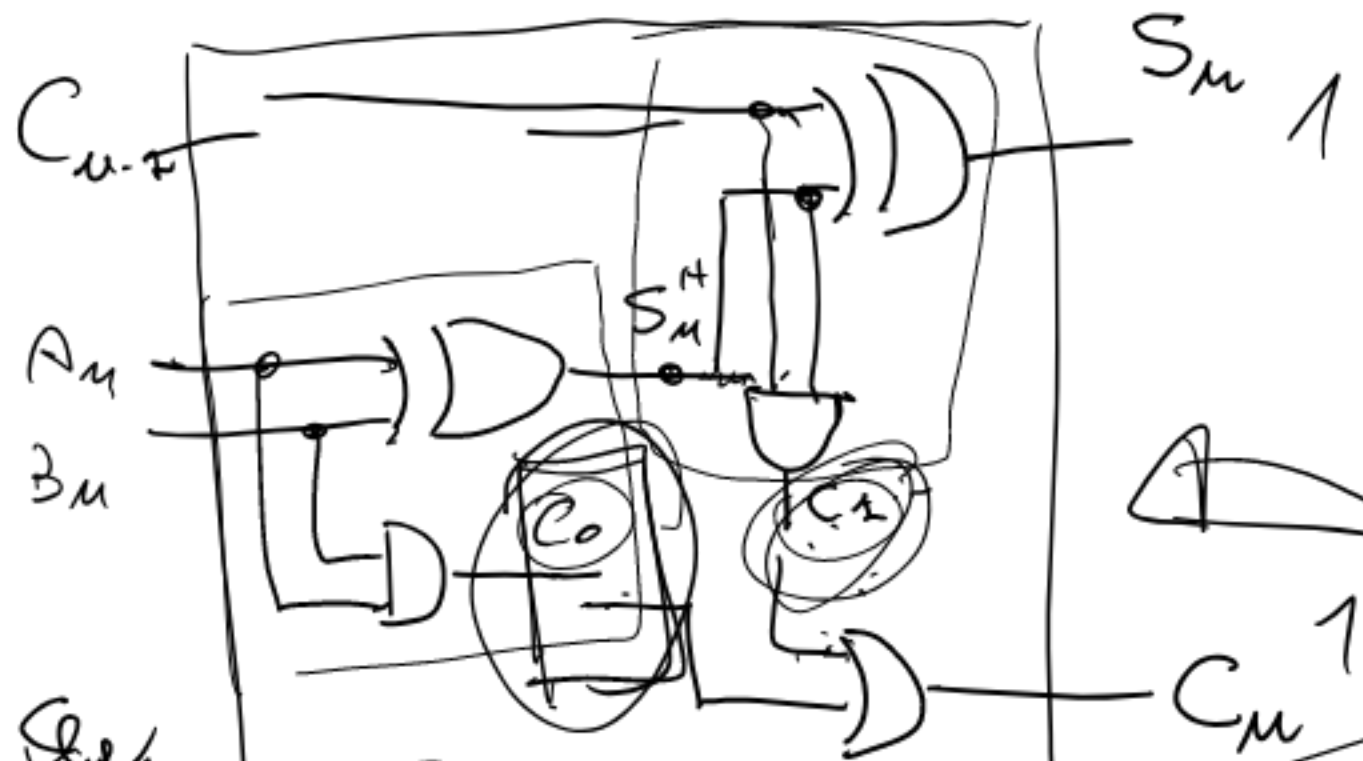

$$C_m = C_0 + C_1$$

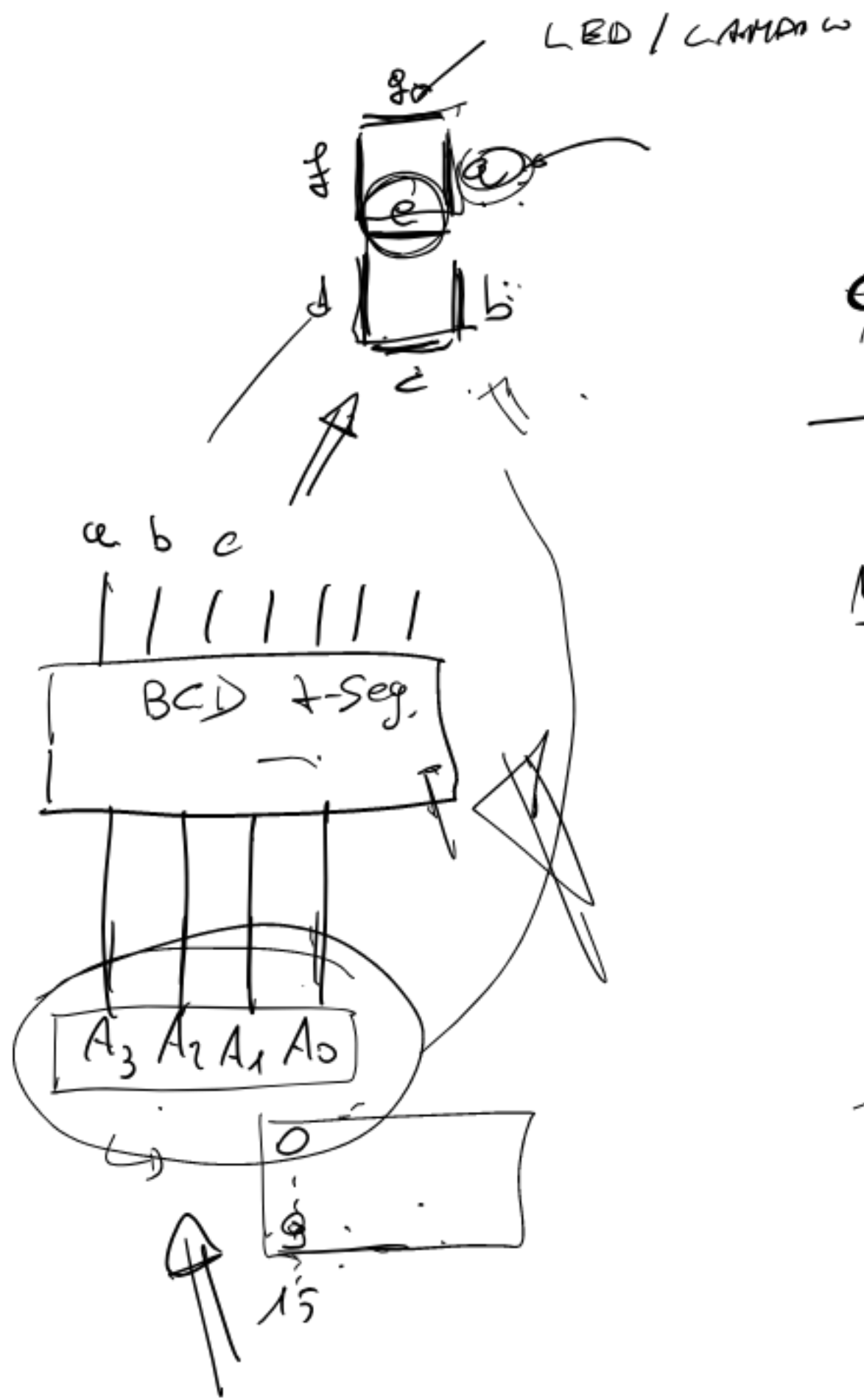

DISPLAY

	A ₃	A ₂	A ₁	A ₀	a	b
0	0	0	0	0	1	
1	0	0	0	1	1	
2	0	0	1	0	1	
3	0	0	1	1	1	
4	0	1	0	0	0	
5	0	1	0	1	0	
6	0	1	1	0		
7	1	0	0	0		
8	1	0	0	1		
9	1	0	1	0		