




$$X + Y = \overline{X \cdot Y}$$

$$A \oplus B = \overline{A}B + A\overline{B} = \overline{A}B + A\overline{B}$$

A	B	$A \oplus B$
0	0	0
0	1	1
1	0	1
1	1	0

$$\overline{A}B = \overline{A}B + \overline{A}B\overline{B} = B(\overline{A} + \overline{A}\overline{B}) = B \cdot \overline{A}$$
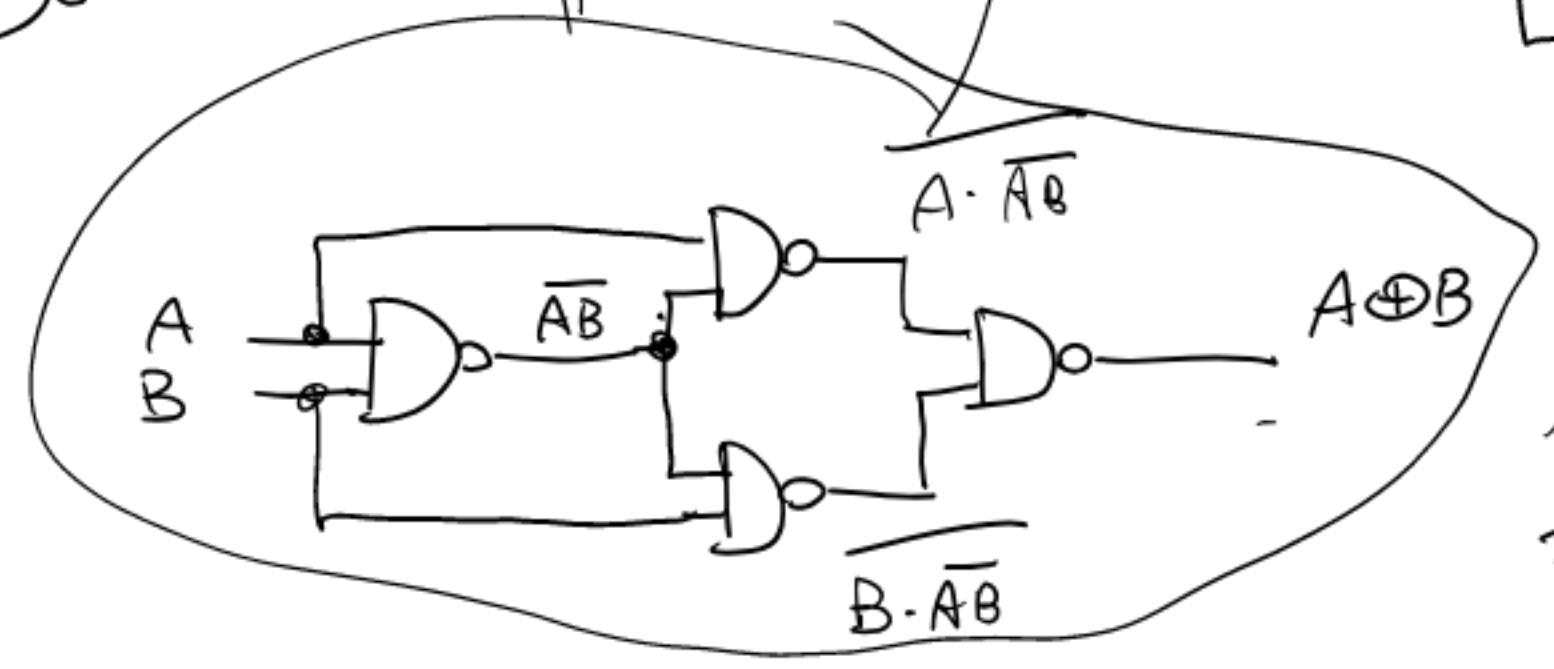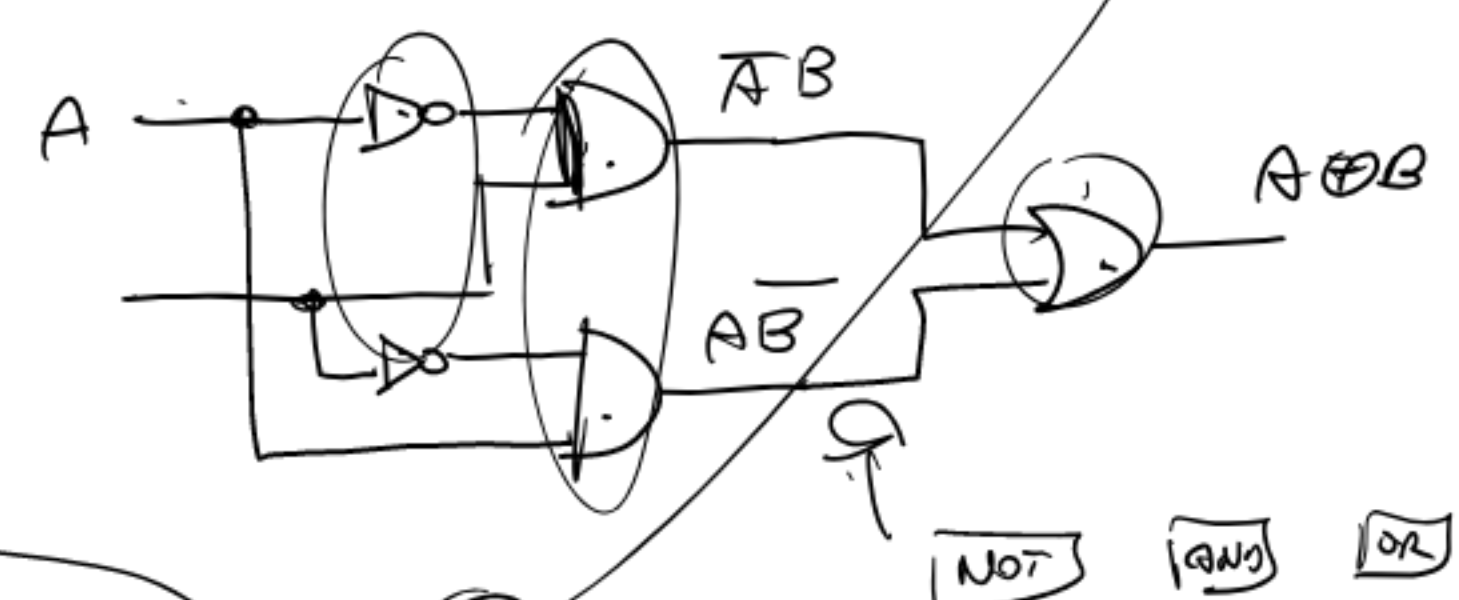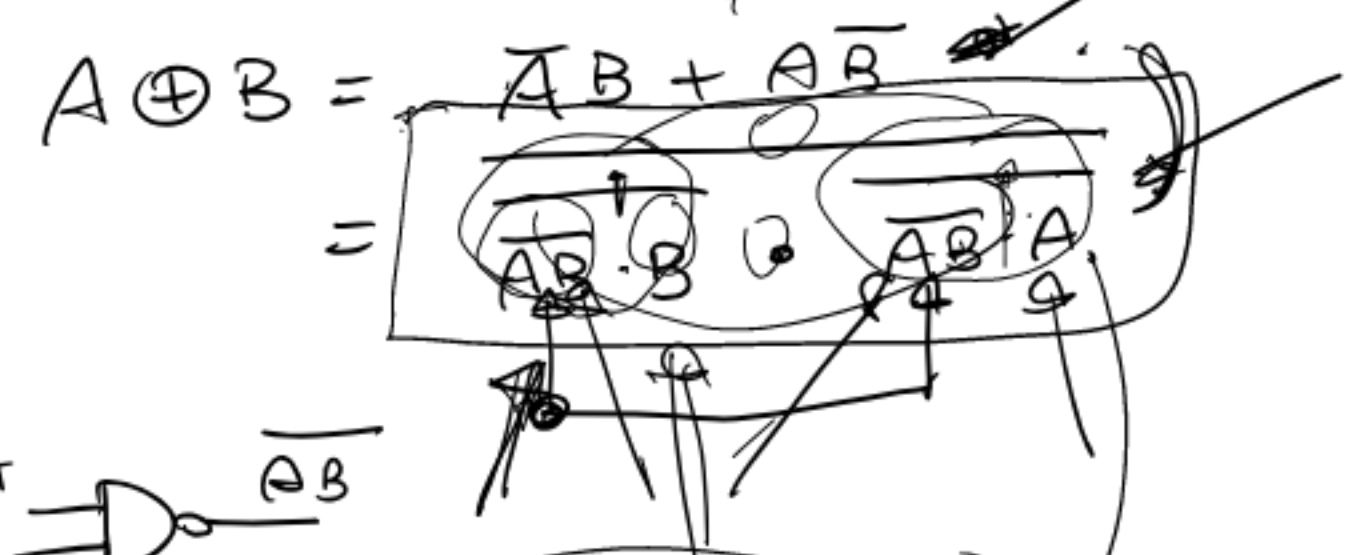
$$\overline{A\overline{B}} = \overline{A\overline{B} + A\overline{B}A} = \overline{A(\overline{B} + \overline{B}A)} = \overline{A \cdot \overline{B}}$$



4 PORTS

NOT AND OR

4 PORTS

XOR  $A \oplus B = \overline{\overline{A \cdot B} + \overline{A \cdot \overline{B}}} = F_{xor} \neq$

②

SCAMBIO (AND → OR) ⇒ F



$$F = \overline{A+B} + B + \overline{A+B} + A = \overline{A \cdot B} + B + \overline{A \cdot \overline{B}} + A$$


A	B	F	XOR
0	0	1	0
0	1	0	1
1	0	0	1
1	1	1	1

$$= \overline{(\overline{A \cdot B} + B) \cdot (\overline{A \cdot \overline{B}} + A)} = (\overline{A \cdot B} + B)(\overline{A \cdot \overline{B}} + A) =$$

$$= \overline{A \cdot B} + \overline{A \cdot \overline{B}} + B \cdot \overline{A \cdot \overline{B}} + A \cdot B = \overline{A \cdot B} + \overline{A \cdot \overline{B}} + A \cdot B$$

XNOR

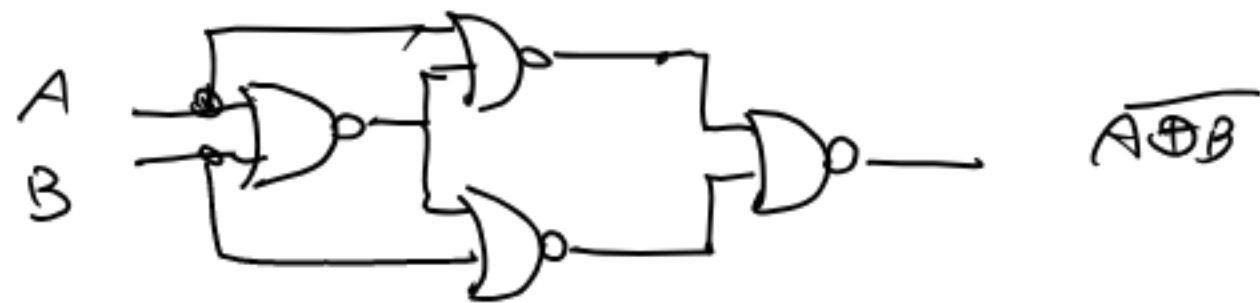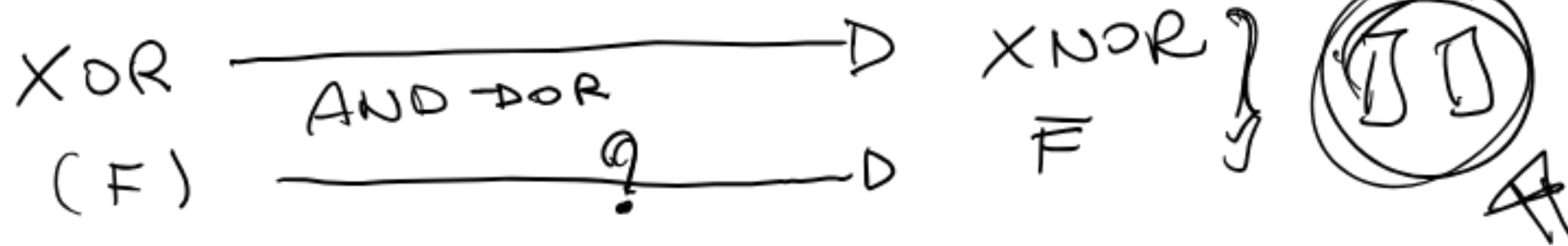

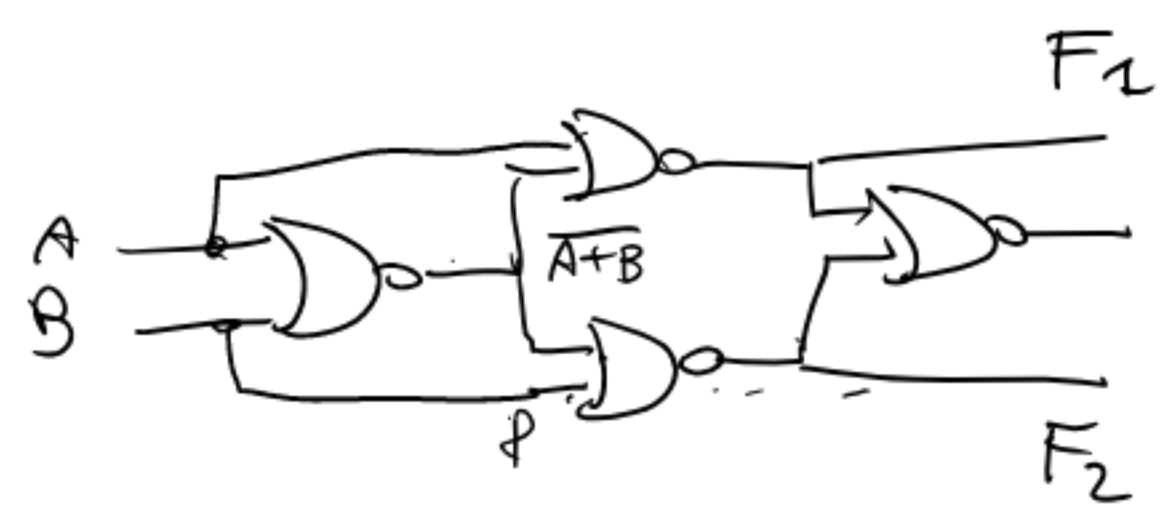

$A \oplus B$



A	B	$A \oplus B$	$F_1$	$F_2$
0	0	0	0	0
0	1	1	0	1
1	0	1	1	0
1	1	0	1	1


$\boxed{E}$        $\boxed{A < B}$        $\boxed{A > B}$

$$F_1 = \overline{A+B} + A = (A+B) \cdot \bar{A} = \bar{A} + AB = \bar{A}B$$



$$F_2 = \overline{A+B} + B = (A+B) \bar{B} = A\bar{B} + \bar{B}B = A\bar{B}$$

COMPARATORE

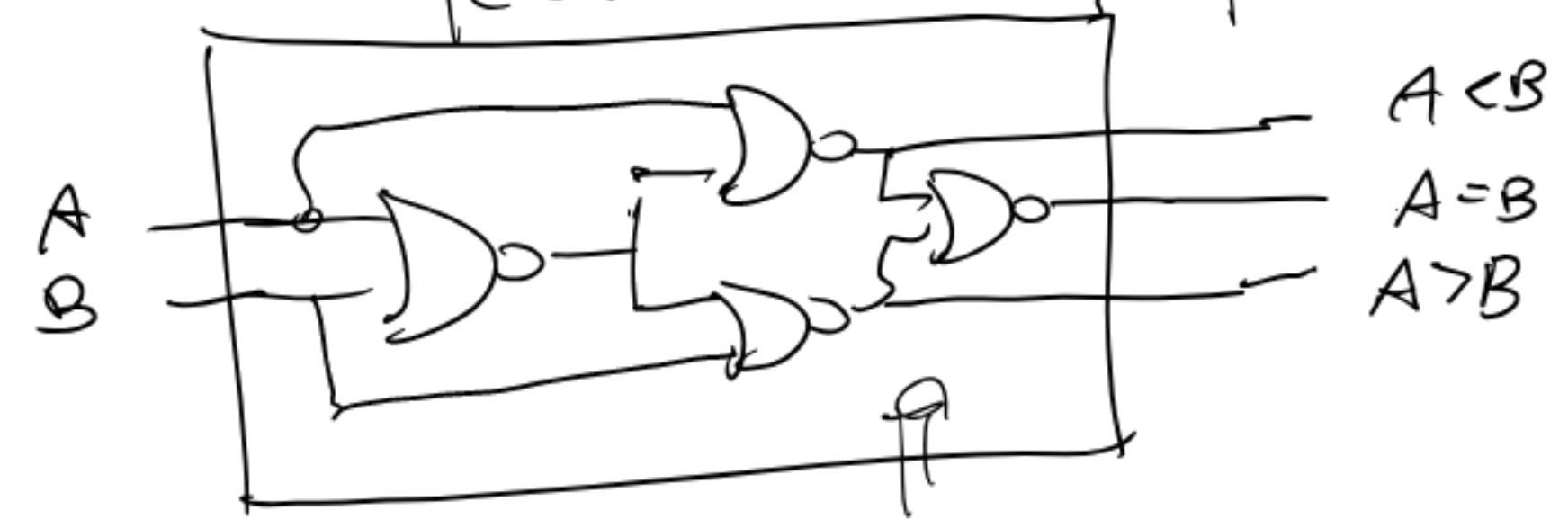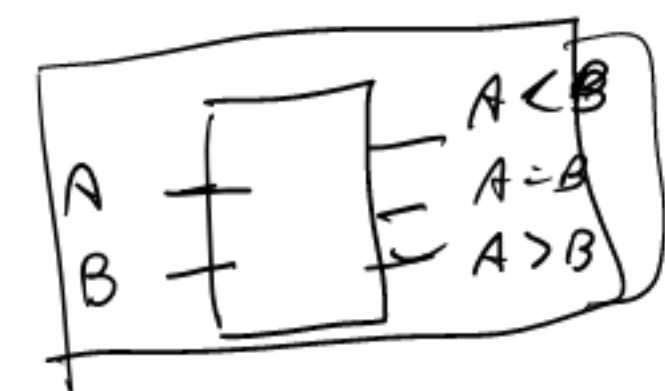

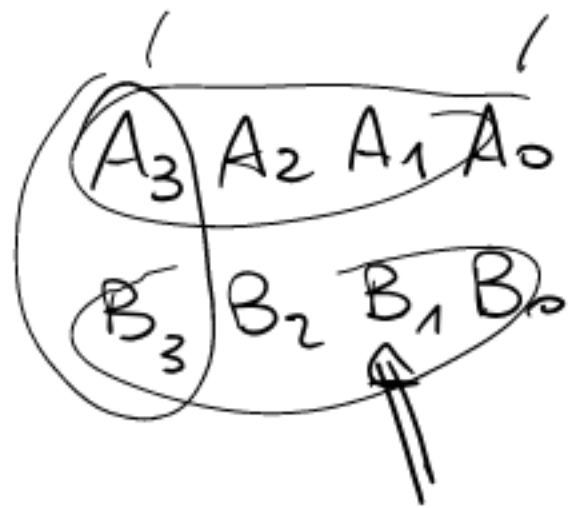

→ 0 ÷ 16

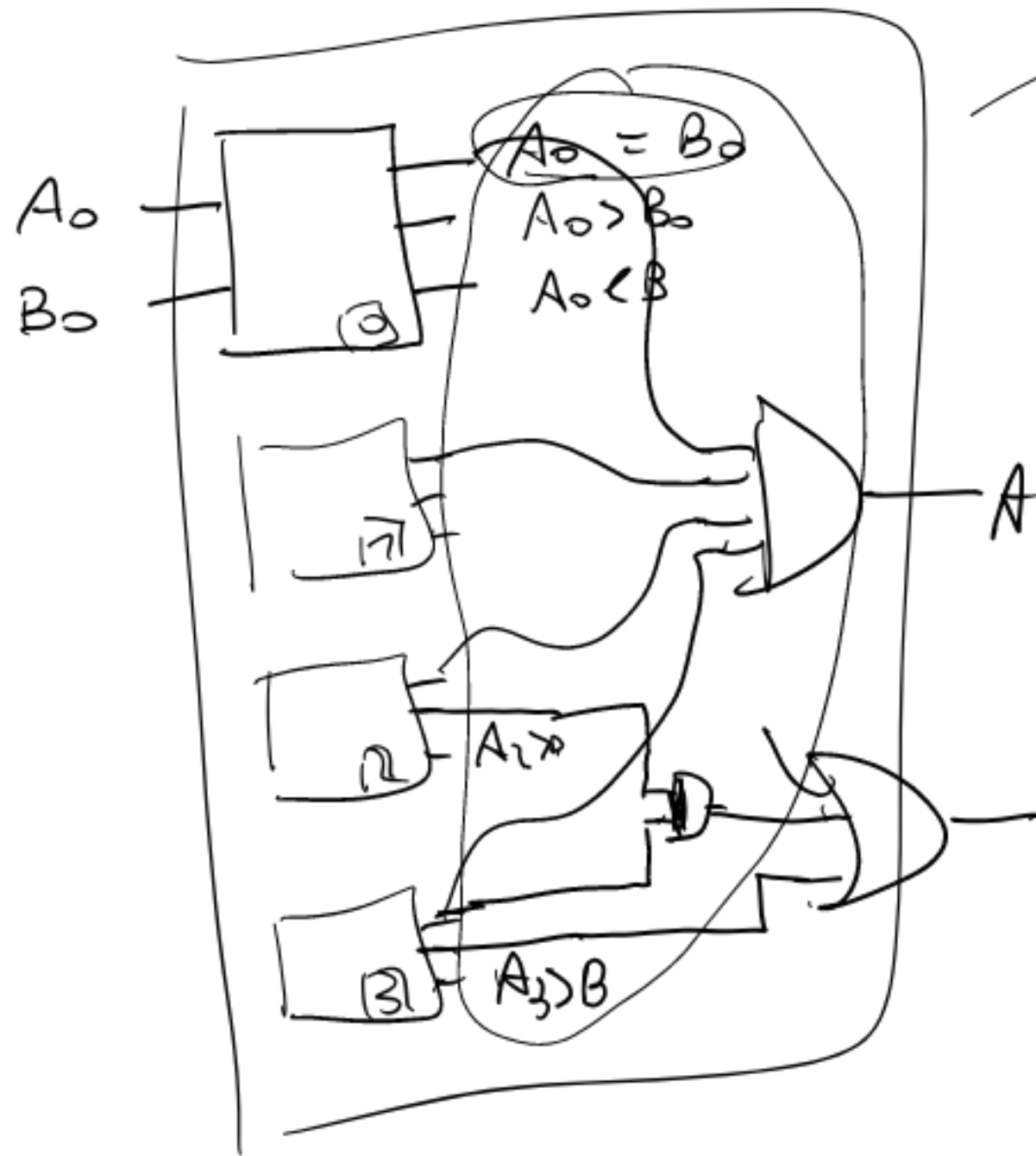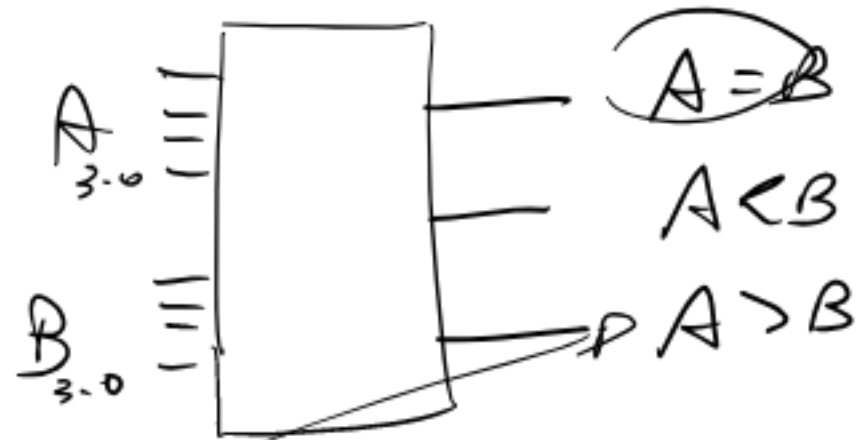

$$\underline{A=B} \iff A_0=B_0 \text{ AND } A_1=B_1 \text{ AND } A_2=B_2 \text{ AND } A_3=B_3$$





$$\underline{A > B} = (A_3 = B_3 \text{ AND } A_2 > B_2) \text{ OR } (A_3 = B_3 \text{ AND } A_2 = B_2 \text{ AND } A_1 > B_1) \text{ OR } (A_3 = B_3 \text{ AND } A_2 = B_2 \text{ AND } A_1 = B_1 \text{ AND } A_0 > B_0)$$



COMPARATOR 4 BIT.

5

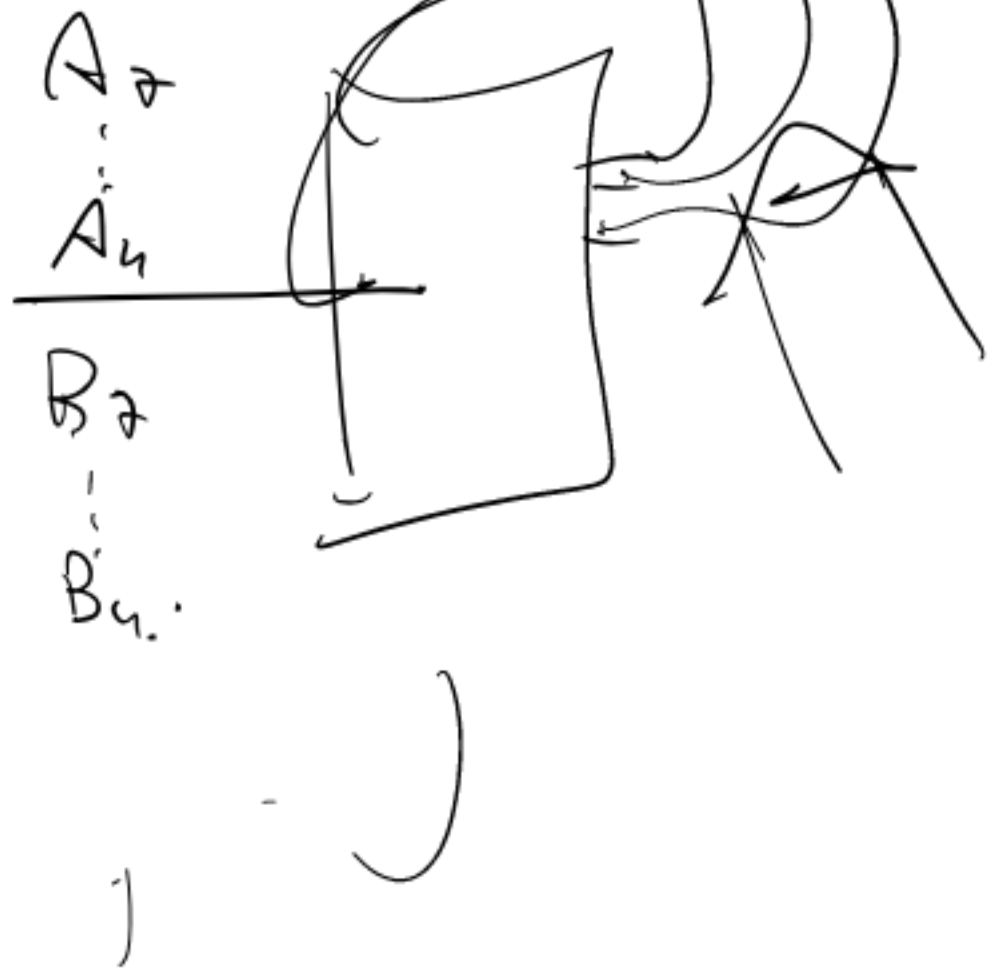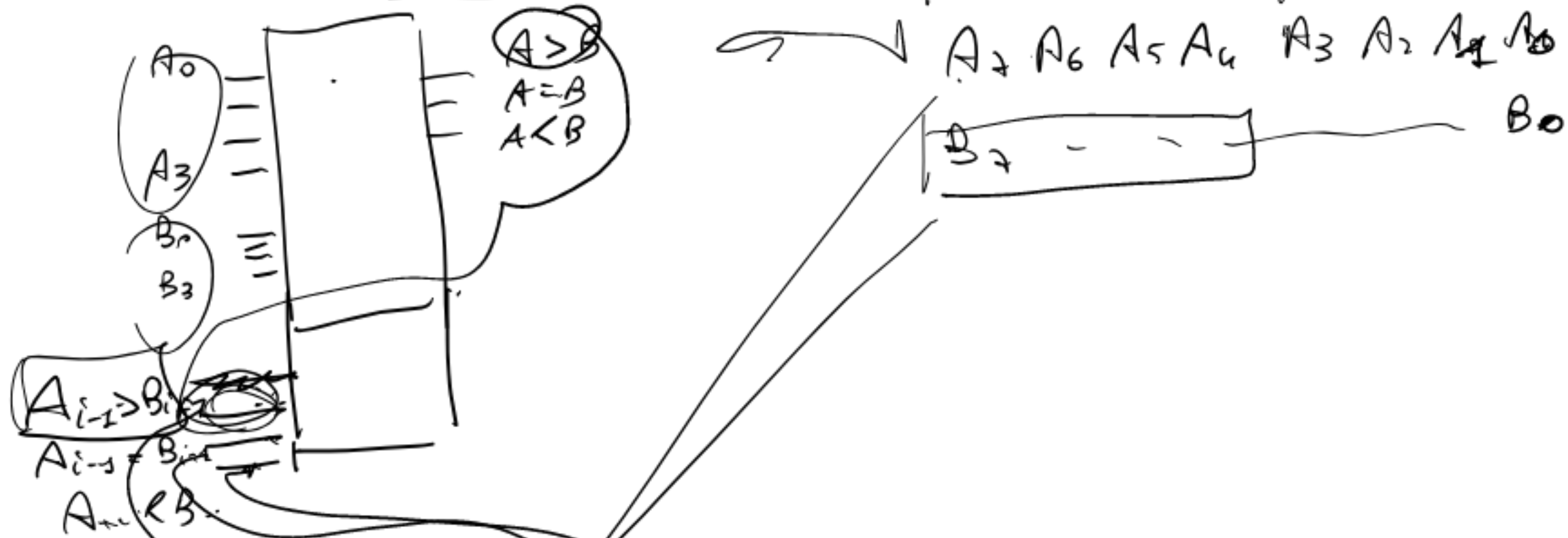

XOR }  
 AND → OR }  
 XNOR }  
 VOR }  
 XNOR }  
 SYMMETRISCHE  
 RESP. TO VAR IN  
A ↔ B

- F → F̄
- 1) AND → OR
  - 2) OR → AND
  - 3) NOT VAR

$$F(A, B, C, \dots, +) \Rightarrow \bar{F}(\bar{A}, \bar{B}, \bar{C}, \dots, +, \dots)$$

deutsches De Morgan

A ⊕ B → A + B =  $\bar{A} \cdot \bar{B}$

A · B →  $\overline{A \cdot B} = \bar{A} + \bar{B}$

$$F = \sum \prod_i = \prod$$

$$\prod =$$

- PORTA. BASE
- UNIVERS
- XOR XOR
- ENABLE / DISABILT
- TRUE / FALSE
- HALF ADDER / FULL ADDER
- COMPARATOR
- MUX / DEMUX

A	B	C	$A \oplus B$	$(A \oplus B) \oplus C$
0	0	0	0	0
0	0	1	0	1
0	1	0	1	1
0	1	1	1	0
1	0	0	1	1
1	0	1	1	0
1	1	0	0	0
1	1	1	0	1

→ Somma strutturata

→ N4 DISPARI

# MAPPE DI KARNAUGH

TAU. VERITA'


A	B	F
0	0	0
0	1	1
1	0	0
1	1	0
<hr/>		
0	1	1
0	0	0
1	0	0
1	1	0
<hr/>		
1	1	0
0	0	0
1	0	1
0	1	

SEQ. COMBINAZIONI :


for me combie e quello succ/prec deve combie solo UNA VARIABILE.

A, B

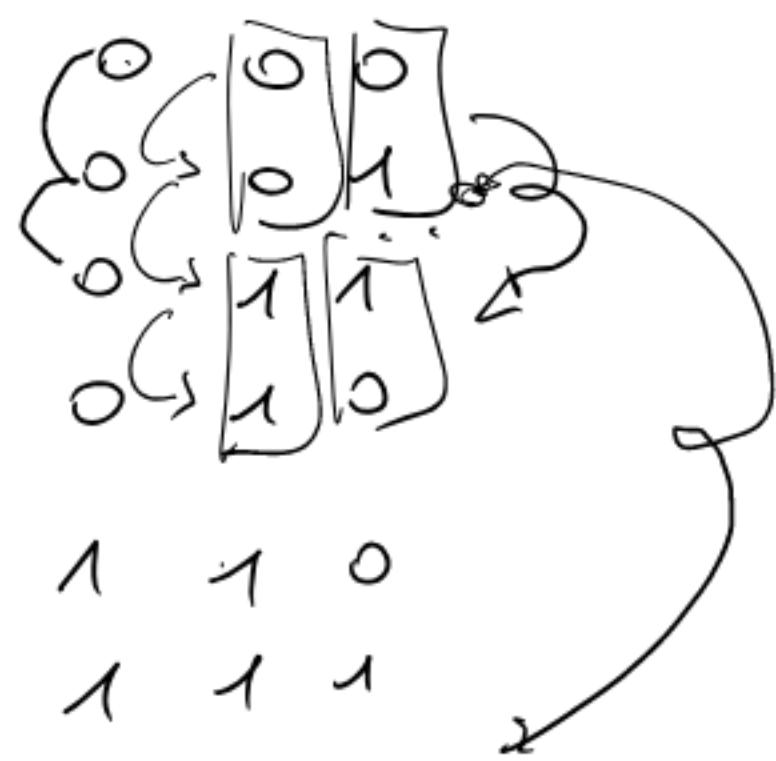
TAB N. CELLE =  $2^{NVAR}$  =  $N$  minterme



1	1	0
1	1	1
1	0	1
1	0	0

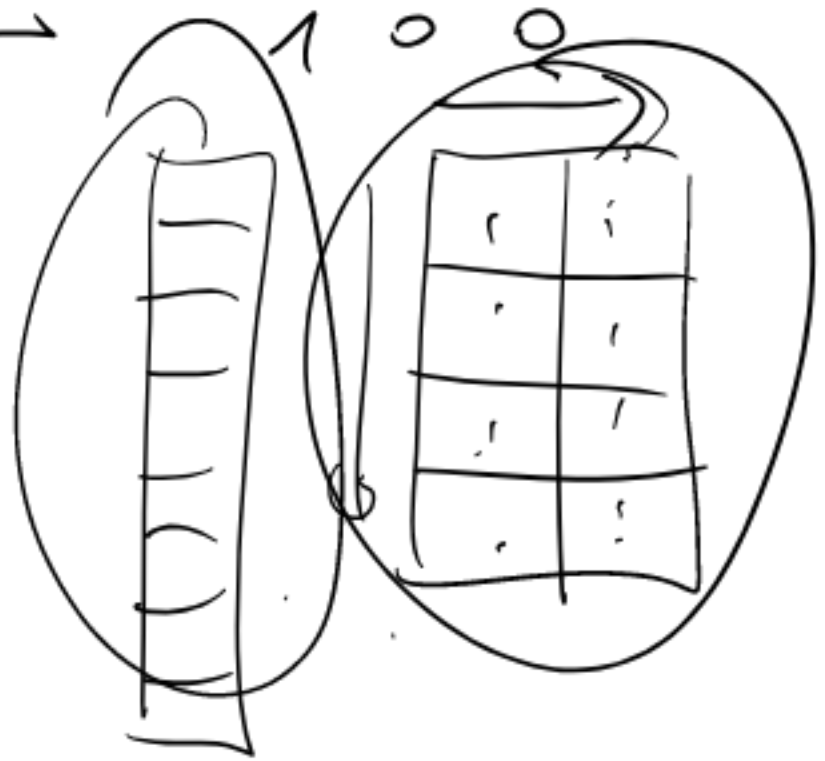

<del>AB</del>	AB
00	
01	
11	
10	

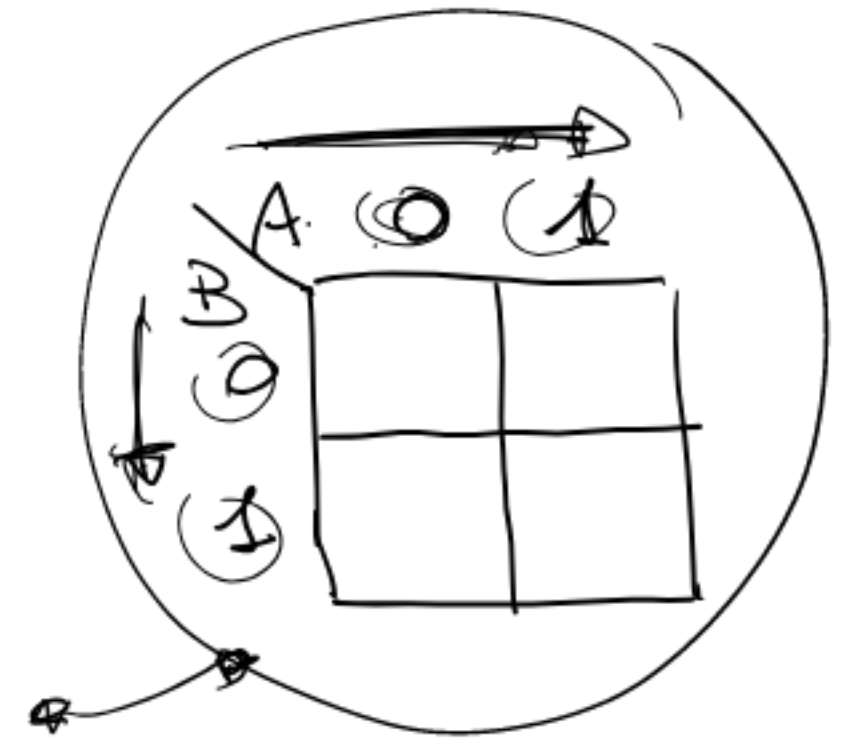



A	B	F	M
0	0	0	$A\bar{B}$
0	1	1	$\bar{A}B$
1	1	1	$AB$
1	0	0	$A\bar{B}$

B/A	0	1
0	$\bar{A}\bar{B}$	$A\bar{B}$
1	$\bar{A}B$	$AB$

Solo celle  
min,  $F_i = 1$

$B = \text{cos}$

B/A	0	1
0	1	1
1	1	1

$M-K$

$F = \bar{A}B + AB$

$F = \bar{A}B + AB = B(\bar{A} + A)$

$F = B$

SIMPLIF. ALGEBRA

RAGGRUPPARE LE CELLE ADIACENTI.

TERMINE SEMPLIFICAZIONE

REGOLE

VAR CAMBIANO  $\frac{1}{2}$  se tutte le costanti


VAR COSTANTI

ROMANA

U  
SEMPLIFICAZIONE




ABC	
000	
001	
011	
010	
110	
111	
101	
100	

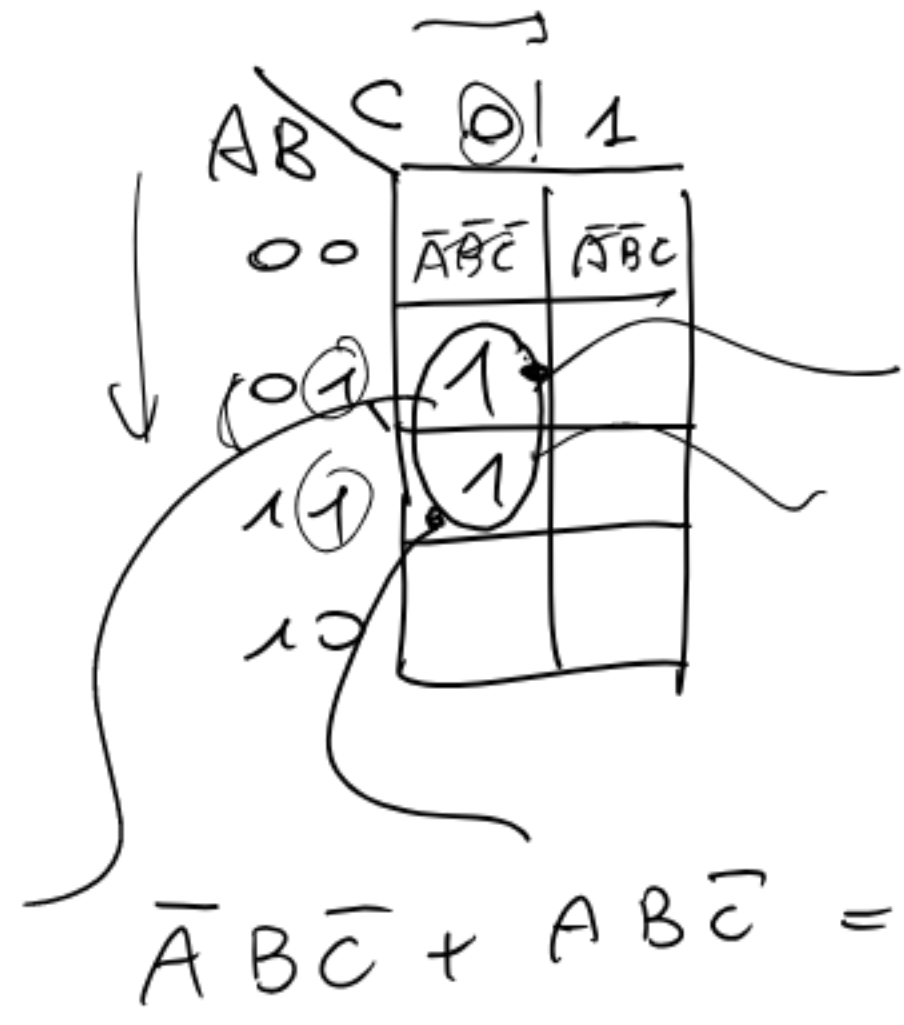

~~A~~ $\bar{B}\bar{C}$   
 $\bar{B}\bar{C}$

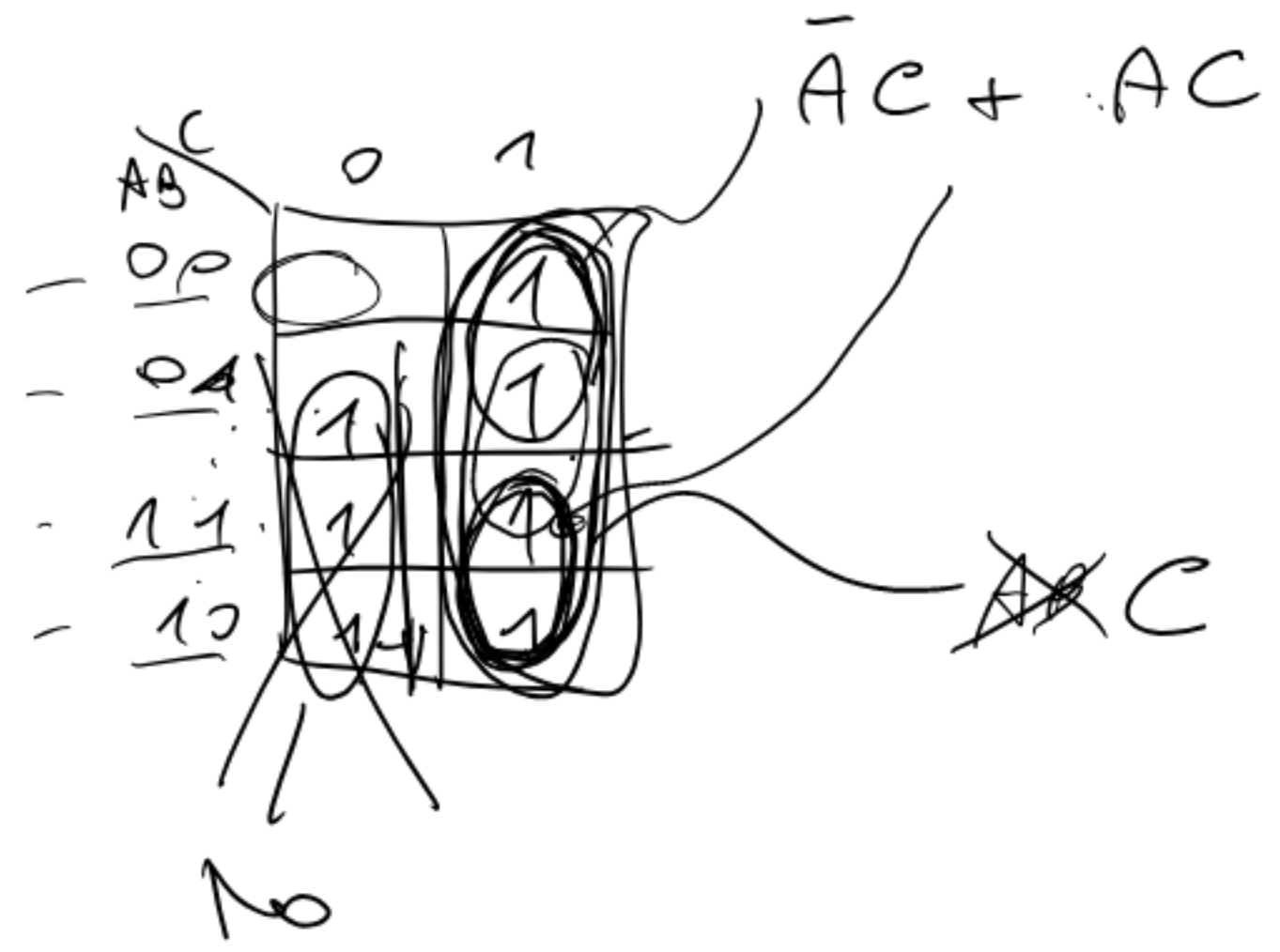$\bar{A}\bar{B}\bar{C} + A\bar{B}\bar{C} = \bar{B}\bar{C}(\bar{A} + A) = \bar{B}\bar{C}$



- I) RAGGAP.  
PIU GRANDE  
POSSIBILE.
- II) N CELLE RAGGAP.  
2<sup>n</sup> !!

	0	1
00		1
01	1	1
10	1	1
11		

$C + CB$

III) Ragg. si possono  
intersecare.

$B\bar{C} + A\bar{C} = \bar{C}(A+B)$

IV) NO Ragg. contenuto  
in altro  
ragg.

$C + CB = C(1+B) = C$

	0	1
00		1
01		1
10	1	1
11	1	1

$N \neq 2^i$

V) Ragg. quadrato / rettangolare.

$A + C$

Più sono grandi Ragg.

⇒ MEMO VAR  
Contengono

$F = \text{MINITERM}$

	<u>ABCD</u>			
AB	00	01	11	10
CD	00	01	11	10
00	1		1	1
01				
11	1	1	1	1
10	1	1	1	1

~~ABC~~  
3 VAR

~~CD~~  
2 VAR


~~C~~  
1 VAR

$= A \cdot BC + \overline{A} \overline{B} \overline{C} \overline{D}$

A


AB	00	01	11	10
CD	00	01	11	10
00				1
01	1			1
11				
10				1

AB	00	01	11	10
CD	00	01	11	10
00				
01				
11				
10				

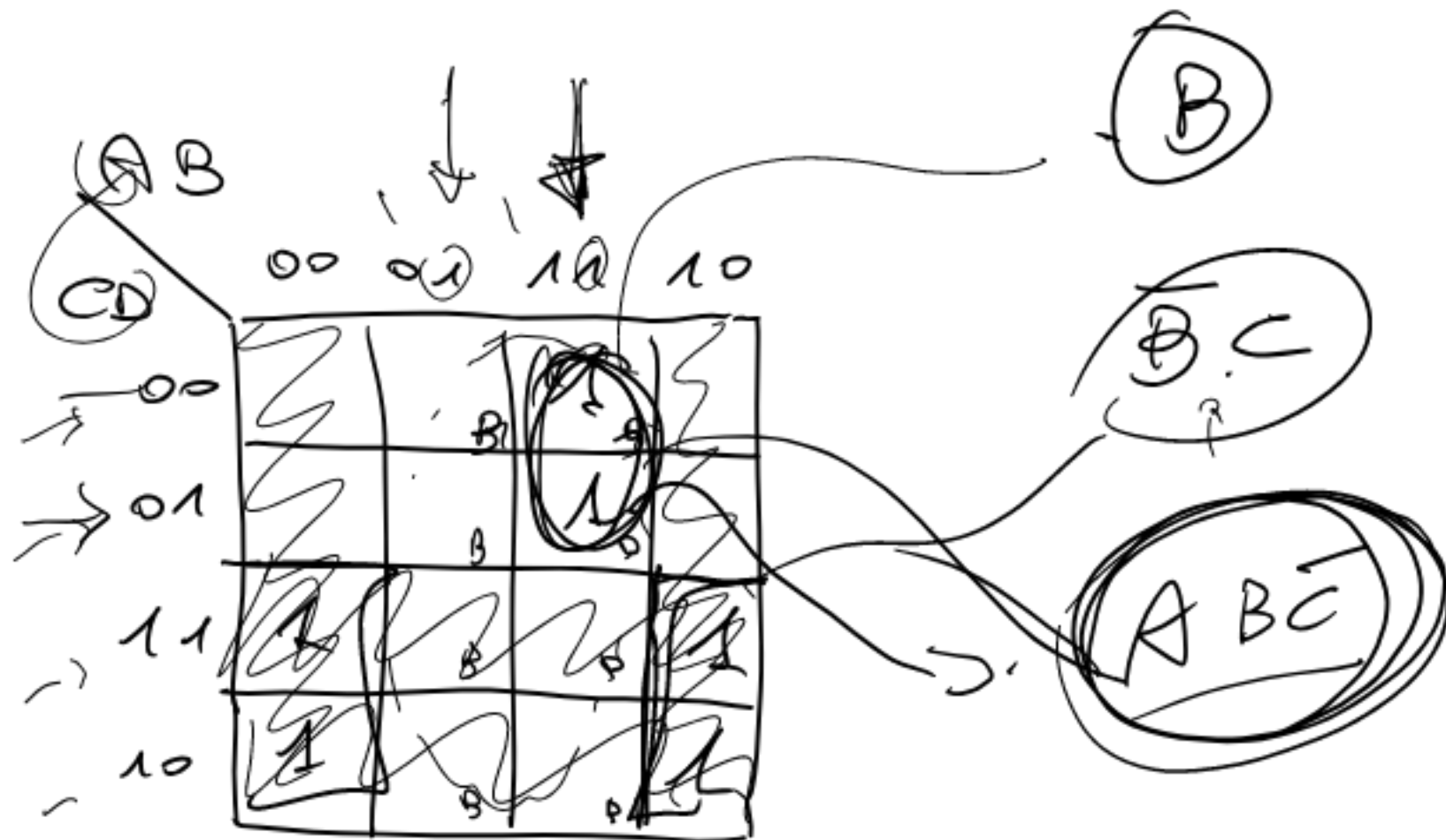

- MAPPA "QUADRATA"
- SEQ. COMBINAZIONI  
⇒ CELLE ADIACENTI
- CELLE MINTER.
- Regg.

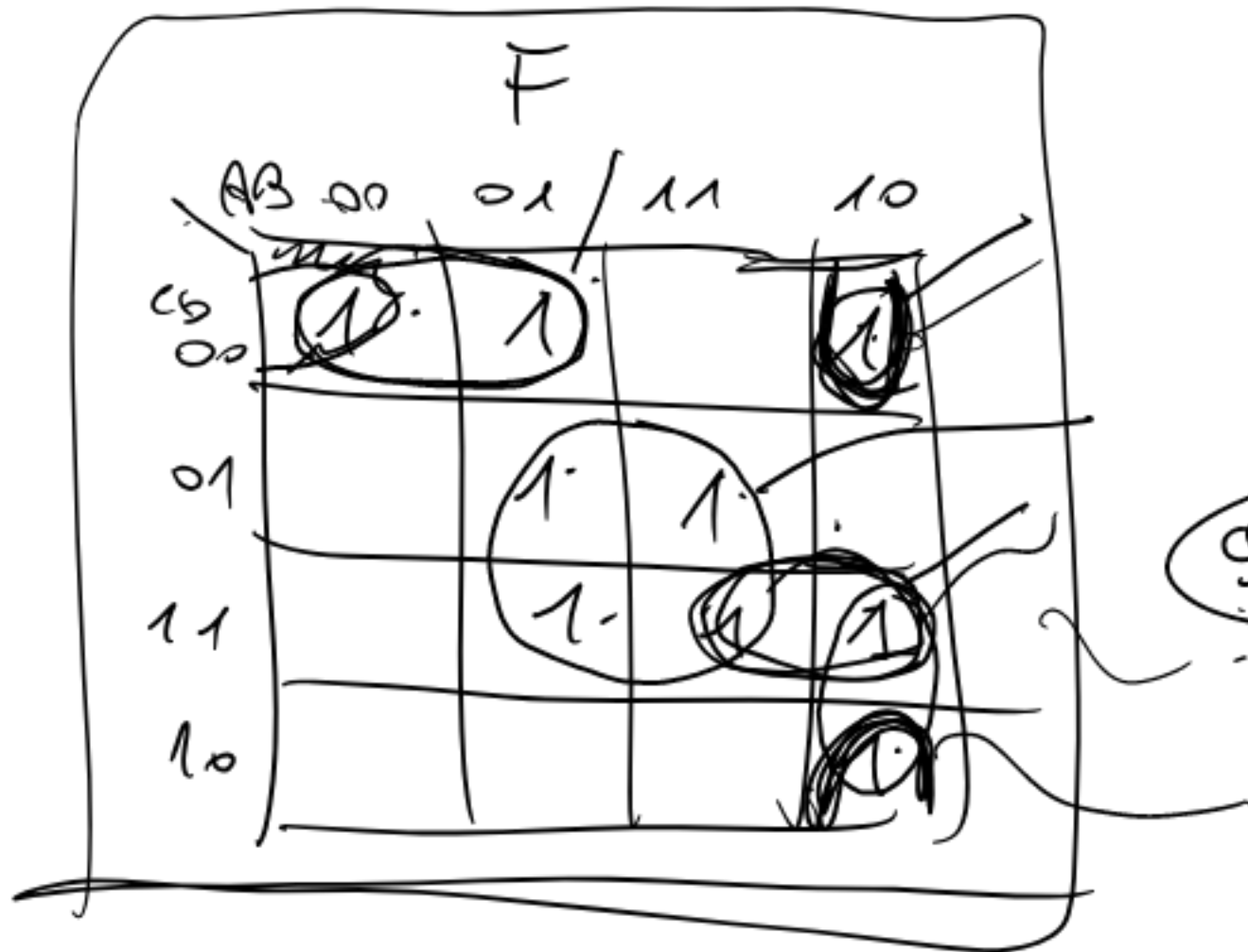- o)  $N = 2^i$
- o) N più grande possibile
- o) quadrato/rettangolo
- o) si intersecano
- o) "NO" ~~CONTRIBUTO~~



MIN TERM